

# Microelectronic Circuits

## 8<sup>th</sup> Edition


A. Sedra, K.C. Smith  
T. Chan Carusone, V. Gaudet

*Spice Examples for  
Appendix B*

*Prepared by: Nijwm Wary  
2019*

**Example S.2.1**


(a) The schematic for this example is shown below

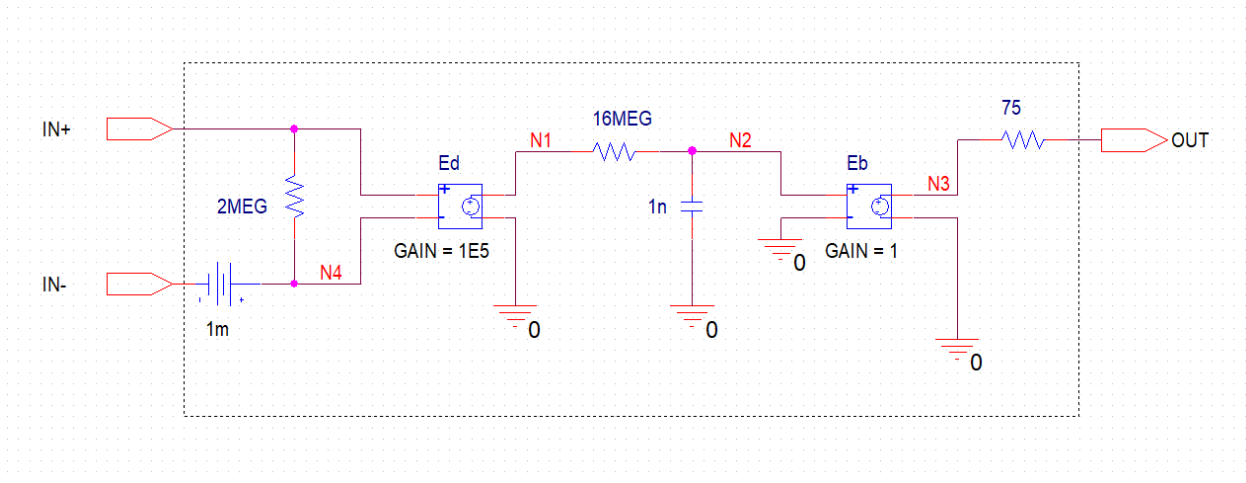**Netlist:**

The netlist is given below

```
.SUBCKT OPAMP_MACRO      IN+ IN- OUT
Ro          OUT N3  75
VOS        N4 IN- 1m
Eb         N3 0 N2 0 1
Rb         N2 N1 16MEG
Cb         0 N2 1n
Ed         N1 0 IN+ N4 1E5
Rid        IN+ N4 2MEG
.ENDS
```

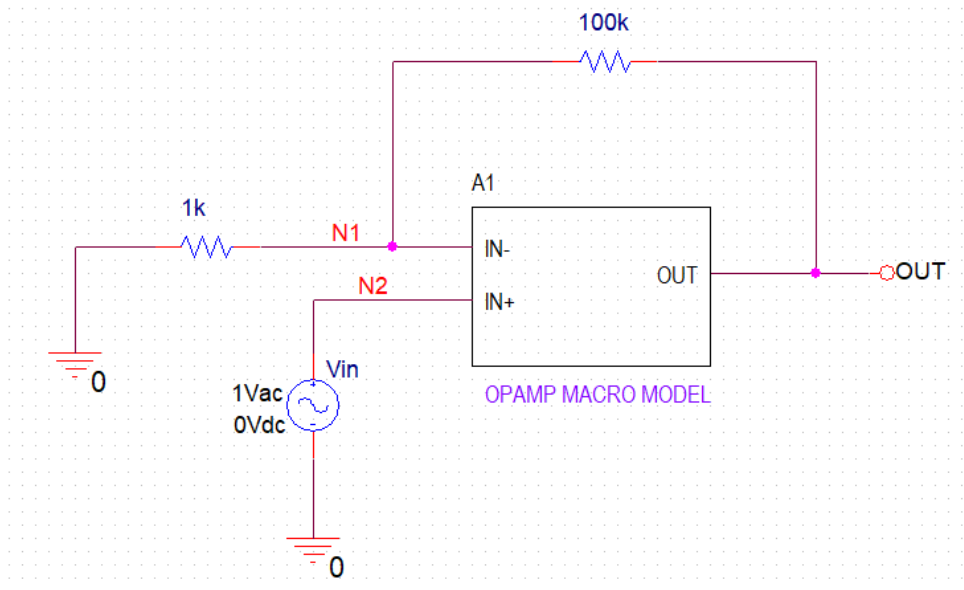(b) The schematic for this part of the example, sub-parts (i), (ii) and (iii) is shown below



### Netlist:

Copy the netlist given below and paste it into a text file and save it with \*.cir extension.

```


*****Example S 2.1(b) (i), (ii), (iii)*****
***** Main circuit begins here*****
R1      N1 0 1k
Vin     N2 0 DC 0Vdc AC 1Vac
R2      N1 OUT 100k
X_A1    N2 N1 OUT OPAMP_MACRO
***** Main circuit ends here *****

***** Opamp macro model begins here *****
.SUBCKT OPAMP_MACRO  IN+ IN- OUT
Ro      OUT N3 75
VOS     N4 IN- 1m
Eb      N3 0 N2 0 1
Rb      N2 N1 16MEG
Cb      0 N2 1n
Ed      N1 0 IN+ N4 1E5
Rid     IN+ N4 2MEG
.ENDS
***** Opamp macro model ends here *****

***** Analysis begins here*****
.OP
.AC DEC 20 0.1 10MEG
.PROBE
.END
***** Analysis ends here*****

```

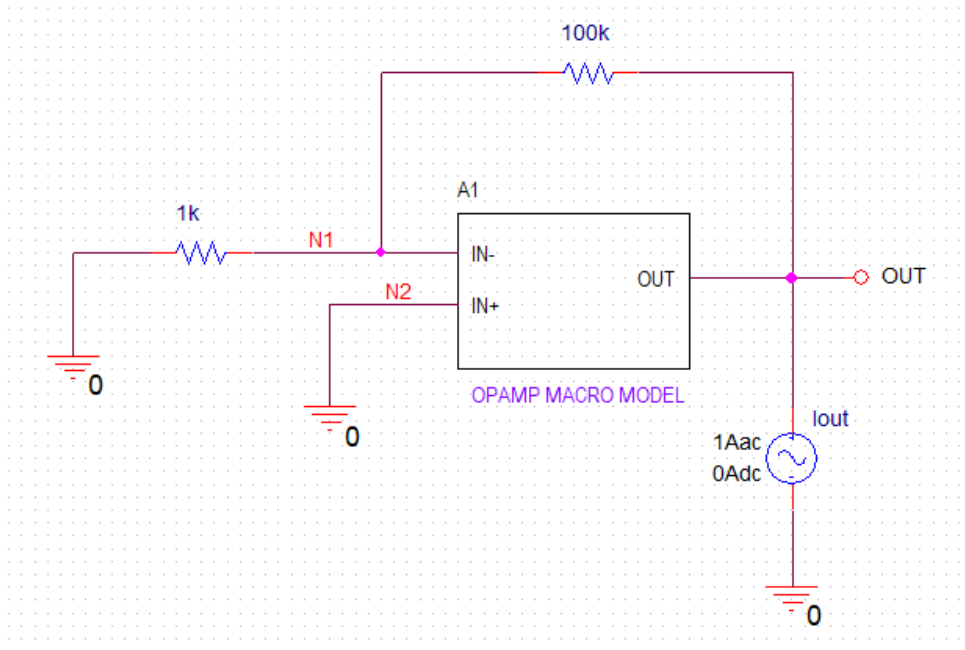The schematic sub-part (iv) is shown below



### Netlist:


Copy the netlist given below and paste it into a text file and save it with \*.cir extension.

```

*****Example S 2.1(b) (iv)*****
***** Main circuit begins here*****
Iout      OUT 0 DC 0Adc AC 1Aac
R2        N1 OUT 100k
R1        N1 0 1k
X_A1     0 N1 OUT OPAMP_MACRO
***** Main circuit ends here *****
***** Opamp macro model begins here *****
.SUBCKT OPAMP_MACRO  IN+ IN- OUT
Ro        OUT N3 75
VOS       N4 IN- 1m
Eb        N3 0 N2 0 1
Rb        N2 N1 16MEG
Cb        0 N2 1n
Ed        N1 0 IN+ N4 1E5
Rid       IN+ N4 2MEG
.ENDS
***** Opamp macro model ends here *****
***** Analysis begins here*****
.OP
.AC DEC 20 0.1 10
.PROBE
.END
***** Analysis ends here*****

```

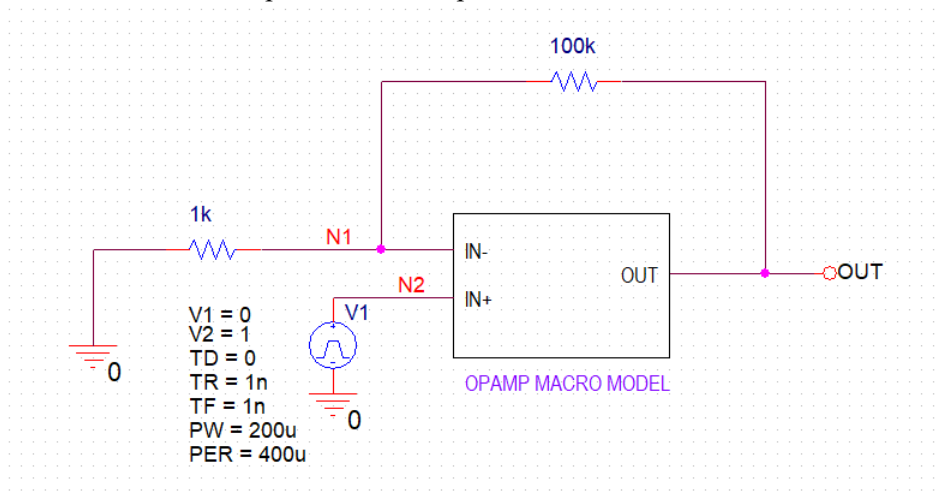(c) The schematic for this part of the example is shown below.



### Netlist:

Copy the netlist given below and paste it into a text file and save it with \*.cir extension.

```


*****Example S 2.1(c) *****
***** Main circuit begins here*****
V1      N2 0
+PULSE 0 1 10u 1n 1n 200u 400u
R1      N1 0 1k
R2      N1 OUT 100k
X_A1    N2 N1 OUT OPAMP_MACRO

***** Main circuit ends here *****
***** Opamp macro model begins here *****
.SUBCKT OPAMP_MACRO  IN+ IN- OUT
Ro      OUT N3 75
VOS     N4 IN- 1m
Eb      N3 0 N2 0 1
Rb      N2 N1 16MEG
Cb      0 N2 1n
Ed      N1 0 IN+ N4 1E5
Rid     IN+ N4 2MEG
.ENDS
***** Opamp macro model ends here *****
***** Analysis begins here*****
.TRAN 0.1uS 100uS
.PROBE
.END
***** Analysis ends here*****

```

**Example S.2.2**

The schematic of this example for calculation of AC gain is shown below

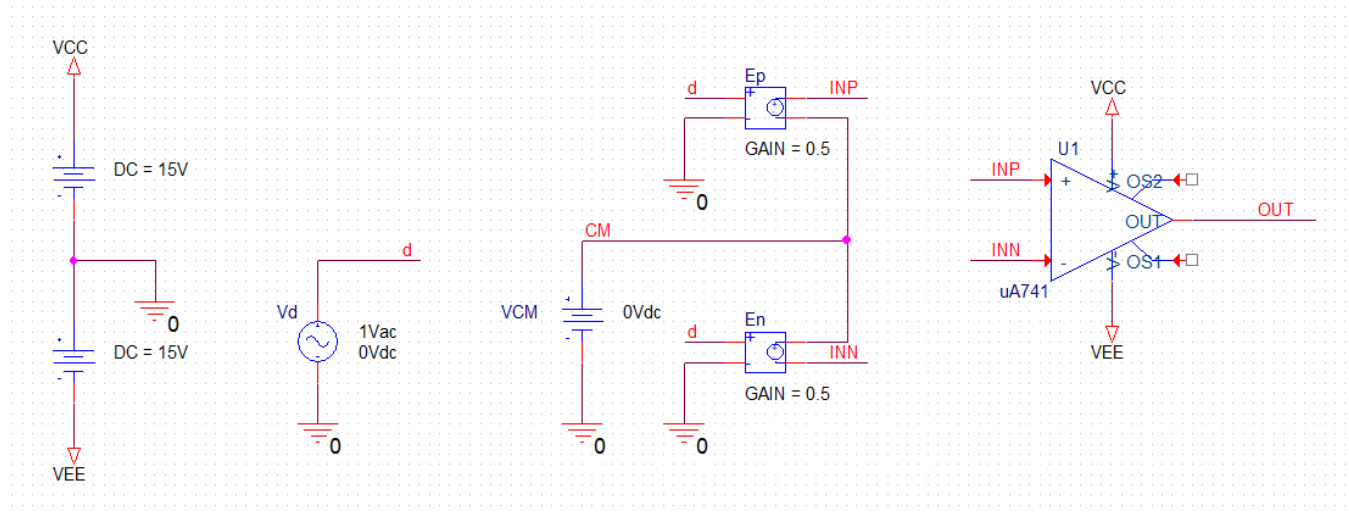**Netlist:**

Copy the netlist given below and paste it into a text file and save it with \*.cir extension.

```

*****Example S 2.2 (AC Gain) *****
***** Main circuit begins here*****
X_U1      INP INN VCC VEE OUT uA741
Ep        INP CM D 0 0.5
VCM       CM 0 0Vdc
Vd        D 0 DC 0Vdc AC 1Vac
VEE       0 VEE 15V
VCC       VCC 0 15V
En        CM INN D 0 0.5
***** Main circuit ends here *****
***** Model of uA741 begins here*****
* connections:  non-inverting input
*                | inverting input
*                | | positive power supply
*                | | | negative power supply
*                | | | | output
*                | | | | |
.subckt uA741  1 2 3 4 5
*
c1  11 12 8.661E-12
c2  6 7 30.00E-12
dc  5 53 dx
de  54 5 dx
dlp 90 91 dx
dln 92 90 dx
dp  4 3 dx
egnd 99 0 poly(2) (3,0) (4,0) 0 .5 .5
fb  7 99 poly(5) vb vc ve vlp vln 0 10.61E6 -10E6 10E6 10E6 -10E6
ga  6 0 11 12 188.5E-6
gcm 0 6 10 99 5.961E-9


```

```

iee 10 4 dc 15.16E-6
hlim 90 0 vlim 1K
q1 11 2 13 qx
q2 12 1 14 qx
r2 6 9 100.0E3
rc1 3 11 5.305E3
rc2 3 12 5.305E3
re1 13 10 1.836E3
re2 14 10 1.836E3
ree 10 99 13.19E6
ro1 8 5 50
ro2 7 99 100
rp 3 4 18.16E3
vb 9 0 dc 0
vc 3 53 dc 1
ve 54 4 dc 1
vlim 7 8 dc 0
vlp 91 0 dc 40
vln 0 92 dc 40
.model dx D(Is=800.0E-18 Rs=1)
.model qx NPN(Is=800.0E-18 Bf=93.75)
.ends
***** Model of uA741 ends here*****
***** Analysis begins here*****
.AC DEC 20 1 10MEG
.PROBE
.END
***** Analysis ends here*****

```

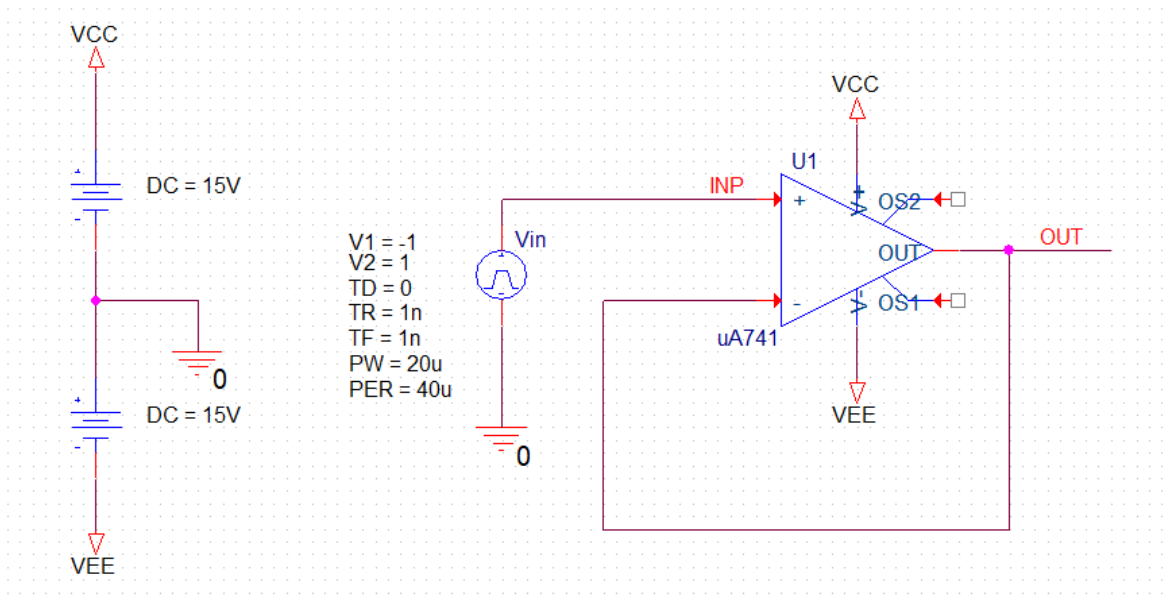The schematic of this example for investigating SR limitations is shown below



**Netlist:**

Copy the netlist given below and paste it into a text file and save it with \*.cir extension.

```

*****Example S 2.2 (Slew Rate) *****
***** Main circuit begins here*****


X_U1          INP OUT VCC VEE OUT uA741
Vin           INP 0
+PULSE -1 1 0 1n 1n 20u 40u
VEE           0 VEE 15V
VCC           VCC 0 15V
***** Main circuit ends here *****
***** Model of uA741 begins here*****
* connections:  non-inverting input
*               | inverting input
*               | | positive power supply
*               | | | negative power supply
*               | | | | output
*               | | | | |
.subckt uA741  1 2 3 4 5
*
c1  11 12 8.661E-12
c2  6 7 30.00E-12
dc  5 53 dx
de  54 5 dx
dlp 90 91 dx
dln 92 90 dx
dp  4 3 dx
egnd 99 0 poly(2) (3,0) (4,0) 0 .5 .5
fb  7 99 poly(5) vb vc ve vlp vln 0 10.61E6 -10E6 10E6 10E6 -10E6
ga  6 0 11 12 188.5E-6
gcm 0 6 10 99 5.961E-9
iee 10 4 dc 15.16E-6
hlim 90 0 vlim 1K
q1  11 2 13 qx
q2  12 1 14 qx
r2  6 9 100.0E3
rc1 3 11 5.305E3
rc2 3 12 5.305E3
re1 13 10 1.836E3
re2 14 10 1.836E3
ree 10 99 13.19E6
ro1 8 5 50
ro2 7 99 100
rp  3 4 18.16E3
vb  9 0 dc 0
vc  3 53 dc 1
ve  54 4 dc 1
vlim 7 8 dc 0
vlp 91 0 dc 40
vln 0 92 dc 40
.model dx D(Is=800.0E-18 Rs=1)
.model qx NPN(Is=800.0E-18 Bf=93.75)
.ends
***** Model of uA741 ends here*****
***** Analysis begins here*****
.TRAN 0.01uS 80uS
.PROBE
.END
***** Analysis ends here*****

```


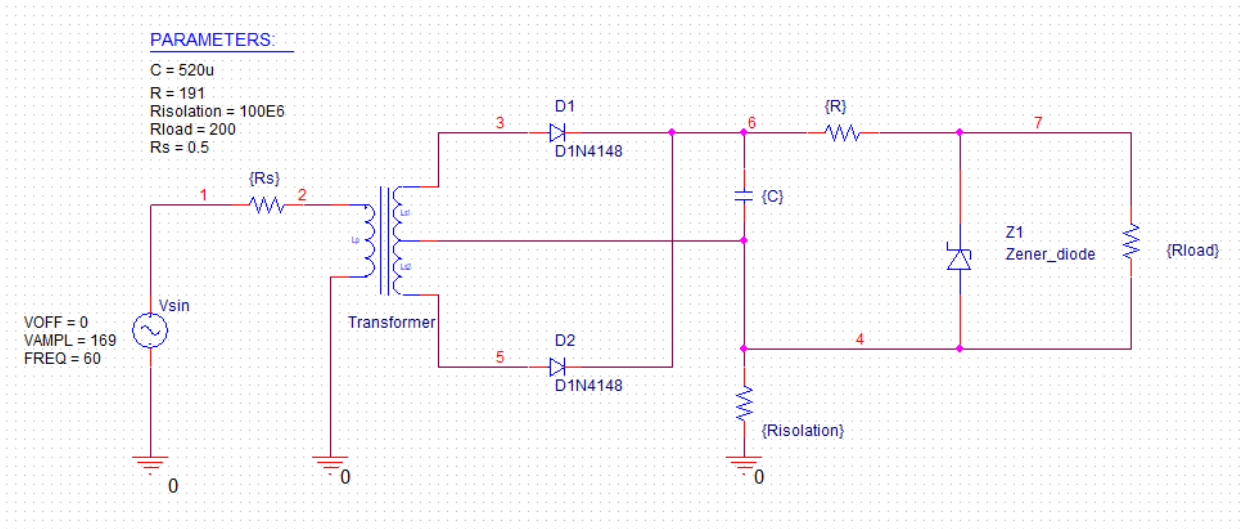
### Example S.4.1

The schematic of this example is shown below.



### Netlist:

Copy the netlist given below and paste it into a text file and save it with \*.cir extension.

```
*****Example S 4.1 *****
***** Main circuit begins here*****
D1      3 6 D1N4148
D2      5 6 D1N4148
R3      7 4 {Rload}
Vsin    1 0
+SIN 0 169 60 0 0 0
C1      4 6 {C}
R1      7 6 {R}
X_Z1    4 7 ZENER_DIODE
R4      4 0 {Risolation}
R2      2 1 {Rs}
X_TX1   0 2 3 4 5 TX
.PARAM  rs=0.5 risolation=100e6 c=520u rload=200 r=191
***** Main circuit ends here *****

***** Model of ZENER DIODE begins here*****
.SUBCKT ZENER_DIODE 1 2
*connections:  | |
*              |
*              andode |
*              cathode
Dforward 1 2 1mA_diode
Dreverse 2 4 ideal_diode
Vz0 4 3 DC 4.9V
Rz 1 3 10
* diode model statements
.model 1mA_diode D (Is=100pA n=1.679)
.model ideal_diode D (Is=100pA n=0.01)
.ends ZENER_DIODE
***** Model of ZENER DIODE ends here*****
```


```
***** Model of 1N4148 Diode (from EVAL library in PSpice) begins here*****
.model D1N4148 D(Is=2.682n N=1.836 Rs=.5664 Ikf=44.17m Xti=3 Eg=1.11 Cjo=4p
+
M=.3333 Vj=.5 Fc=.5 Isr=1.565n Nr=2 Bv=100 Ibv=100u Tt=11.54n)
***** Model of 1N4148 Diode (from EVAL library in PSpice) ends here*****

***** Model of Nonlinear Transformer with Center-Tapped Secondary begins here*****
.subckt TX 1 2 3 4 5 Params:
Lp 2 1 10mH
Ls1 3 4 52uH
Ls2 4 5 52uH
K1 Lp Ls1 0.999
K2 Lp Ls2 0.999
K3 Ls1 Ls2 0.999
.ends TX
***** Model of Nonlinear Transformer with Center-Tapped Secondary ends here*****

***** Analysis begins here*****
.TRAN 0.1mS 200mS
.PROBE
.END
***** Analysis ends here*****
```

**Example S.6.1**

The schematic of this example is shown below.

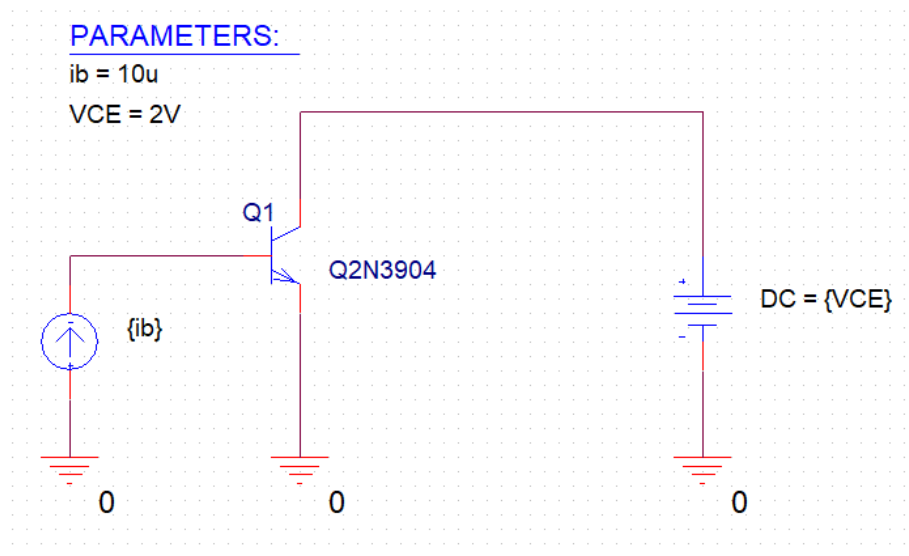**Netlist:**

Copy the netlist given below and paste it into a text file and save it with \*.cir extension.


```

*****Example S 6.1 *****
***** Main circuit begins here*****
Q1      N111317 N111357 0 Q2N3904
V1      N111317 0 {VCE}
Ibase   0 N111357 DC {ib}
.PARAM  ib=10u vce=2v
***** Main circuit ends here*****
*****Model for 2N3904 NPN BJT (from Eval library in Pspice) begins here*****
.model Q2N3904 NPN(Is=6.734f Xti=3 Eg=1.11 Vaf=74.03 Bf=416.4 Ne=1.259
+      Ise=6.734f Ikf=66.78m Xtb=1.5 Br=.7371 Nc=2 Isc=0 Ikr=0 Rc=1
+      Cjc=3.638p Mjc=.3085 Vjc=.75 Fc=.5 Cje=4.493p Mje=.2593 Vje=.75
+      Tr=239.5n Tf=301.2p Itf=.4 Vtf=4 Xtf=2 Rb=10)
*****Model for 2N3904 NPN BJT (from Eval library in Pspice) ends here*****
***** Analysis begins here*****
.DC [LIN] Ibase 1u 200u 1u
.PROBE
.END
***** Analysis ends here*****

```

**Example S.7.1**

The schematic of this example is shown below.

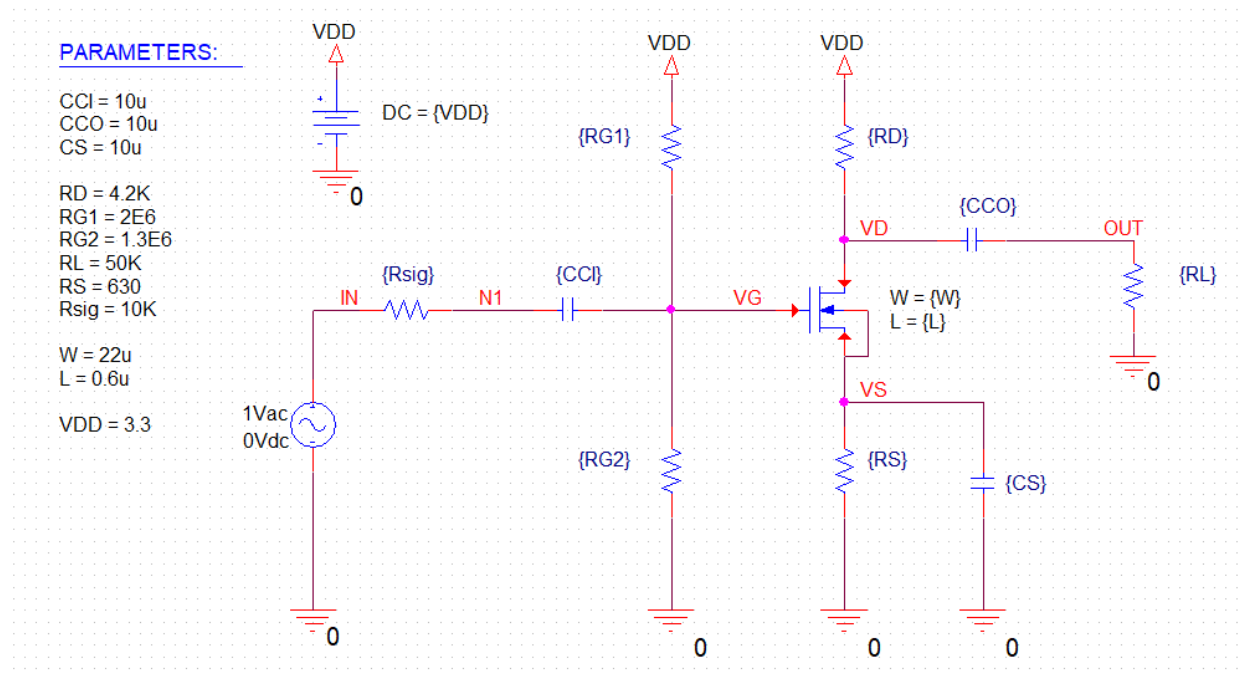**Netlist:**

Copy the netlist given below and paste it into a text file and save it with \*.cir extension.


```
*****Example S 7.1 *****
***** Main circuit begins here*****
M2      VD VG VS VS NMOS0P5
+ L={L}
+ W={W}
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M=1
R11     VG VDD {RG1}
R16     0 VS {RS}
R15     0 VG {RG2}
R12     VD VDD {RD}
C6      0 VS {CS}
C4      VD OUT {CCO}
R14     IN N1 {Rsig}
C5      N1 VG {CCI}
R13     0 OUT {RL}
V3      IN 0 DC 0Vdc AC 1Vac
V1      VDD 0 {VDD}
.PARAM  RS=630 CS=10u L=0.6u CCO=10u VDD=3.3 CCI=10u RG1=2e6 RL=50k RG2=1.3e6
+ RSIG=10k W=22u RD=4.2k
***** Main circuit ends here*****
```

```
*****Model for NMOS in 0.5um CMOS Technology begins here*****
*
  (created by Anas Hamoui & Olivier Trescases)
.model NMOS0P5 NMOS(Level=1 VTO=0.7 GAMMA=0.5 PHI=0.8
+
  LD=0.08E-06 WD=0 UO=460 LAMBDA=0.1 TOX=9.5E-9 PB=0.9 CJ=0.57E-3
+
  CJSW=120E-12 MJ=0.5 MJSW=0.4 CGDO=0.4E-9 JS=10E-9 CGBO=0.38E-9
+
  CGSO=0.4E-9)
*****Model for NMOS in 0.5um CMOS Technology ends here*****

***** Analysis begins here*****
.OP
.AC DEC 20 10m 10G
.PROBE
.END
***** Analysis ends here*****
```

**Example S.7.2**

The schematic of this example is shown below.

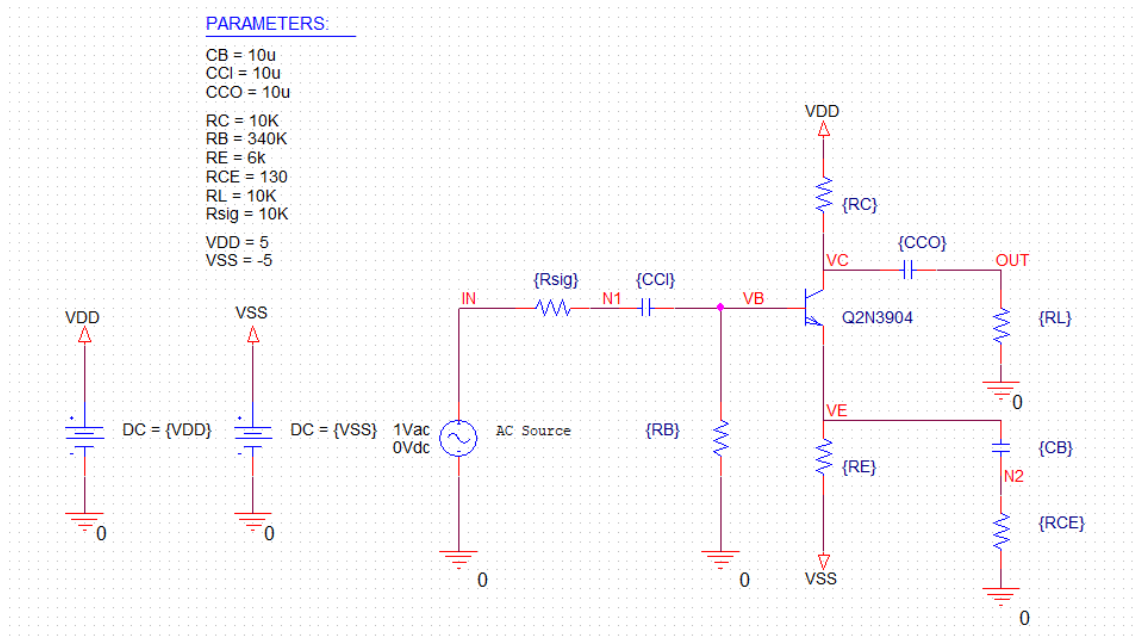**Netlist:**

Copy the netlist given below and paste it into a text file and save it with \*.cir extension.

```

*****Example S 7.2 *****
***** Main circuit begins here*****
C2      N1 VB  {CCI}
R7      0 VB  {RB}
V5      IN 0 DC 0Vdc AC 1Vac
Q2      VC VB VE Q2N3904
V7      VSS 0 {VSS}
R4      VC VDD {RC}
R9      0 N2  {RCE}
R8      VSS VE {RE}
C1      VC OUT {CCO}
C3      N2 VE {CB}
R6      0 OUT {RL}
R5      IN N1 {Rsig}
V6      VDD 0 {VDD}
.PARAM rc=10k cb=10u re=1 vss=-5 rb=340k re1=6k cco=10u vdd=5 cci=10u rl=10k
+ rsig=10k rx=1 re=6k rce=130
***** Main circuit ends here*****


*****Model for 2N3904 NPN BJT (from Eval library in Pspice) begins here*****
.model Q2N3904 NPN(Is=6.734f Xti=3 Eg=1.11 Vaf=74.03 Bf=416.4 Ne=1.259
+ Ise=6.734f Ikf=66.78m Xtb=1.5 Br=.7371 Nc=2 Isc=0 Ikr=0 Rc=1
+ Cjc=3.638p Mjc=.3085 Vjc=.75 Fc=.5 Cje=4.493p Mje=.2593 Vje=.75
+ Tr=239.5n Tf=301.2p Itf=.4 Vtf=4 Xtf=2 Rb=10)
*****Model for 2N3904 NPN BJT (from Eval library in Pspice) ends here*****

```

```
***** Analysis begins here*****  
.OP  
.AC DEC 20 1 10MEG  
.PROBE  
.END  
***** Analysis ends here*****
```

**Example S.7.3**

The schematic of this example for finding  $A_v$  is shown below.

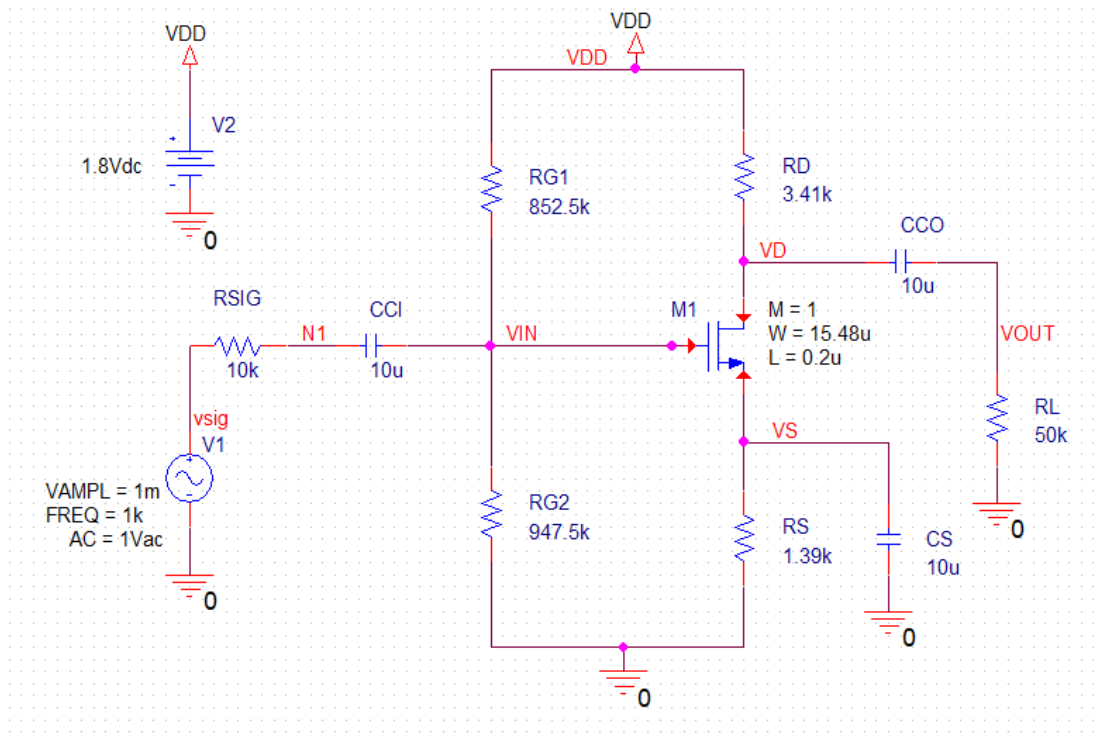**Netlist:**

Copy the netlist given below and paste it into a text file and save it with \*.cir extension.

```

*****Example S 7.3 *****
***** Main circuit begins here*****
R_RG1      VIN VDD 852.5k TC=0,0
R_RG2      0 VIN 947.5k TC=0,0
M_M1       VD VIN VS 0 NMOS4
+ L=0.2u
+ W=15.48u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M=1
R_RD       VD VDD 3.41k TC=0,0
R_RS       0 VS 1.39k TC=0,0
R_RL       0 VOUT 50k TC=0,0
C_CCO      VD VOUT 10u TC=0,0
C_CS       0 VS 10u TC=0,0
C_CCI      N1 VIN 10u TC=0,0
V_V1       VSIG 0 AC 1Vac
+SIN 0 1m 1k 0 0 0
R_RSIG     N1 VSIG 10k TC=0,0
V_V2       VDD 0 1.8Vdc


```



```
***** Main circuit ends here*****  
  
*****NMOS models begin here*****  
.model NMOS4 NMOS(LEVEL= 1 VTO=0.45 GAMMA= 0.3 PHI=0.84  
+ LAMBDA= 0.08  
+ RS= 0.0  
+ RD= 0.0  
+ CBD= 0.0  
+ CBS= 0.0  
+ IS= 1.0e-14  
+ PB= 0.9  
+ CGSO= 0.3665e-9  
+ CGDO= 0.3665e-9  
+ CGBO= 0.38e-9  
+ RSH= 0  
+ CJ= 1.6e-3  
+ MJ= 0.5  
+ CJSW= 2.0405e-10  
+ MJSW= 0.200379  
+ JS= 8.38e-6  
+ TOX= 4.08e-09  
+ NSS= 0.0  
+ TPG= 1.0  
+ LD= 10e-9  
+ U0 = 291  
+ KF= 0.0  
+ AF= 1.0  
+ FC= 0.5  
+ TNOM= 27  
+ )  
*****NMOS models end here*****  
  
***** Analysis begins here*****  
.OP  
.TRAN 0.01m 2.5m  
.PROBE  
.END  
***** Analysis ends here*****
```

**Example S.8.1**

The schematic of this example is shown below.

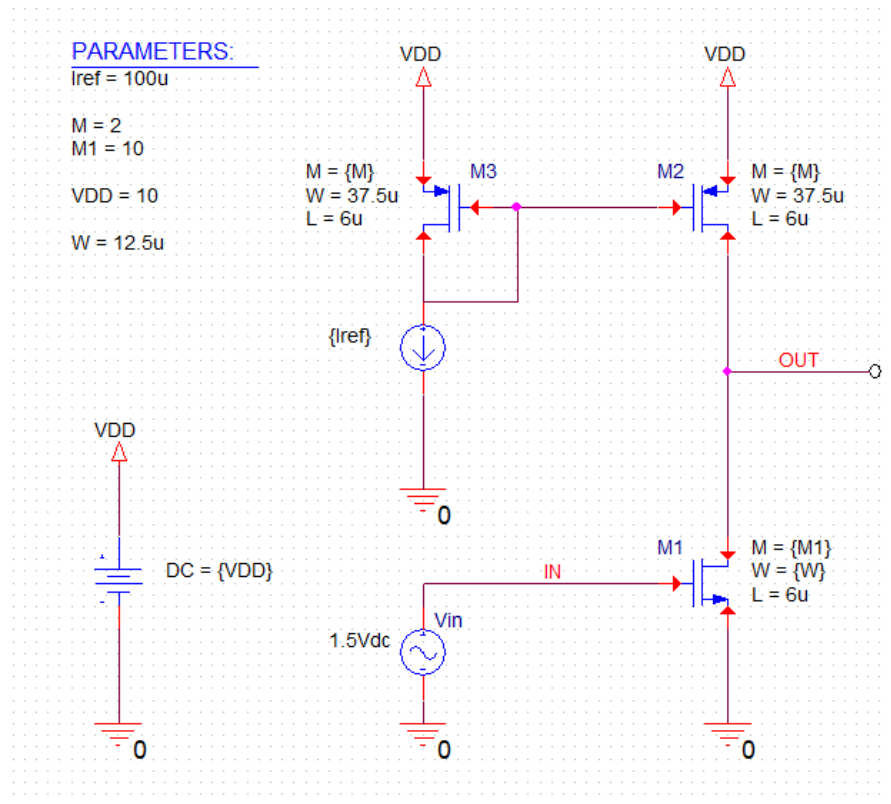**Netlist:**

Copy the netlist given below and paste it into a text file and save it with \*.cir extension.

```
*****Example S 8.1 *****
***** Main circuit begins here*****
M1      OUT IN 0 0 NMOS5P0
+ L=6u
+ W={W}
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M={M1}
V2      VDD 0 {VDD}
M3      VG23 VG23 VDD VDD PMOS5P0
+ L=6u
+ W=37.5u
+ AD=1.72E-10
+ AS=1.72E-10
+ PD=5.25e-5
+ PS=5.25E-5
+ M={M}
I2      VG23 0 DC {Iref}
```

```


V Vin          IN 0 DC 1.5Vdc AC 1Vac
M2            OUT VG23 VDD VDD PMOS5P0
+ L=6u
+ W=37.5u
+ AD=1.72E-10
+ AS=1.72E-10
+ PD=5.25e-5
+ PS=5.25E-5
+ M={M}
.PARAM  iref=100u m=2 vdd=10 ml=10 w=12.5u
***** Main circuit ends here*****
*****Model for NMOS in 5um CMOS Technology begins here*****
*
      (created by Anas Hamoui & Olivier Trescases)
.model NMOS5P0 NMOS(Level=1 VTO=1 GAMMA=1.4 PHI=0.7
+
      LD=0.7E-06 WD=0 UO=750 LAMBDA=0.01 TOX=85E-9 PB=0.7 CJ=0.4E-3
+
      CJSW=0.8E-9 MJ=0.5 MJSW=0.5 CGDO=0.4E-9 JS=1E-6 CGBO=0.2E-9
+
      CGSO=0.4E-9)
*****Model for NMOS in 5um CMOS Technology ends here*****
*****Model for PMOS in 5um CMOS Technology begins here*****
*
      (created by Anas Hamoui & Olivier Trescases)
.model PMOS5P0 PMOS(Level=1 VTO=-1 GAMMA=0.65 PHI=0.65
+
      LD=0.6E-06 WD=0 UO=250 LAMBDA=0.03 TOX=85E-9 PB=0.7 CJ=0.18E-3
+
      CJSW=0.6E-9 MJ=0.5 MJSW=0.5 CGDO=0.4E-9 JS=1E-6 CGBO=0.2E-9
+
      CGSO=0.4E-9)
*****Model for PMOS in 5um CMOS Technology ends here*****

***** Analysis begins here*****
.DC [LIN] V_Vin  0 10 0.05
.PROBE
.END
***** Analysis ends here*****

```

**Example S.9.1**

The schematic of this example is shown below.

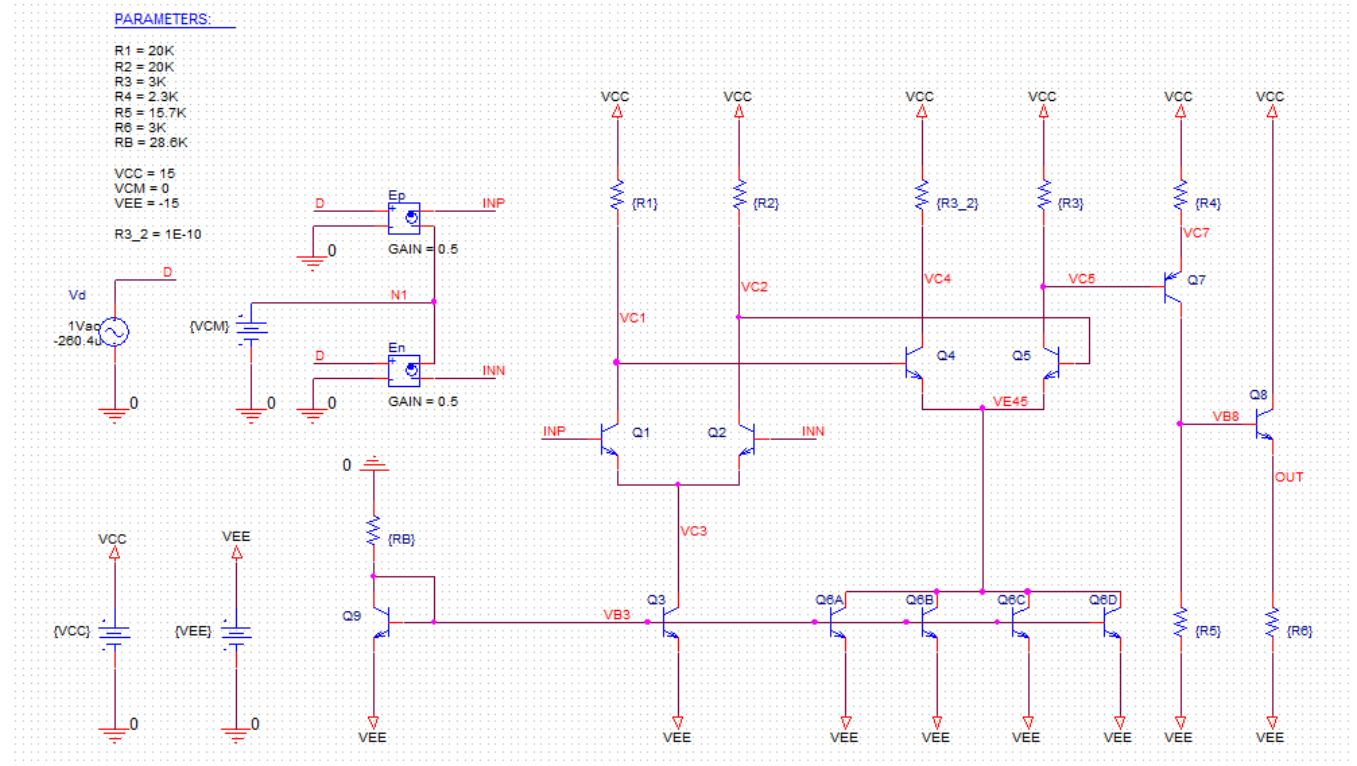**Netlist:**

Copy the netlist given below and paste it into a text file and save it with \*.cir extension.

```
*****Example S 9.1 *****
***** Main circuit begins here*****
Q_Q2      VC2 INN VC3 Q2N3904
Q_Q1      VC1 INP VC3 Q2N3904
R_R3      VC5 VCC {R3}
R_R5      VEE VB8 {R5}
Q_Q5      VC5 VC2 VE45 Q2N3904
Q_Q4      VC4 VC1 VE45 Q2N3904
R_R4      VC7 VCC {R4}
R_RB      VB3 0 {RB}
Q_Q6A     VE45 VB3 VEE Q2N3904
Q_Q6D     VE45 VB3 VEE Q2N3904
V_VCC     VCC 0 {VCC}
V_Vd      D 0 DC -260.4u AC 1Vac
Q_Q6B     VE45 VB3 VEE Q2N3904
V_VEE     VEE 0 {VEE}
E_En      N1 INN D 0 0.5
Q_Q8      VCC VB8 OUT Q2N3904
Q_Q9      VB3 VB3 VEE Q2N3904
R_R2      VC2 VCC {R2}
R_R1      VC1 VCC {R1}
```

```

Q_Q3      VC3 VB3 VEE Q2N3904
Q_Q7      VB8 VC5 VC7 Q2N3906
R_R6      VEE OUT {R6}
R_R7      VC4 VCC {R3_2}
Q_Q6C     VE45 VB3 VEE Q2N3904
E_Ep      INP N1 D 0 0.5
V_VCM     N1 0 {VCM}
.PARAM    vcm=0 rb=28.6k vee=-15 r6=3k r5=15.7k r3_2=1e-10 r4=2.3k r3=3k r2=20k
+ vcc=15 r1=20k
***** Main circuit ends here*****


*****Model for 2N3904 NPN BJT (from Eval library in Pspice) begins here*****
.model Q2N3904 NPN(Is=6.734f Xti=3 Eg=1.11 Vaf=74.03 Bf=416.4 Ne=1.259
+ Ise=6.734f Ikf=66.78m Xtb=1.5 Br=.7371 Nc=2 Isc=0 Ikr=0 Rc=1
+ Cjc=3.638p Mjc=.3085 Vjc=.75 Fc=.5 Cje=4.493p Mje=.2593 Vje=.75
+ Tr=239.5n Tf=301.2p Itf=.4 Vtf=4 Xtf=2 Rb=10)
*****Model for 2N3904 NPN BJT (from Eval library in Pspice) ends here*****

*****Model for 2N3906 NPN BJT (from Eval library in Pspice) begins here*****
.model Q2N3906 PNP(Is=1.41f Xti=3 Eg=1.11 Vaf=18.7 Bf=180.7 Ne=1.5 Ise=0
+ Ikf=80m Xtb=1.5 Br=4.977 Nc=2 Isc=0 Ikr=0 Rc=2.5 Cjc=9.728p
+ Mjc=.5776 Vjc=.75 Fc=.5 Cje=8.063p Mje=.3677 Vje=.75 Tr=33.42n
+ Tf=179.3p Itf=.4 Vtf=4 Xtf=6 Rb=10)
*****Model for 2N3906 NPN BJT (from Eval library in Pspice) begins here*****
***** Analysis begins here*****
.OP
.DC [LIN] V_Vd -15 15 0.1
*.AC DEC 20 1 1G
*.DC [LIN] V_VCM -15 15 0.1
.PROBE
.END
***** Analysis ends here*****

```
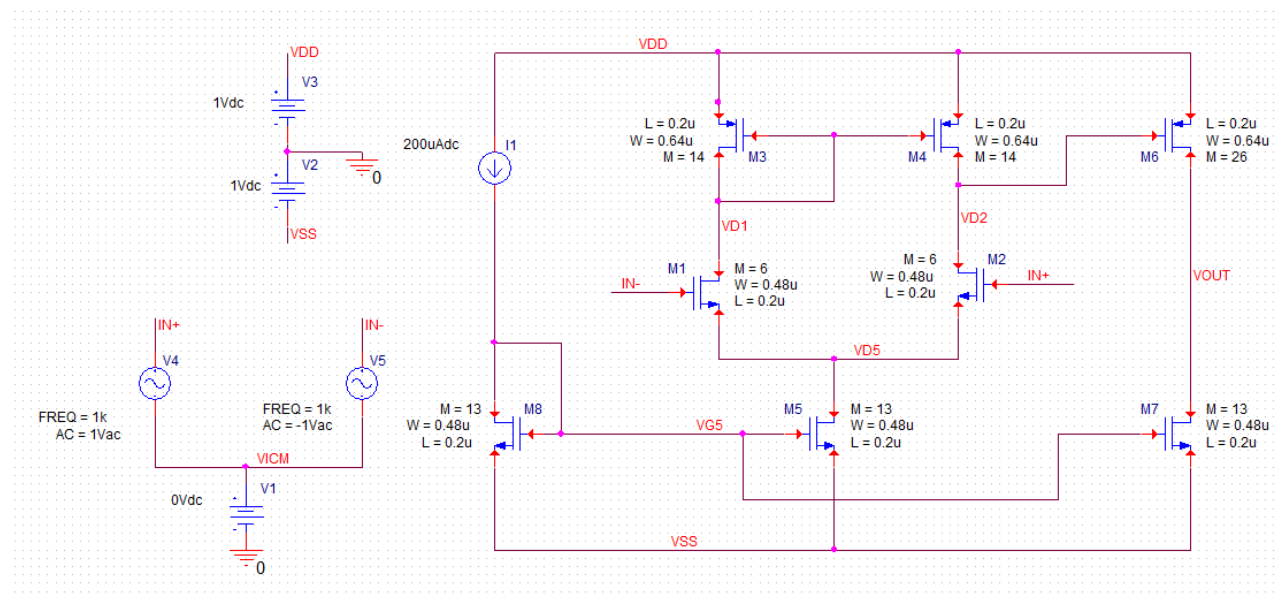
### Example S.9.2

The schematic of this example is shown below.



### Netlist:

Copy the netlist given below and paste it into a text file and save it with \*.cir extension.

```

*****Example S 9.2 *****
***** Main circuit begins here*****
M_M4      VD2 VD1 VDD VDD PMOS4
+ L=0.2u
+ W=0.64u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25e-6
+ PS=5.25E-6
+ M=14
M_M3      VD1 VD1 VDD VDD PMOS4
+ L=0.2u
+ W=0.64u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25e-6
+ PS=5.25E-6
+ M=14
M_M1      VD1 IN- VD5 0 NMOS4
+ L=0.2u
+ W=0.48u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M=6
M_M2      VD2 IN+ VD5 0 NMOS4
+ L=0.2u
+ W=0.48u

```

```


+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M=6
M_M5          VD5 VG5 VSS 0 NMOS4
+ L=0.2u
+ W=0.48u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M=13
M_M7          VOUT VG5 VSS 0 NMOS4
+ L=0.2u
+ W=0.48u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M=13
M_M6          VOUT VD2 VDD VDD PMOS4
+ L=0.2u
+ W=0.64u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M=26
M_M8          VG5 VG5 VSS 0 NMOS4
+ L=0.2u
+ W=0.48u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M=13
I_I1          VDD VG5 DC 200uAdc
V_V2          0 VSS 1Vdc
V_V1          VICM 0 0Vdc
V_V3          VDD 0 1Vdc
V_V4          IN+ VICM AC 1Vac
+SIN 0 1m 1k 0 0 0
V_V5          IN- VICM AC -1Vac
+SIN 0 1m 1k 0 0 0
***** Main circuit ends here*****
*****PMOS and NMOS models begin here*****
.model PMOS4  PMOS(Level=1 VTO=-0.5 GAMMA=0.3 PHI=0.8
+             LD=0.01E-06 WD=0 UO=132 LAMBDA=0.11 TOX=5E-9 PB=0.9 CJ=0.93E-3
+             CJSW=170E-12 MJ=0.5 MJSW=0.35 CGDO=0.35E-9 JS=5E-9 CGBO=0.38E-9
+             CGSO=0.35E-9)
.model NMOS4  NMOS(Level=1 VTO=0.5 GAMMA=0.3 PHI=0.8
+             LD=0.01E-06 WD=0 UO=370 LAMBDA=0.08 TOX=5E-9 PB=0.9 CJ=0.57E-3
+             CJSW=120E-12 MJ=0.5 MJSW=0.4 CGDO=0.4E-9 JS=10E-9 CGBO=0.38E-9
+             CGSO=0.4E-9)
*****PMOS and NMOS models end here*****
***** Analysis begins here*****
.DC [LIN] V_V1 -1.0 1.0 100m
*.AC DEC 20 1 10K
*.DC LIN V_V5 -750u 400u 20u

.PROBE
.END
***** Analysis ends here*****

```

**Example S.10.1**

The schematic of the CS amplifier of this example is shown below.

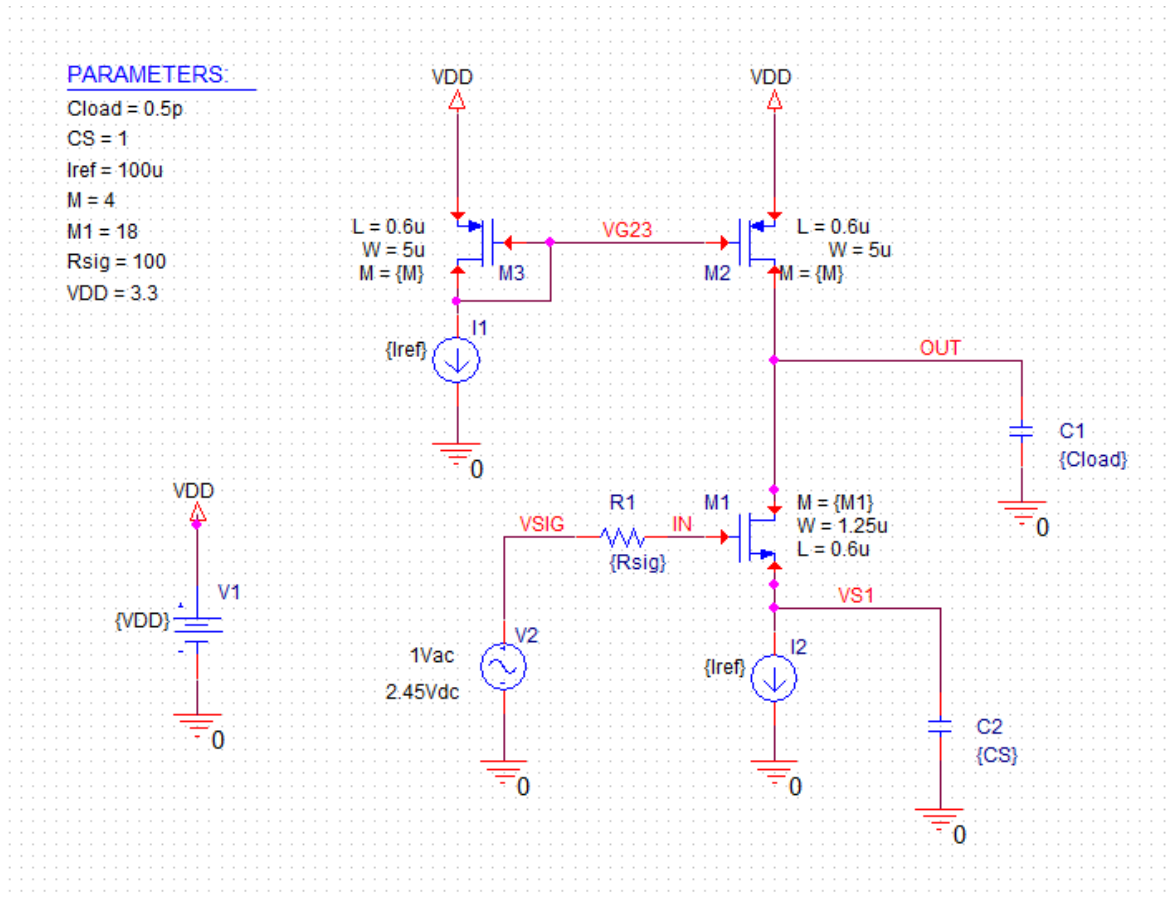**Netlist:**

Copy the netlist given below and paste it into a text file and save it with \*.cir extension.

```
*****Example S 10.1 CS amplifier *****
***** Main circuit begins here*****
M_M1      OUT IN VS1 0 NMOS0P5
+ L=0.6u
+ W=1.25u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M={M1}
I_I1      VG23 0 DC {Iref}
I_I2      VS1 0 DC {Iref}
V_V1      VDD 0 {VDD}
R_R1      VSIG IN {Rsig} TC=0,0
C_C1      0 OUT {Cload} TC=0,0
C_C2      0 VS1 {CS} TC=0,0
```



```

M_M3          VG23 VG23 VDD VDD PMOS0P5
+ L=0.6u
+ W=5u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25e-6
+ PS=5.25E-6
+ M={M}
M_M2          OUT VG23 VDD VDD PMOS0P5
+ L=0.6u
+ W=5u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25e-6
+ PS=5.25E-6
+ M={M}
V_V2          VSIG 0 AC 1Vac
+SIN 2.45Vdc 1 1k 0 0 0
.PARAM  iref=100u cs=1 m=4 vdd=3.3 cload=0.5p rsig=100 ml=18
***** Main circuit ends here*****


*****Model for NMOS in 0.5um CMOS Technology begins here*****
*
  (created by Anas Hamoui & Olivier Trescases)
.model NMOS0P5 NMOS(Level=1 VTO=0.7 GAMMA=0.5 PHI=0.8
+
  LD=0.08E-06 WD=0 UO=460 LAMBDA=0.1 TOX=9.5E-9 PB=0.9 CJ=0.57E-3
+
  CJSW=120E-12 MJ=0.5 MJSW=0.4 CGDO=0.4E-9 JS=10E-9 CGBO=0.38E-9
+
  CGSO=0.4E-9)
*****Model for NMOS in 0.5um CMOS Technology ends here*****

*****Model for PMOS in 0.5um CMOS Technology begins here*****
*
  (created by Anas Hamoui & Olivier Trescases)
.model PMOS0P5 PMOS(Level=1 VTO=-0.8 GAMMA=0.45 PHI=0.8
+
  LD=0.09E-06 WD=0 UO=115 LAMBDA=0.2 TOX=9.5E-9 PB=0.9 CJ=0.93E-3
+
  CJSW=170E-12 MJ=0.5 MJSW=0.35 CGDO=0.35E-9 JS=5E-9 CGBO=0.38E-9
+
  CGSO=0.35E-9)
*****Model for PMOS in 0.5um CMOS Technology ends here*****

***** Analysis begins here*****
.OP
.AC DEC 20 1 1G
.PROBE
.END
***** Analysis ends here*****

```

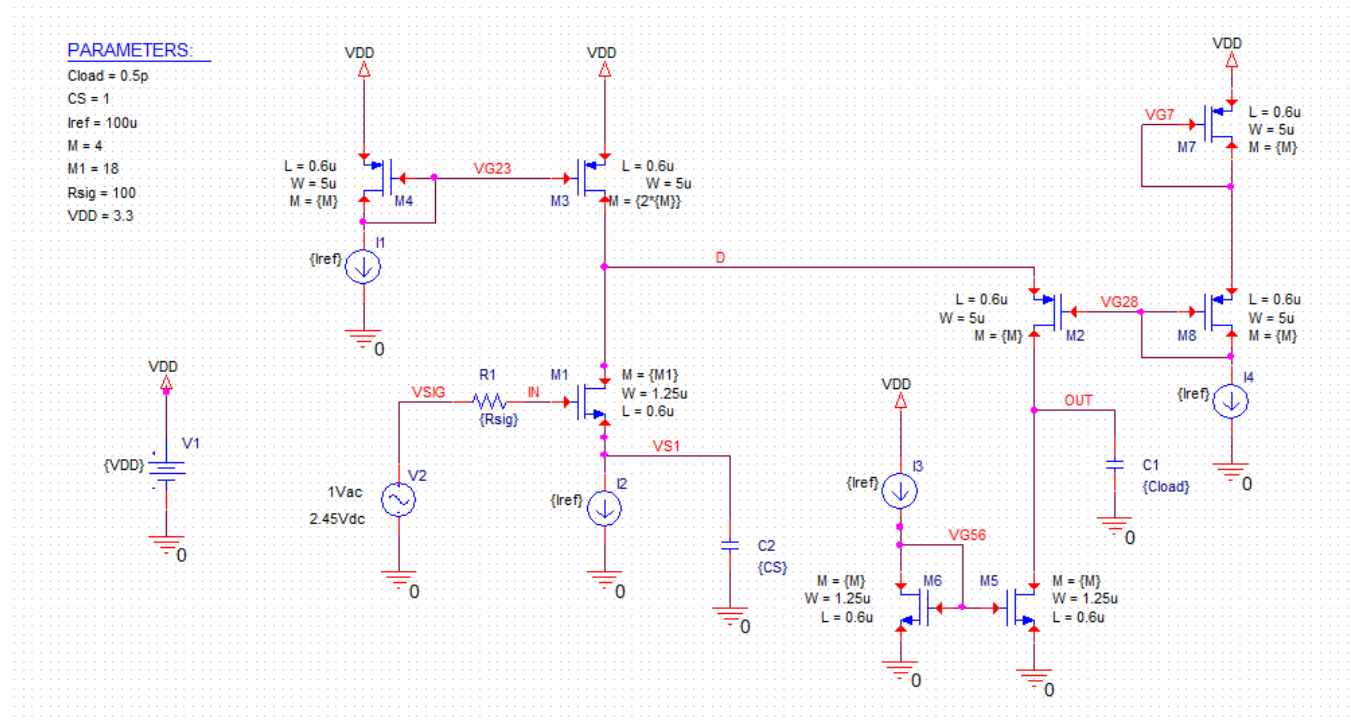The schematic of the folded-cascode amplifier of this example is shown below



### Netlist:

Copy the netlist given below and paste it into a text file and save it with \*.cir extension.

```
*****Example S 10.1 folded-cascode amplifier *****
***** Main circuit begins here*****
I_I2      VS1 0 DC {Iref}
I_I1      VG23 0 DC {Iref}
M_M3      D VG23 VDD VDD PMOS0P5
+ L=0.6u
+ W=5u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25e-6
+ PS=5.25E-6
+ M={2*{M}}
R_R1      VSIG IN {Rsig} TC=0,0
C_C2      0 VS1 {CS} TC=0,0
V_V2      VSIG 0 AC 1Vac
+SIN 2.45Vdc 1 1k 0 0 0
M_M1      D IN VS1 0 NMOS0P5
+ L=0.6u
+ W=1.25u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
```

```

+ M={M1}
M_M4      VG23 VG23 VDD VDD PMOS0P5
+ L=0.6u
+ W=5u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25e-6
+ PS=5.25E-6
+ M={M}
V_V1      VDD 0 {VDD}
C_C1      0 OUT {Cload} TC=0,0
M_M2      OUT VG28 D VDD PMOS0P5
+ L=0.6u
+ W=5u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25e-6
+ PS=5.25E-6
+ M={M}
M_M7      VG7 VG7 VDD VDD PMOS0P5
+ L=0.6u
+ W=5u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25e-6
+ PS=5.25E-6
+ M={M}
M_M8      VG28 VG28 VG7 VDD PMOS0P5
+ L=0.6u
+ W=5u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25e-6
+ PS=5.25E-6
+ M={M}
I_I3      VDD VG56 DC {Iref}
I_I4      VG28 0 DC {Iref}
M_M5      OUT VG56 0 0 NMOS0P5
+ L=0.6u
+ W=1.25u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M={M}
M_M6      VG56 VG56 0 0 NMOS0P5
+ L=0.6u
+ W=1.25u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M={M}
.PARAM   iref=100u cs=1 m=4 vdd=3.3 cload=0.5p rsig=100 ml=18
***** Main circuit ends here*****

*****Model for NMOS in 0.5um CMOS Technology begins here*****
*
* (created by Anas Hamoui & Olivier Trescases)
.model NMOS0P5 NMOS(Level=1 VTO=0.7 GAMMA=0.5 PHI=0.8
+ LD=0.08E-06 WD=0 UO=460 LAMBDA=0.1 TOX=9.5E-9 PB=0.9 CJ=0.57E-3
+ CJSW=120E-12 MJ=0.5 MJSW=0.4 CGDO=0.4E-9 JS=10E-9 CGBO=0.38E-9
+ CGSO=0.4E-9)
*****Model for NMOS in 0.5um CMOS Technology ends here*****


```

```
*****Model for PMOS in 0.5um CMOS Technology begins here*****
*
  (created by Anas Hamoui & Olivier Trescases)
.model PMOS0P5 PMOS(Level=1 VTO=-0.8 GAMMA=0.45 PHI=0.8
+
  LD=0.09E-06 WD=0 UO=115 LAMBDA=0.2 TOX=9.5E-9 PB=0.9 CJ=0.93E-3
+
  CJSW=170E-12 MJ=0.5 MJSW=0.35 CGDO=0.35E-9 JS=5E-9 CGBO=0.38E-9
+
  CGSO=0.35E-9)
*****Model for PMOS in 0.5um CMOS Technology ends here*****

***** Analysis begins here*****
.OP
.AC DEC 20 1 1G
.PROBE
.END
***** Analysis ends here*****
```

**Example S.10.2**

The schematic of this example is shown below.

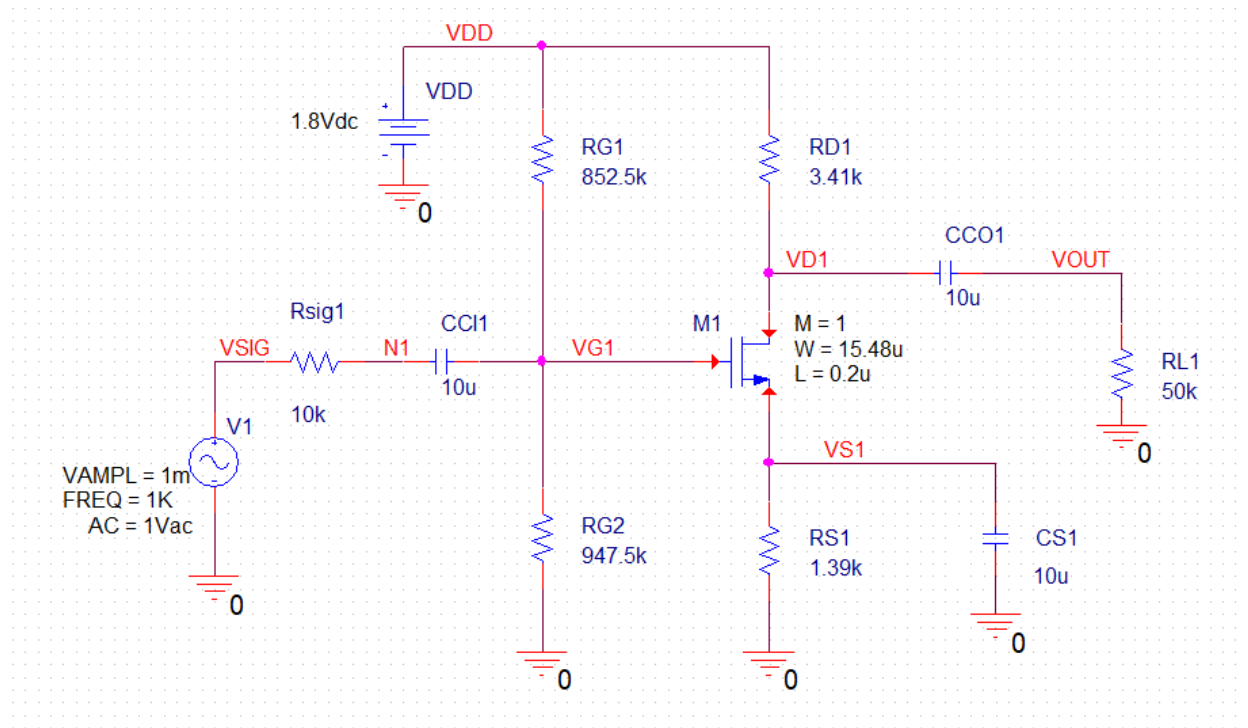**Netlist:**

Copy the netlist given below and paste it into a text file and save it with \*.cir extension.

```

*****Example S 10.2 *****
***** Main circuit begins here*****
M M1      VD1 VG1 VS1 0 NMOS4
+ L=0.2u
+ W=15.48u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M=1
R RG1     VG1 VDD 852.5k TC=0,0
R RG2     0 VG1 947.5k TC=0,0
R RD1     VD1 VDD 3.41k TC=0,0
R RS1     0 VS1 1.39k TC=0,0
R RL1     0 VOUT 50k TC=0,0
R Rsig1   N1 VSIG 10k TC=0,0
C CCI1    N1 VG1 10u TC=0,0
C CCO1    VD1 VOUT 10u TC=0,0
V V1      VSIG 0 AC 1Vac
+SIN 0 1m 1K 0 0 0
V VDD     VDD 0 1.8Vdc
C CS1     0 VS1 10u TC=0,0
***** Main circuit ends here*****


```

```
*****NMOS models end here*****
.model NMOS4    NMOS(Level=1 VTO=0.45 GAMMA=0.3 PHI=0.8
+              LD=0.01E-06 WD=0 UO=370 LAMBDA=0.08 TOX=5E-9 PB=0.9 CJ=0.57E-3
+              CJSW=120E-12 MJ=0.5 MJSW=0.4 CGDO=0.4E-9 JS=10E-9 CGBO=0.38E-9
+              CGSO=0.4E-9)
*****NMOS models end here*****

***** Analysis begins here*****
.OP
.AC DEC 20 10m 10G
.PROBE
.END
***** Analysis ends here*****
```

**Example S.11.1**

The schematic of this example using method 1 is shown below.

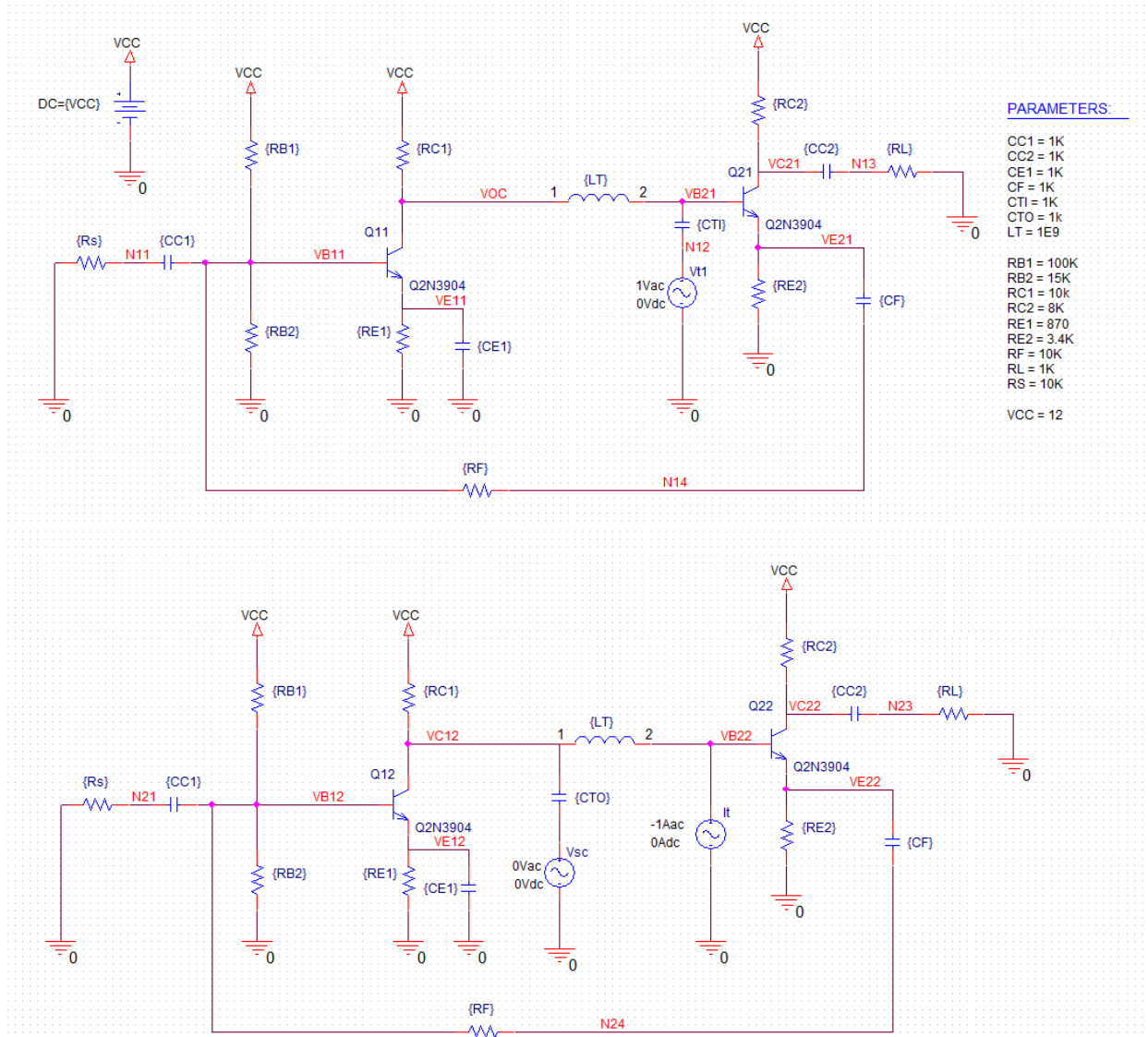**Netlist:**

Copy the netlist given below and paste it into a text file and save it with \*.cir extension.

```
*****Example S 11.1 Method 1 *****
***** Main circuit begins here*****
R_Rb8      0 VB12 {RB2}
R_RF3      N24 VB12 {RF}
R_Rb7      VB12 VCC {RB1}
C_CC7      VC22 N23 {CC2}
```

```

Q_Q22      VC22 VB22 VE22 Q2N3904
L_LT3      VOC VB21 {LT}
C_CC9      VC21 N13 {CC2}
R_RE8      VE22 0 {RE2}
I_It       VB22 0 DC 0Adc AC -1Aac
R_Rb9      VB11 VCC {RB1}
C_Cc8      N21 VB12 {CC1}
L_LT2      VC12 VB22 {LT}
C_Cc10     N11 VB11 {CC1}
C_CE5      0 VE11 {CE1}
C_CTI3     N257744 VC12 {CTO}
Q_Q21      VC21 VB21 VE21 Q2N3904
C_CE4      0 VE12 {CE1}
C_CTI4     N12 VB21 {CTI}
R_RF4      N14 VB11 {RF}
C_CF3      N24 VE22 {CF}
R_RC8      VC12 VCC {RC1}
R_Re7      VE12 0 {RE1}
R_RS4      N11 0 {Rs}
Q_Q11      VOC VB11 VE11 Q2N3904
R_RL3      N23 0 {RL}
R_RE10     VE21 0 {RE2}
R_RC9      VC21 VCC {RC2}
V_VCC      VCC 0 DC={VCC}
R_RS3      N21 0 {Rs}
V_Vt1     N12 0 DC 0Vdc AC 1Vac
R_Rb10     0 VB11 {RB2}
C_CF4      N14 VE21 {CF}
R_RC10     VOC VCC {RC1}
Q_Q12      VC12 VB12 VE12 Q2N3904
R_RL4      N13 0 {RL}
R_RC7      VC22 VCC {RC2}
R_Re9      VE11 0 {RE1}
V_Vsc     N257744 0 DC 0Vdc AC 0Vac
.PARAM    re2=3.4k cto=1k rs=10k cap=1k rb2=15k re1=870 rb1=100k vcc=12 rl=1k
+ rc1=10k rc2=8k cti=1k ccl=1k cf=1k ce1=1k rf=10k cc2=1k lt=1e9
***** Main circuit ends here*****


***** Model for 2N3904 NPN BJT begins here*****
.model Q2N3904 NPN(Is=6.734f Xti=3 Eg=1.11 Vaf=74.03 Bf=416.4 Ne=1.259
+ Ise=6.734f Ikf=66.78m Xtb=1.5 Br=.7371 Nc=2 Isc=0 Ikr=0 Rc=1
+ Cjc=3.638p Mjc=.3085 Vjc=.75 Fc=.5 Cje=4.493p Mje=.2593 Vje=.75
+ Tr=239.5n Tf=301.2p Itf=.4 Vtf=4 Xtf=2 Rb=10)
***** Model for 2N3904 NPN BJT ends here*****

***** Analysis begins here*****
.AC DEC 20 1 1G
.PROBE ; While plotting using the expression (1/(1/ V(VOC)+1/ I(V_Vsc))) for magnitude plot and
(-1/(1/ V(VOC)+1/ I(V_Vsc))) for phase plot
.END
***** Analysis ends here*****

```



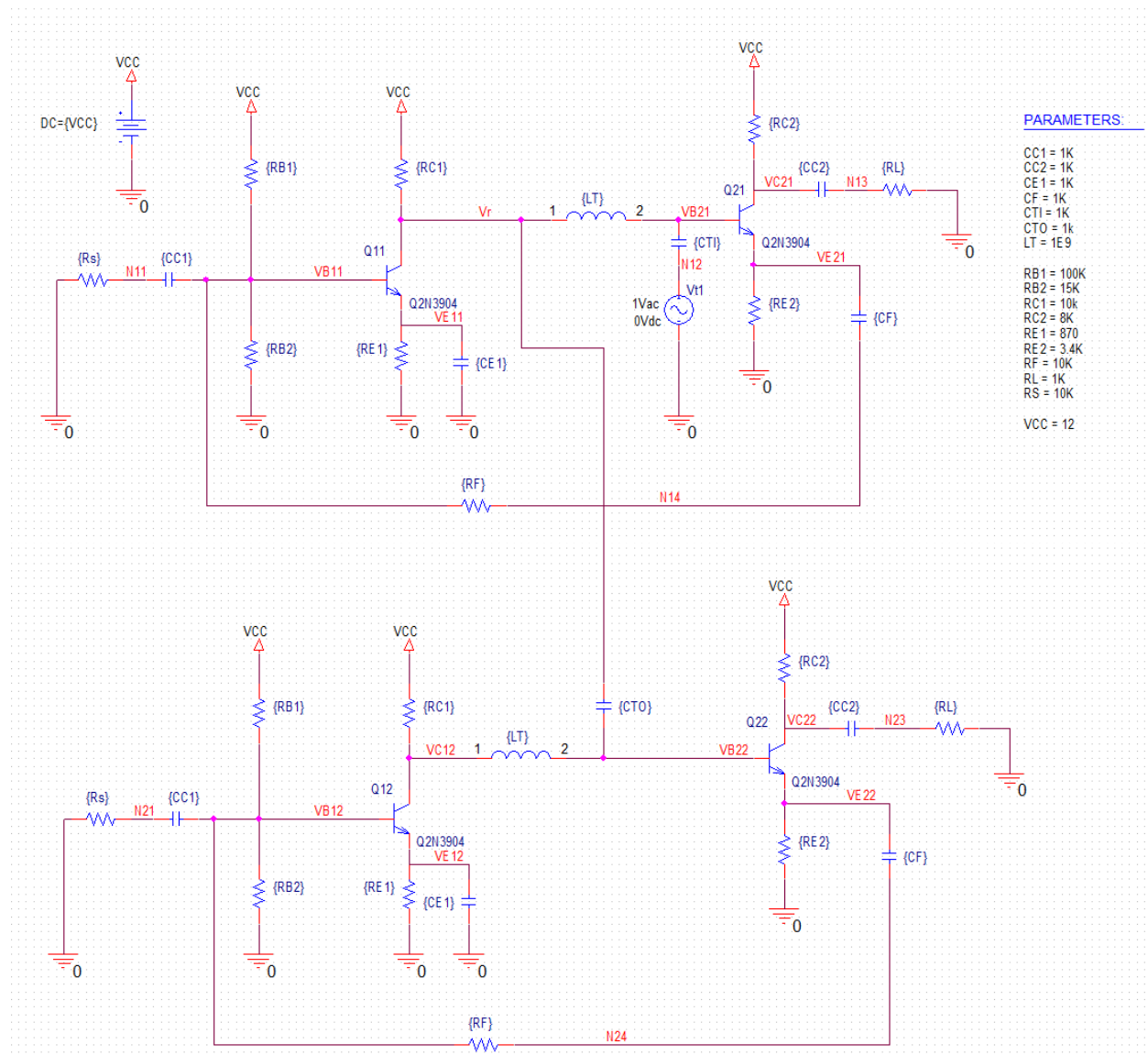The schematic of this example using method 2 is shown below.



### Netlist:

Copy the netlist given below and paste it into a text file and save it with \*.cir extension.

```
*****Example S 11.1 Method 2 *****
***** Main circuit begins here*****
R_RL3      N23 0 {RL}
R_RF3      N24 VB12 {RF}
R_Rb9      VB11 VCC {RB1}
L_LT2      VC12 VB22 {LT}
R_Rb7      VB12 VCC {RB1}
R_RE10     VE21 0 {RE2}
```

```

R_RF4      N14 VB11 {RF}
R_RS4      N11 0 {Rs}
R_Re7      VE12 0 {RE1}
R_RC9      VC21 VCC {RC2}
R_RE8      VE22 0 {RE2}
C_Cc8      N21 VB12 {CC1}
C_Cc10     N11 VB11 {CC1}
C_CC7      VC22 N23 {CC2}
R_RC7      VC22 VCC {RC2}
Q_Q21      VC21 VB21 VE21 Q2N3904
Q_Q22      VC22 VB22 VE22 Q2N3904
C_CF3      N24 VE22 {CF}
C_CE4      0 VE12 {CE1}
R_Re9      VE11 0 {RE1}
R_RC8      VC12 VCC {RC1}
Q_Q12      VC12 VB12 VE12 Q2N3904
R_RC10     VR VCC {RC1}
C_CTI4     N12 VB21 {CTI}
R_Rb10     0 VB11 {RB2}
C_CC9      VC21 N13 {CC2}
C_CF4      N14 VE21 {CF}
V_VCC      VCC 0 DC={VCC}
V_Vt1     N12 0 DC 0Vdc AC 1Vac
R_RS3      N21 0 {Rs}
R_Rb8      0 VB12 {RB2}
R_RL4      N13 0 {RL}
C_CE5      0 VE11 {CE1}
Q_Q11      VR VB11 VE11 Q2N3904
L_LT3      VR VB21 {LT}
C_CTI3     VB22 VR {CTO}
.PARAM cto=1k re2=3.4k rs=10k cap=1k re1=870 rb2=15k rb1=100k vcc=12 rl=1k
+ rc1=10k rc2=8k cti=1k ccl=1k cel=1k cf=1k rf=10k cc2=1k lt=1e9
***** Main circuit ends here*****


***** Model for 2N3904 NPN BJT begins here*****
.model Q2N3904 NPN(Is=6.734f Xti=3 Eg=1.11 Vaf=74.03 Bf=416.4 Ne=1.259
+ Ise=6.734f Ikf=66.78m Xtb=1.5 Br=.7371 Nc=2 Isc=0 Ikr=0 Rc=1
+ Cjc=3.638p Mjc=.3085 Vjc=.75 Fc=.5 Cje=4.493p Mje=.2593 Vje=.75
+ Tr=239.5n Tf=301.2p Itf=.4 Vtf=4 Xtf=2 Rb=10)
***** Model for 2N3904 NPN BJT ends here*****

***** Analysis begins here*****
.AC DEC 20 1 1G
.PROBE
.END
***** Analysis ends here*****

```

**Example S.11.2**

The schematic of this example for finding  $A_v$  is shown below.

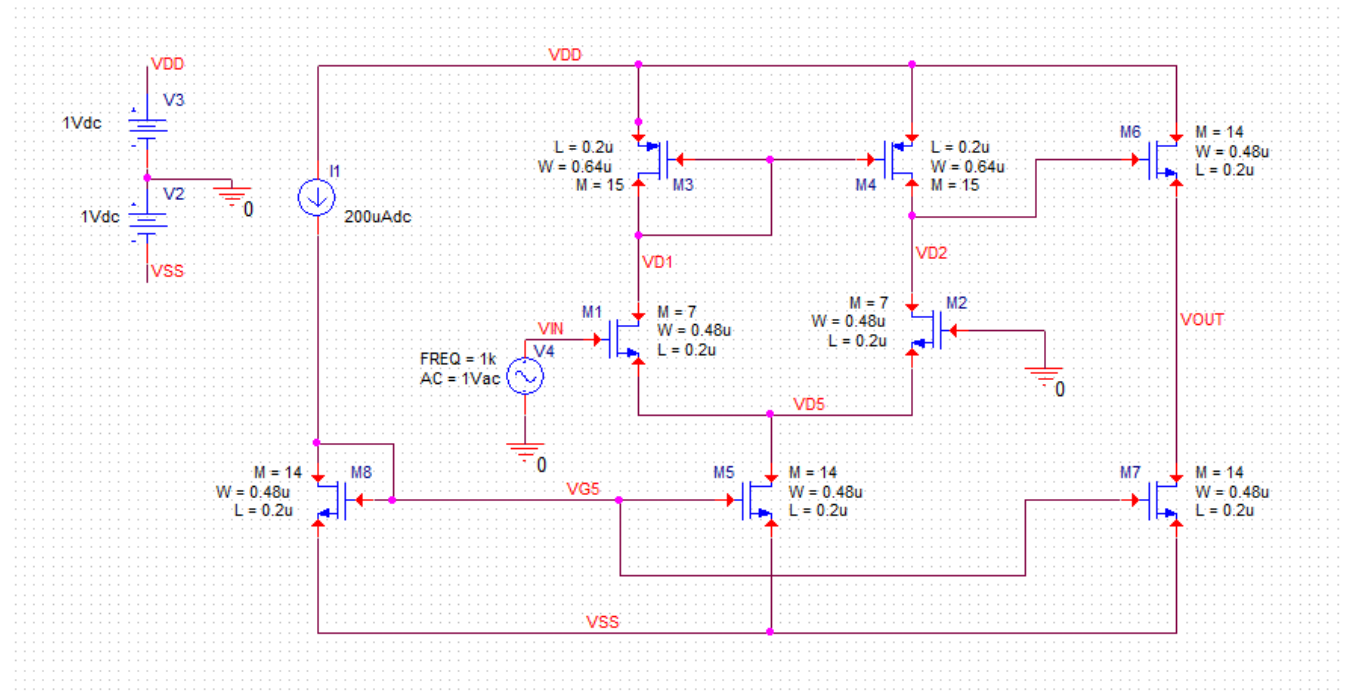**Netlist:**

Copy the netlist given below and paste it into a text file and save it with \*.cir extension.

```
*****Example S 11.2 (Av) *****
***** Main circuit begins here*****
V_V4      VIN 0 AC 1Vac
+SIN 0 1m 1k 0 0 0
M_M1      VD1 VIN VD5 0 NMOS4
+ L=0.2u
+ W=0.48u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M=7
M_M3      VD1 VD1 VDD VDD PMOS4
+ L=0.2u
+ W=0.64u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25e-6
+ PS=5.25E-6
+ M=15
I_I1      VDD VG5 DC 200uAdc
M_M5      VD5 VG5 VSS 0 NMOS4
+ L=0.2u
+ W=0.48u
```

```

+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M=14
M_M8      VG5 VG5 VSS 0 NMOS4
+ L=0.2u
+ W=0.48u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M=14
V_V2      0 VSS 1Vdc
M_M4      VD2 VD1 VDD VDD PMOS4
+ L=0.2u
+ W=0.64u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M=15
M_M7      VOUT VG5 VSS 0 NMOS4
+ L=0.2u
+ W=0.48u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M=14
M_M2      VD2 0 VD5 0 NMOS4
+ L=0.2u
+ W=0.48u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M=7
V_V3      VDD 0 1Vdc
M_M6      VDD VD2 VOUT 0 NMOS4
+ L=0.2u
+ W=0.48u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M=14
***** Main circuit ends here*****

*****PMOS and NMOS models begin here*****
.model NMOS4 NMOS(LEVEL= 1 VTO=0.5 GAMMA= 0.3 PHI=0.84
+ LAMBDA= 0.08
+ RS= 0.0
+ RD= 0.0
+ CBD= 0.0
+ CBS= 0.0
+ IS= 1.0e-14
+ PB= 0.9
+ CGSO= 0.3665e-9
+ CGDO= 0.3665e-9
+ CGBO= 0.38e-9
+ RSH= 0
+ CJ= 1.6e-3
+ MJ= 0.5

```

```


+ CJSW= 2.0405e-10
+ MJSW= 0.200379
+ JS= 8.38e-6
+ TOX= 4.08e-09
+ NSS= 0.0
+ TPG= 1.0
+ LD= 10e-9
+ U0 = 291
+ KF= 0.0
+ AF= 1.0
+ FC= 0.5
+ TNOM= 27
+ )

.model PMOS4 PMOS (LEVEL= 1 VTO=-0.5 KP=86.1e-6 GAMMA= 0.3
+ PHI= 0.8
+ LAMBDA= 0.11
+ RS= 0.0
+ RD= 0.0
+ CBD= 0.0
+ CBS= 0.0
+ IS= 1.0e-14
+ PB= 0.9
+ CGSO= 0.3426e-9
+ CGDO= 0.3426e-9
+ CGBO= 0.35e-9
+ RSH= 0
+ CJ= 1.01574e-03
+ MJ= 0.4490538
+ CJSW= 2.0405e-10
+ MJSW= 0.2931001
+ JS= 4e-7
+ NSS= 0.0
+ TPG= 1.0
+ LD= 10e-9
+ KF= 0.0
+ AF= 1.0
+ FC= 0.5
+ TNOM= 27
+ )
*****PMOS and NMOS models end here*****

***** Analysis begins here*****
.OP
.AC DEC 20 1MEG 5G
.PROBE
.END
***** Analysis ends here*****

```

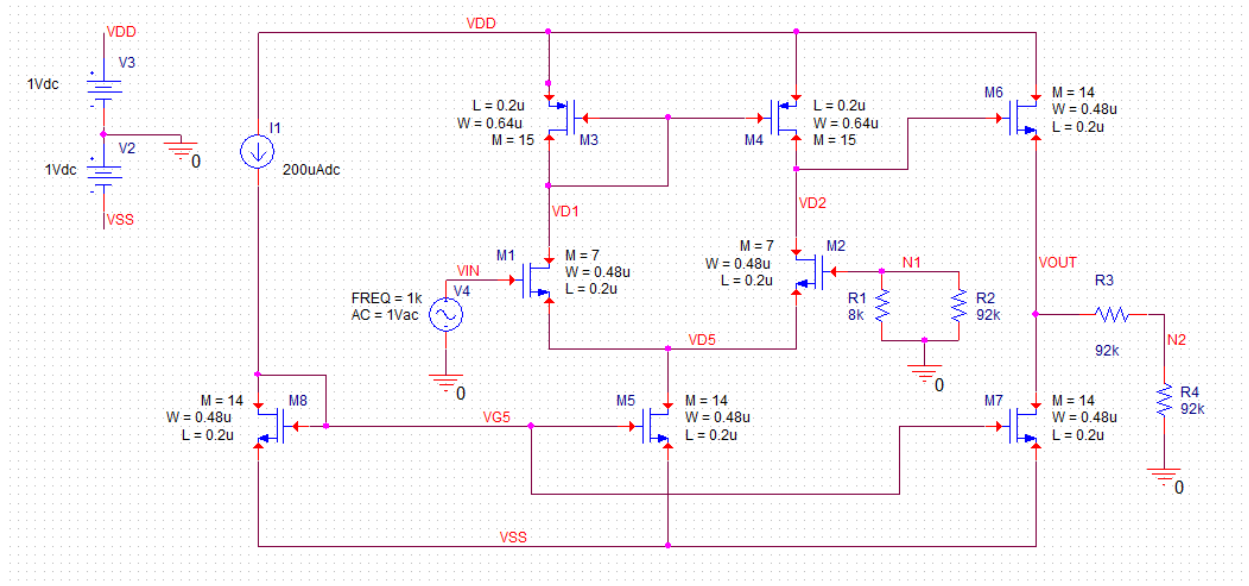The schematic of this example for finding A is shown below.



**Netlist:**

Copy the netlist given below and paste it into a text file and save it with \*.cir extension.

```

*****Example S 11.2 (A) *****
***** Main circuit begins here*****
M_M6          VDD VD2 VOUT 0 NMOS4
+ L=0.2u
+ W=0.48u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M=14
M_M5          VD5 VG5 VSS 0 NMOS4
+ L=0.2u
+ W=0.48u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M=14
I_I1          VDD VG5 DC 200uAdc
M_M3          VD1 VD1 VDD VDD PMOS4
+ L=0.2u
+ W=0.64u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25e-6
+ PS=5.25E-6
+ M=15
V_V2          0 VSS 1Vdc
V_V4          VIN 0 AC 1Vac
+SIN 0 1m 1k 0 0 0
M_M1          VD1 VIN VD5 0 NMOS4
+ L=0.2u
+ W=0.48u
+ AD=1.72E-12
+ AS=1.72E-12

```

```

+ PD=5.25E-6
+ PS=5.25E-6
+ M=7
V_V3          VDD 0 1Vdc
M_M8          VG5 VG5 VSS 0 NMOS4
+ L=0.2u
+ W=0.48u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M=14
M_M2          VD2 N1 VD5 0 NMOS4
+ L=0.2u
+ W=0.48u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M=7
M_M4          VD2 VD1 VDD VDD PMOS4
+ L=0.2u
+ W=0.64u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M=15
M_M7          VOUT VG5 VSS 0 NMOS4
+ L=0.2u
+ W=0.48u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M=14
R_R1          0 N1 8k TC=0,0
R_R2          0 N1 92k TC=0,0
R_R3          N2 VOUT 92k TC=0,0
R_R4          0 N2 92k TC=0,0
***** Main circuit ends here*****
*****PMOS and NMOS models begin here*****
.model NMOS4  NMOS(LEVEL= 1 VTO=0.5 GAMMA= 0.3 PHI=0.84
+ LAMBDA= 0.08
+ RS= 0.0
+ RD= 0.0
+ CBD= 0.0
+ CBS= 0.0
+ IS= 1.0e-14
+ PB= 0.9
+ CGSO= 0.3665e-9
+ CGDO= 0.3665e-9
+ CGBO= 0.38e-9
+ RSH= 0
+ CJ= 1.6e-3
+ MJ= 0.5
+ CJSW= 2.0405e-10
+ MJSW= 0.200379
+ JS= 8.38e-6
+ TOX= 4.08e-09
+ NSS= 0.0
+ TPG= 1.0
+ LD= 10e-9
+ U0 = 291


```

```
+ KF= 0.0
+ AF= 1.0
+ FC= 0.5
+ TNOM= 27
+ )

.model PMOS4 PMOS (LEVEL= 1 VTO=-0.5 KP=86.1e-6 GAMMA= 0.3
+ PHI= 0.8
+ LAMBDA= 0.11
+ RS= 0.0
+ RD= 0.0
+ CBD= 0.0
+ CBS= 0.0
+ IS= 1.0e-14
+ PB= 0.9
+ CGSO= 0.3426e-9
+ CGDO= 0.3426e-9
+ CGBO= 0.35e-9
+ RSH= 0
+ CJ= 1.01574e-03
+ MJ= 0.4490538
+ CJSW= 2.0405e-10
+ MJSW= 0.2931001
+ JS= 4e-7
+ NSS= 0.0
+ TPG= 1.0
+ LD= 10e-9
+ KF= 0.0
+ AF= 1.0
+ FC= 0.5
+ TNOM= 27
+ )
*****PMOS and NMOS models end here*****
***** Analysis begins here*****
.OP
.AC DEC 20 1MEG 5G
.PROBE
.END
***** Analysis ends here*****
```



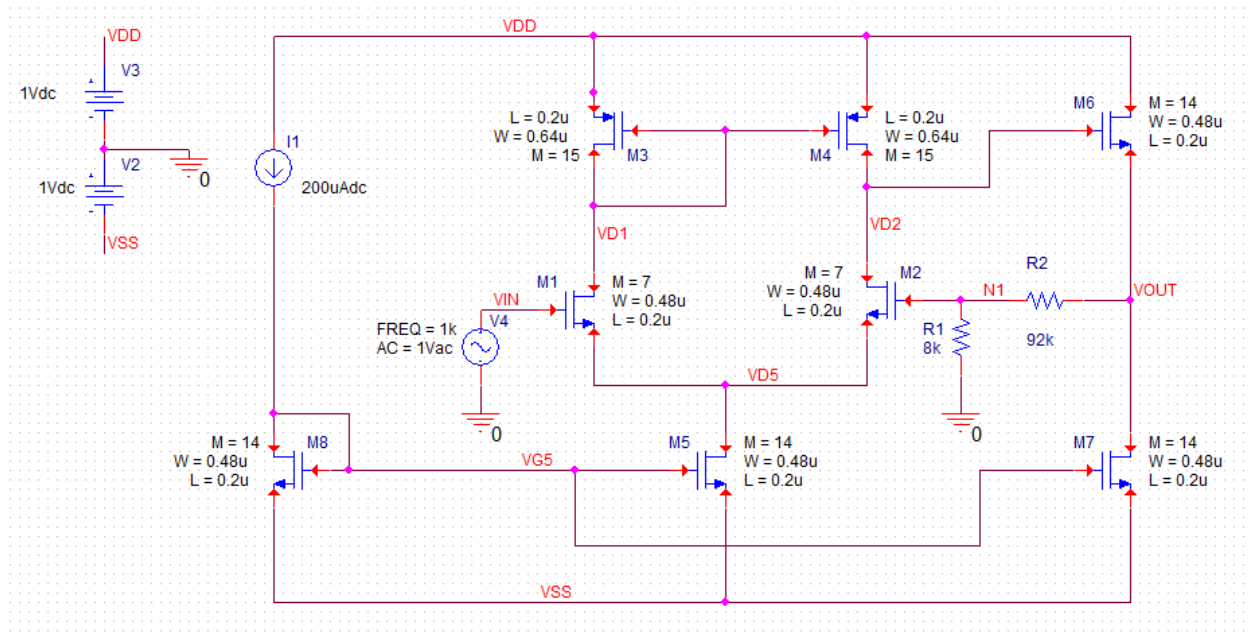The schematic for finding  $A_f$  in this example is shown below.



### Netlist:

Copy the netlist given below and paste it into a text file and save it with \*.cir extension.

```
*****Example S 11.2 (Af) *****
***** Main circuit begins here*****
R_R1      0 N1  8k TC=0,0
R_R2      VOUT N1  92k TC=0,0
M_M4      VD2 VD1 VDD VDD PMOS4
+ L=0.2u
+ W=0.64u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M=15
M_M7      VOUT VG5 VSS 0 NMOS4
+ L=0.2u
+ W=0.48u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M=14
V_V3      VDD 0 1Vdc
V_V4      VIN 0 AC 1Vac
+SIN 0 1m 1k 0 0 0
M_M6      VDD VD2 VOUT 0 NMOS4
+ L=0.2u
+ W=0.48u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
```

```

+ M=14
V_V2          0 VSS 1Vdc
M_M1          VD1 VIN VD5 0 NMOS4
+ L=0.2u
+ W=0.48u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M=7
M_M8          VG5 VG5 VSS 0 NMOS4
+ L=0.2u
+ W=0.48u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M=14
M_M2          VD2 N1 VD5 0 NMOS4
+ L=0.2u
+ W=0.48u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M=7
I_I1          VDD VG5 DC 200uAdc
M_M3          VD1 VD1 VDD VDD PMOS4
+ L=0.2u
+ W=0.64u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M=15
M_M5          VD5 VG5 VSS 0 NMOS4
+ L=0.2u
+ W=0.48u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M=14
***** Main circuit ends here*****

*****PMOS and NMOS models begin here*****
.model NMOS4  NMOS(LEVEL= 1 VTO=0.5 GAMMA= 0.3 PHI=0.84
+ LAMBDA= 0.08
+ RS= 0.0
+ RD= 0.0
+ CBD= 0.0
+ CBS= 0.0
+ IS= 1.0e-14
+ PB= 0.9
+ CGSO= 0.3665e-9
+ CGDO= 0.3665e-9
+ CGBO= 0.38e-9
+ RSH= 0
+ CJ= 1.6e-3
+ MJ= 0.5
+ CJSW= 2.0405e-10
+ MJSW= 0.200379
+ JS= 8.38e-6
+ TOX= 4.08e-09

```

```

+ NSS= 0.0
+ TPG= 1.0
+ LD= 10e-9
+ U0 = 291
+ KF= 0.0
+ AF= 1.0
+ FC= 0.5
+ TNOM= 27
+ )


.model PMOS4 PMOS(LEVEL= 1 VTO=-0.5 KP=86.1e-6 GAMMA= 0.3
+ PHI= 0.8
+ LAMBDA= 0.11
+ RS= 0.0
+ RD= 0.0
+ CBD= 0.0
+ CBS= 0.0
+ IS= 1.0e-14
+ PB= 0.9
+ CGSO= 0.3426e-9
+ CGDO= 0.3426e-9
+ CGBO= 0.35e-9
+ RSH= 0
+ CJ= 1.01574e-03
+ MJ= 0.4490538
+ CJSW= 2.0405e-10
+ MJSW= 0.2931001
+ JS= 4e-7
+ NSS= 0.0
+ TPG= 1.0
+ LD= 10e-9
+ KF= 0.0
+ AF= 1.0
+ FC= 0.5
+ TNOM= 27
+ )
*****PMOS and NMOS models end here*****

***** Analysis begins here*****
.OP
.AC DEC 20 1MEG 5G
.PROBE
.END
***** Analysis ends here*****

```

**Example S.12.1**

The schematic of this example is shown below.

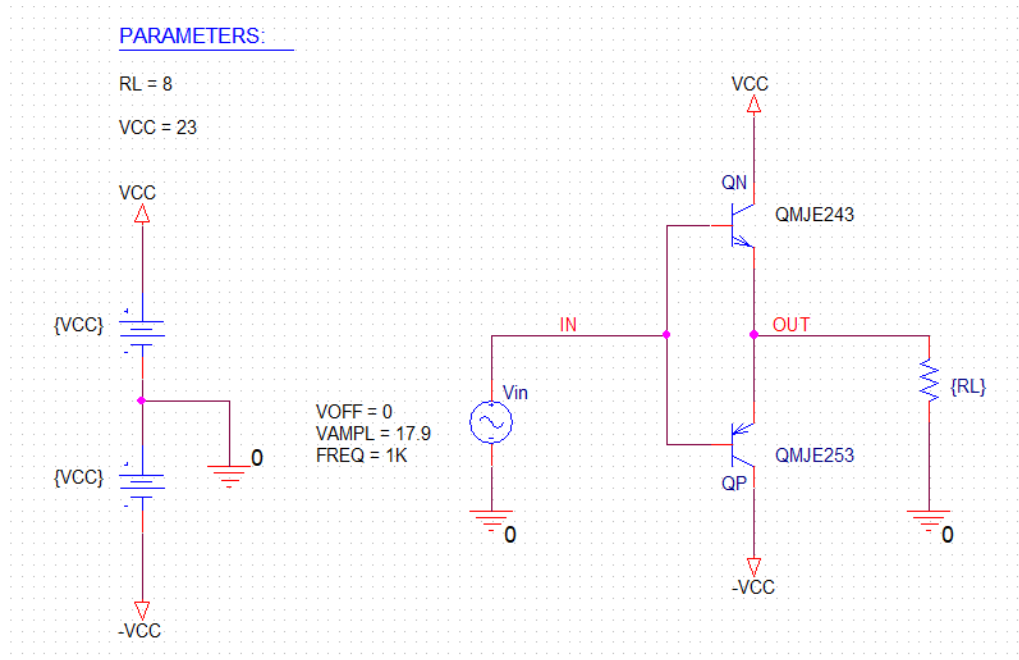**Netlist:**

Copy the netlist given below and paste it into a text file and save it with \*.cir extension.

```
*****Example S 12.1 *****
***** Main circuit begins here*****
Q_QN      VCC IN OUT QMJE243
V_-VCC    0 -VCC {VCC}
R_RL      OUT 0 {RL}
V_VCC     VCC 0 {VCC}
Q_QP      -VCC IN OUT QMJE253
V_Vin     IN 0
+SIN 0 17.9 1K 0 0 0
.PARAM   vcc=23 rl=8
***** Main circuit ends here*****


*****Model for MJE243 Power NPN BJT (from ON Semiconductor) begins here*****
.model   QMJE243 NPN (
+       IS=1.27357e-12 BF=188.792 NF=1.05658 VAF=13.5417
+       IKF=0.442678 ISE=1e-16 NE=4 BR=1.73115
+       NR=1.04113 VAR=135.417 IKR=1.00889 ISC=1e-16
+       NC=2.93725 RB=193.999 IRB=5.29235e-05 RBM=0.000841015
+       RE=9.44257e-05 RC=0.216999 XTB=1.16682 XTI=0.80411
+       EG=1.05 CJE=2.19516e-10 VJE=0.99 MJE=0.39332
+       TF=1.51916e-09 XTF=1.21445 VTF=11.3491 ITF=0.0098534
+       CJC=7.43909e-11 VJC=0.4 MJC=0.287382 XCJC=0.799998
+       FC=0.577401 CJS=0 VJS=0.75 MJS=0.5
+       TR=7.76174e-07 PTF=0 KF=0 AF=1)
*****Model for MJE243 Power NPN BJT (from ON Semiconductor) ends here*****
```

```
***** Model for MJE253 Power PNP BJT (from ON Semiconductor) begins here*****
.model QMJE253 PNP(
+   IS=2.52937e-13 BF=54.36 NF=1.01478 VAF=4.91894
+   IKF=0.84154 ISE=6.32316e-13 NE=3.6001 BR=3.71504
+   NR=1.15303 VAR=49.1894 IKR=4.42705 ISC=6.32316e-13
+   NC=2.93783 RB=417.673 IRB=7.10249e-06 RBM=0.000992345
+   RE=6.68257e-05 RC=0.262081 XTB=1.32735 XTI=0.01
+   EG=1.05 CJE=1.57797e-10 VJE=0.99 MJE=0.339209
+   TF=2.58603e-09 XTF=1.5 VTF=0.999999 ITF=1
+   CJC=6.54856e-11 VJC=0.0328604 MJC=0.208693 XCJC=0.8
+   FC=0.532891 CJS=0 VJS=0.75 MJS=0.5
+   TR=7.83777e-07 PTF=0 KF=0 AF=1)
***** Model for MJE253 Power PNP BJT (from ON Semiconductor) ends here*****

***** Analysis begins here*****
.TRAN 0.01mS 3mS
*.DC [LIN] V_Vin -10 10 1m
.PROBE
.END
***** Analysis ends here*****
```

**Example S.13.1**

The schematic of this example for AC analysis is shown below.

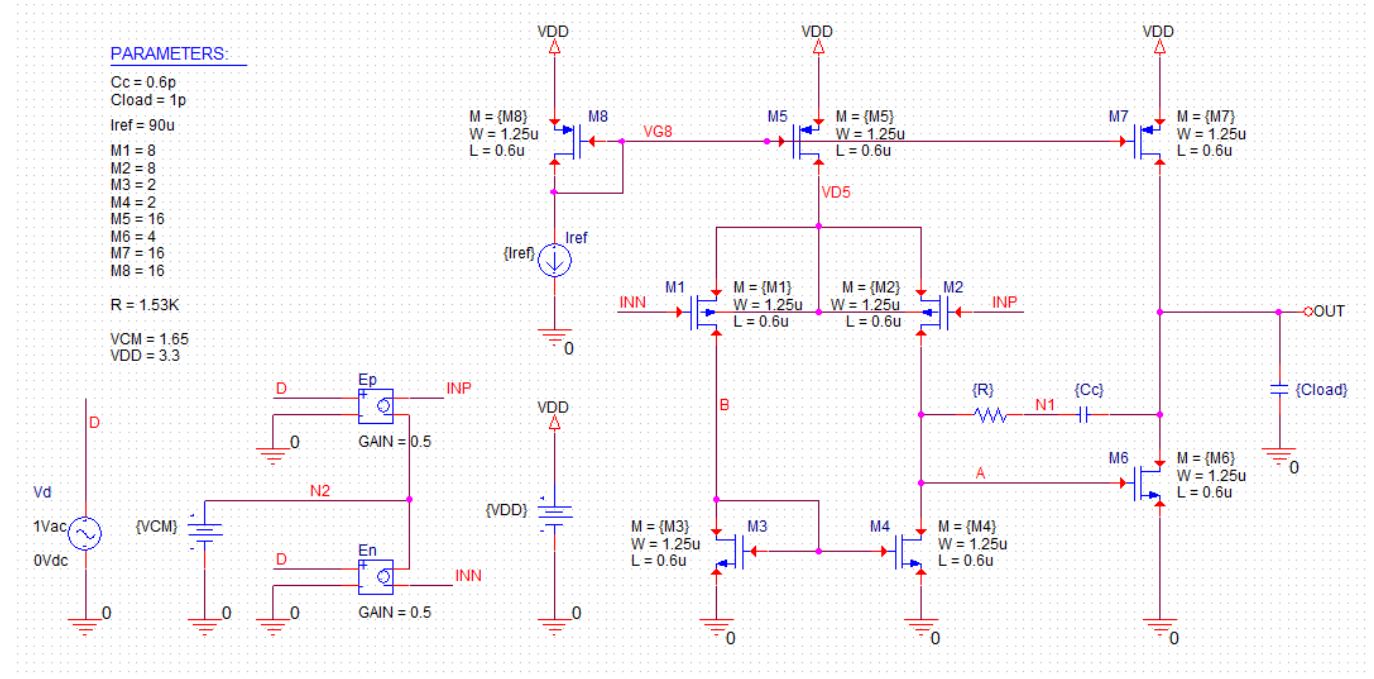**Netlist:**

Copy the netlist given below and paste it into a text file and save it with \*.cir extension.

```
*****Example S 13.1 AC *****
***** Main circuit begins here*****
V_VCM      N2 0 {VCM}
V_VCC      VDD 0 {VDD}
M_M8       VG8 VG8 VDD VDD PMOS0P5
+ L=0.6u
+ W=1.25u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25e-6
+ PS=5.25E-6
+ M={M8}
C_CL       0 OUT {Cload}
M_M7       OUT VG8 VDD VDD PMOS0P5
+ L=0.6u
+ W=1.25u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25e-6
+ PS=5.25E-6
+ M={M7}
E_En       N2 INN D 0 0.5
V_Vd       D 0 DC 0Vdc AC 1Vac
I_Iref     VG8 0 DC {Iref}
M_M5       VD5 VG8 VDD VDD PMOS0P5
```

```

+ L=0.6u
+ W=1.25u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25e-6
+ PS=5.25E-6
+ M={M5}
C_Cc      N1 OUT {Cc}
M_M2      A INP VD5 VD5 PMOS0P5
+ L=0.6u
+ W=1.25u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25e-6
+ PS=5.25E-6
+ M={M2}
M_M4      A B 0 0 NMOS0P5
+ L=0.6u
+ W=1.25u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M={M4}
M_M1      B INN VD5 VD5 PMOS0P5
+ L=0.6u
+ W=1.25u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25e-6
+ PS=5.25E-6
+ M={M1}
M_M3      B B 0 0 NMOS0P5
+ L=0.6u
+ W=1.25u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M={M3}
M_M6      OUT A 0 0 NMOS0P5
+ L=0.6u
+ W=1.25u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M={M6}
E_Ep      INP N2 D 0 0.5
R_R       A N1 {R}
.PARAM   m8=16 vcm=1.65 iref=90u cc=0.6p m6=4 m7=16 m4=2 vdd=3.3 m5=16 m2=8
+   cload=1p m3=2 m1=8 r=1.53k
***** Main circuit ends here*****

*****Model for NMOS in 0.5um CMOS Technology begins here*****
*
      (created by Anas Hamoui & Olivier Trescases)
.model NMOS0P5 NMOS(Level=1 VTO=0.7 GAMMA=0.5 PHI=0.8
+       LD=0.08E-06 WD=0 UO=460 LAMBDA=0.1 TOX=9.5E-9 PB=0.9 CJ=0.57E-3
+       CJSW=120E-12 MJ=0.5 MJSW=0.4 CGDO=0.4E-9 JS=10E-9 CGBO=0.38E-9
+       CGSO=0.4E-9)
*****Model for NMOS in 0.5um CMOS Technology ends here*****


*****Model for PMOS in 0.5um CMOS Technology begins here*****
*
      (created by Anas Hamoui & Olivier Trescases)

```

```
.model PMOS0P5 PMOS(Level=1 VTO=-0.8 GAMMA=0.45 PHI=0.8
+
+ LD=0.09E-06 WD=0 UO=115 LAMBDA=0.2 TOX=9.5E-9 PB=0.9 CJ=0.93E-3
+
+ CJSW=170E-12 MJ=0.5 MJSW=0.35 CGDO=0.35E-9 JS=5E-9 CGBO=0.38E-9
+
+ CGSO=0.35E-9)
*****Model for PMOS in 0.5um CMOS Technology ends here*****

***** Analysis begins here*****
.OP
.AC DEC 20 1 1G
.PROBE
.END
***** Analysis ends here*****
```

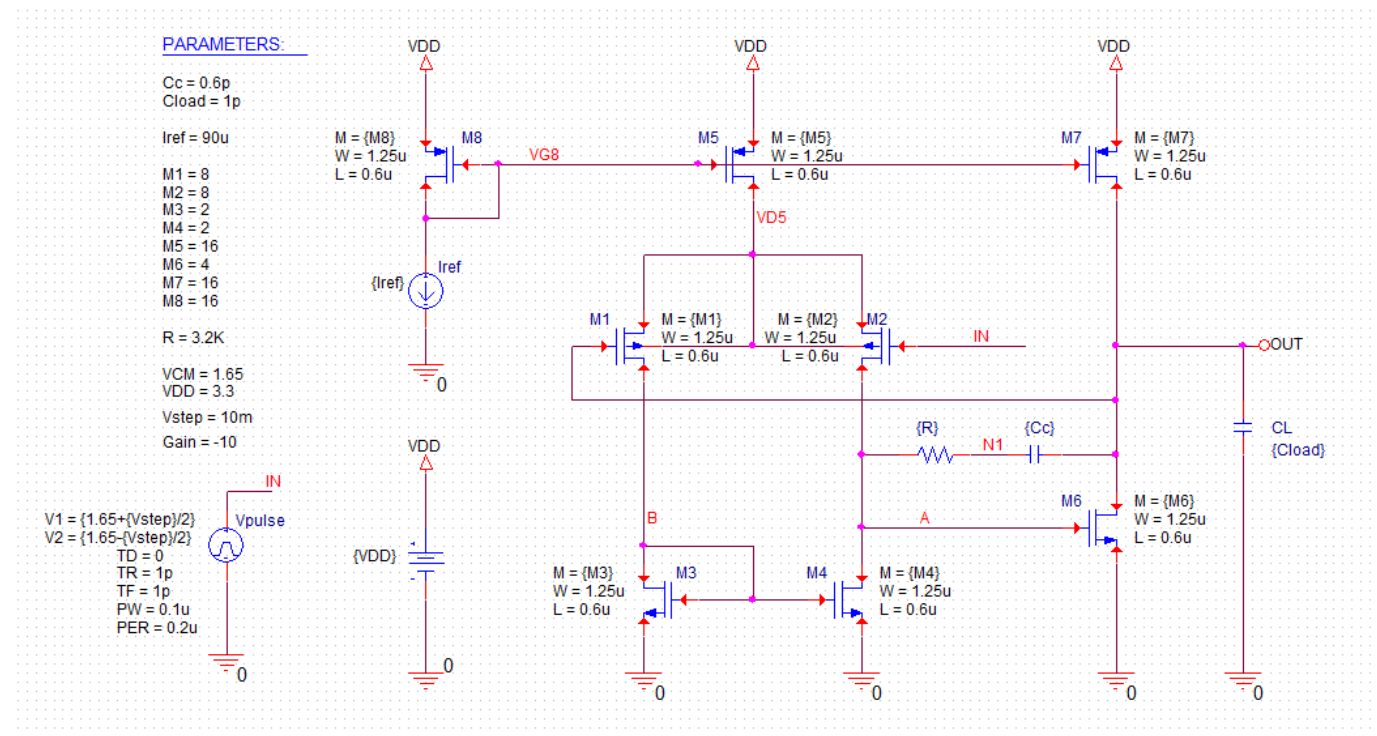The schematic of this example for transient analysis is shown below.



**Netlist:**

Copy the netlist given below and paste it into a text file and save it with \*.cir extension.

```
*****Example PS 13.1 TRANS *****
***** Main circuit begins here*****
C_CL      0 OUT {Cload}
R_R       A N1 {R}
V_VCC    VDD 0 {VDD}
M_M8     VG8 VG8 VDD VDD PMOS0P5
+ L=0.6u
+ W=1.25u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25e-6
```



```

+ PS=5.25E-6
+ M={M8}
V_Vpulse          IN 0 DC 1.65
+PULSE {1.65+{Vstep}/2} {1.65-{Vstep}/2} 0 1p 1p 0.1u 0.2u
M_M6              OUT A 0 0 NMOS0P5
+ L=0.6u
+ W=1.25u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M={M6}
I_Iref            VG8 0 DC {Iref}
M_M2              A IN VD5 VD5 PMOS0P5
+ L=0.6u
+ W=1.25u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25e-6
+ PS=5.25E-6
+ M={M2}
M_M5              VD5 VG8 VDD VDD PMOS0P5
+ L=0.6u
+ W=1.25u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25e-6
+ PS=5.25E-6
+ M={M5}
M_M1              B OUT VD5 VD5 PMOS0P5
+ L=0.6u
+ W=1.25u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25e-6
+ PS=5.25E-6
+ M={M1}
M_M4              A B 0 0 NMOS0P5
+ L=0.6u
+ W=1.25u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M={M4}
C_Cc              N1 OUT {Cc}
M_M3              B B 0 0 NMOS0P5
+ L=0.6u
+ W=1.25u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M={M3}
M_M7              OUT VG8 VDD VDD PMOS0P5
+ L=0.6u
+ W=1.25u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25e-6
+ PS=5.25E-6
+ M={M7}
.PARAM m8=16 vcm=1.65 iref=90u cc=0.6p vstep=10m m6=4 m7=16 m4=2 vdd=3.3 m5=16
+ m2=8 cload=1p m3=2 m1=8 gain=-10 r=3.2k

```

```
***** Main circuit ends here*****


*****Model for NMOS in 0.5um CMOS Technology begins here*****
*
*      (created by Anas Hamoui & Olivier Trescases)
.model NMOS0P5 NMOS(Level=1 VTO=0.7 GAMMA=0.5 PHI=0.8
+
+      LD=0.08E-06 WD=0 UO=460 LAMBDA=0.1 TOX=9.5E-9 PB=0.9 CJ=0.57E-3
+      CJSW=120E-12 MJ=0.5 MJSW=0.4 CGDO=0.4E-9 JS=10E-9 CGBO=0.38E-9
+      CGSO=0.4E-9)
*****Model for NMOS in 0.5um CMOS Technology ends here*****

*****Model for PMOS in 0.5um CMOS Technology begins here*****
*
*      (created by Anas Hamoui & Olivier Trescases)
.model PMOS0P5 PMOS(Level=1 VTO=-0.8 GAMMA=0.45 PHI=0.8
+
+      LD=0.09E-06 WD=0 UO=115 LAMBDA=0.2 TOX=9.5E-9 PB=0.9 CJ=0.93E-3
+      CJSW=170E-12 MJ=0.5 MJSW=0.35 CGDO=0.35E-9 JS=5E-9 CGBO=0.38E-9
+      CGSO=0.35E-9)
*****Model for PMOS in 0.5um CMOS Technology ends here*****


***** Analysis begins here*****
.TRAN 0.01nS 400nS
.PROBE
.END
***** Analysis ends here*****
```
 
### Example S.14.1

The schematic of the op amp macro model for this example is shown below.



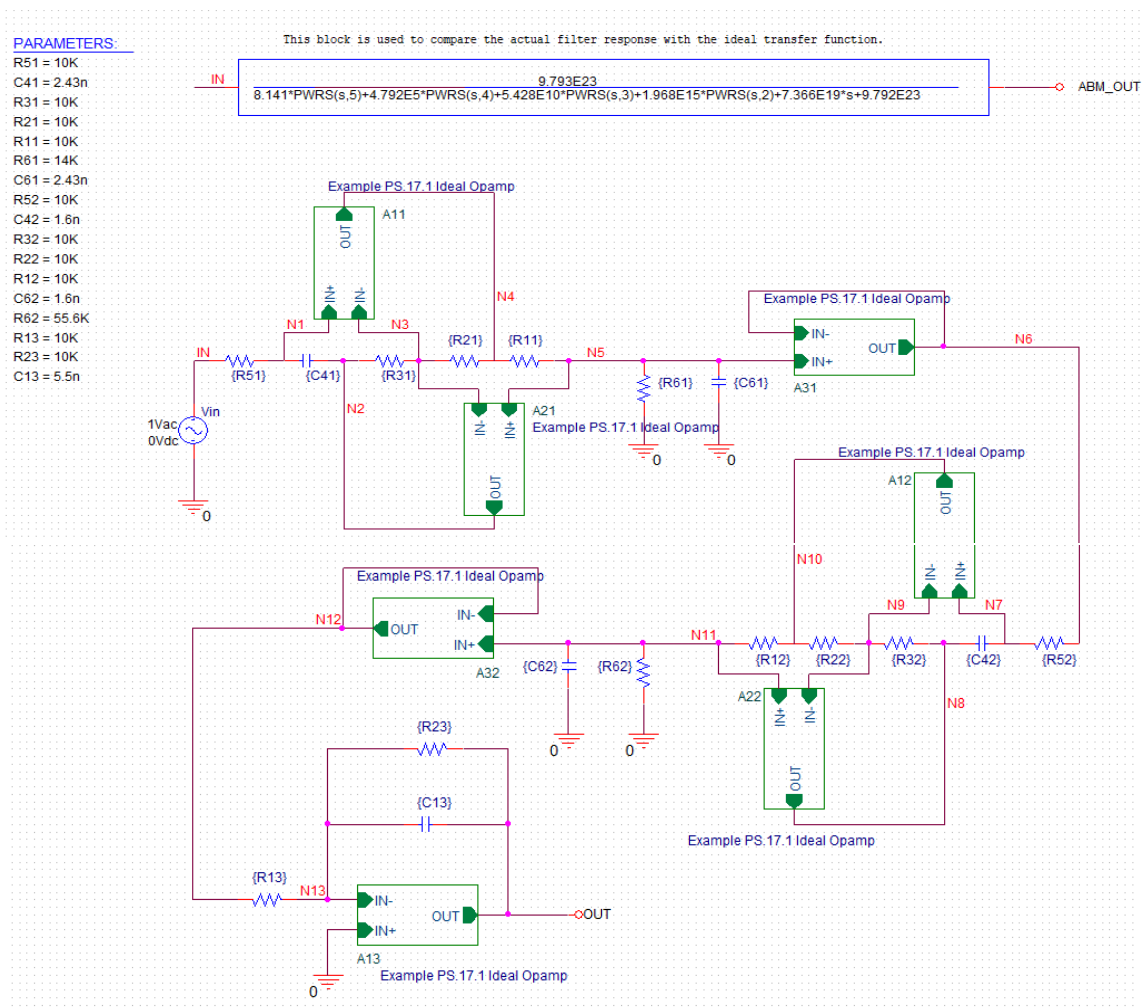The schematic of the main circuit for this example is shown below.



**Netlist:**

Copy the netlist given below and paste it into a text file and save it with \*.cir extension.

```

*****Example S 14.1 *****
***** Main circuit begins here*****
R_R8      N8 N9  {R32}
C_C5      OUT N13 {C13}
R_R3      N3 N4  {R21}
V_Vin     IN 0 DC 0Vdc AC 1Vac
R_R11     OUT N13 {R23}
R_R5      0 N5  {R61}
R_R7      N9 N10 {R22}
R_R4      N4 N5  {R11}
R_R6      N10 N11 {R12}
C_C1      N1 N2  {C41}
C_C3      N7 N8  {C42}
E_LAPLACE1      ABM_OUT 0 LAPLACE {V(IN)}
+
{ (9.793E23) / (8.141*PWRS(s,5)+4.792E5*PWRS(s,4)+5.428E10*PWRS(s,3)+1.968E15*PWRS(s,2)+7.366E19*s+9.792E23) }
R_R1      IN N1  {R51}
C_C4      0 N11  {C62}
R_R9      N6 N7  {R52}
R_R2      N2 N3  {R31}
R_R10     0 N11  {R62}
R_R12     N13 N12 {R13}
C_C2      0 N5  {C61}
X_A11     N3 N1 N4 OPAMP_MACRO
X_A31     N6 N5 N6 OPAMP_MACRO
X_A21     N3 N5 N2 OPAMP_MACRO
X_A12     N9 N7 N10 OPAMP_MACRO
X_A32     N12 N11 N12 OPAMP_MACRO
X_A22     N9 N11 N8 OPAMP_MACRO
X_A13     N13 0 OUT OPAMP_MACRO

.PARAM  c41=2.43n c42=1.6n r62=55.6k r23=10k r61=14k r22=10k r21=10k r31=10k
+ r52=10k r32=10k c62=1.6n r51=10k r12=10k c13=5.5n c61=2.43n r13=10k r11=10k
***** Main circuit ends here *****


***** Opamp macro model begins here *****
.SUBCKT OPAMP_MACRO      IN- IN+ OUT
E_E1      OUT 0 IN+ IN- 10E6
.ENDS
***** Opamp macro model ends here *****

***** Analysis begins here*****
.AC DEC 100 0.1 20K
.PROBE
.END
***** Analysis ends here*****


```
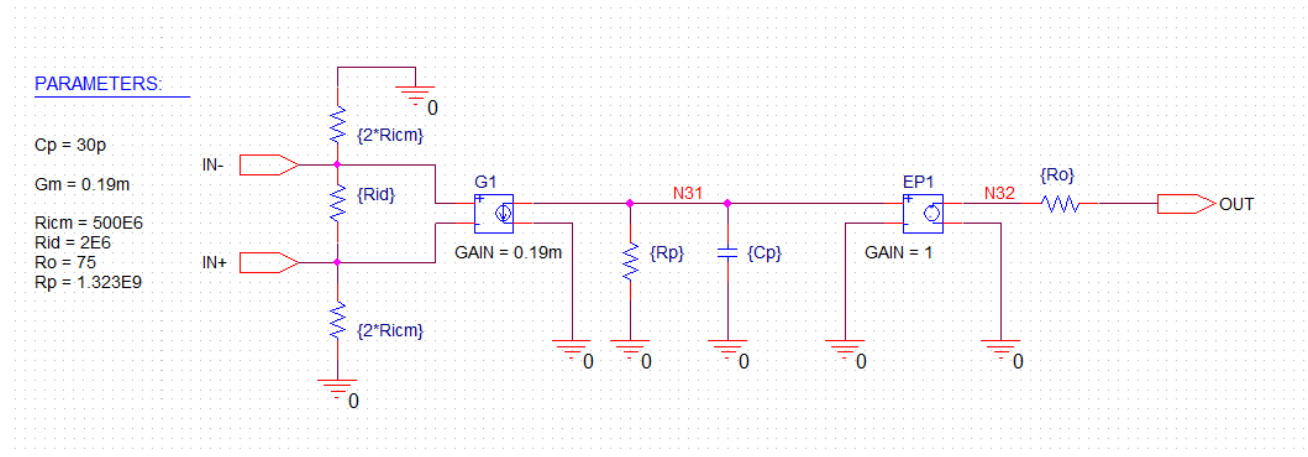
### Example S.14.2

The schematic of the 741 op amp macro model for this example is shown below.



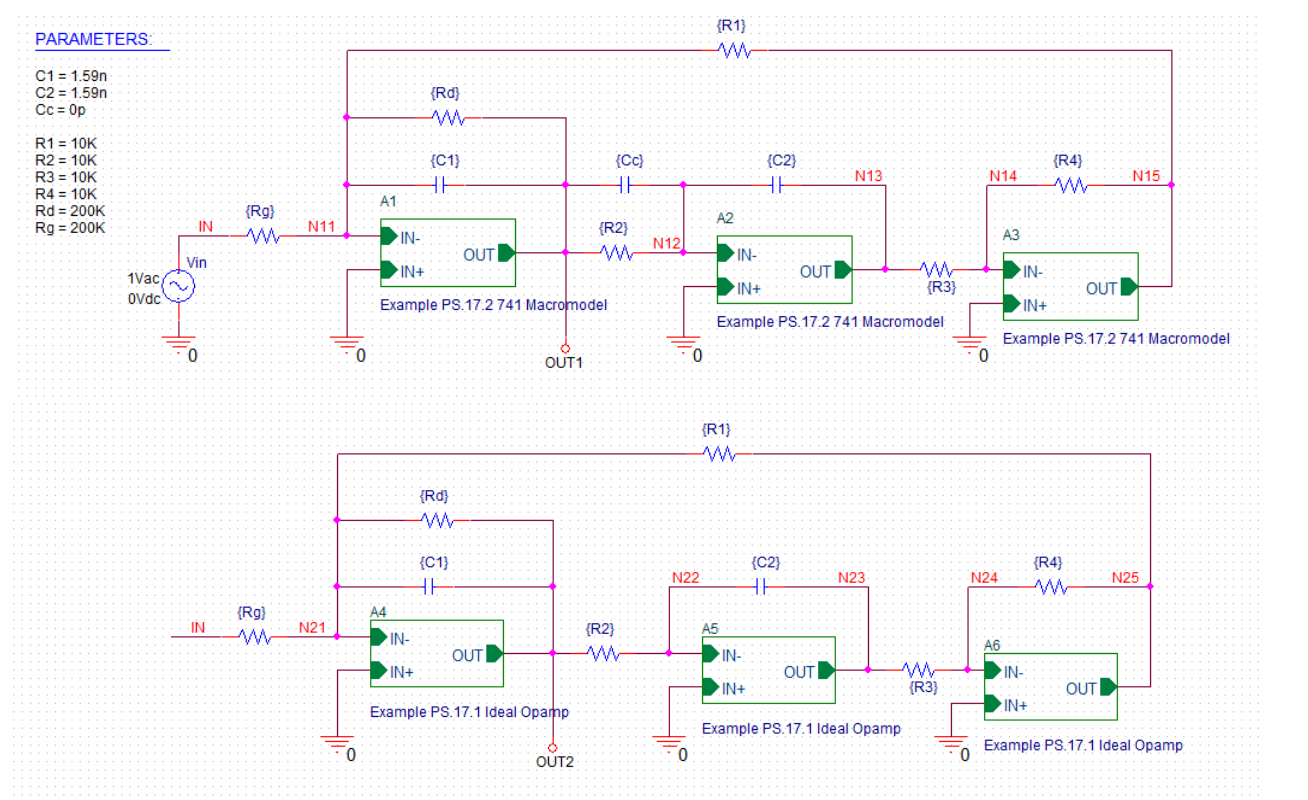The schematic of the main circuit for this example is shown below.



**Netlist:**

Copy the netlist given below and paste it into a text file and save it with \*.cir extension.

```

*****Example S 14.2 *****
***** Main circuit begins here*****
R_R4      N14 N15  {R4}
R_R8      OUT2 N22  {R2}
V_Vin     IN 0 DC 0Vdc AC 1Vac
R_R3      N13 N14  {R3}
C_C5      OUT1 N12  {Cc}
R_R12     IN  N21  {Rg}
C_C3      N21 OUT2  {C1}
C_C2      N12 N13  {C2}
R_R9      N23 N24  {R3}
R_R6      IN  N11  {Rg}
R_R2      OUT1 N12  {R2}
R_R5      N11 N15  {R1}
R_R7      N21 OUT2  {Rd}
R_R1      N11 OUT1  {Rd}
C_C1      N11 OUT1  {C1}
R_R11     N21 N25  {R1}
R_R10     N24 N25  {R4}
C_C4      N22 N23  {C2}
X_A1      0 N11 OUT1 741_OPAMP_MACRO
X_A2      0 N12 N13 741_OPAMP_MACRO
X_A3      0 N14 N15 741_OPAMP_MACRO
X_A4      0 N21 OUT2 IDEAL_OPAMP_MACRO
X_A5      0 N22 N23 IDEAL_OPAMP_MACRO
X_A6      0 N24 N25 IDEAL_OPAMP_MACRO
.PARAM    cc=0p c1=1.59n r4=10k c2=1.59n r3=10k r2=10k r1=10k rg=200k rd=200k
***** Main circuit ends here *****

*****741 Opamp macro model begins here *****
.SUBCKT 741_OPAMP_MACRO  IN+ IN- OUT
R_R4      IN- 0 {2*Ricm}
R_R5      0 IN+ {2*Ricm}
G_G1      N31 0 IN- IN+ 0.19m
R_R1      N32 OUT {Ro}
R_R2      0 N31 {Rp}
R_R3      IN+ IN- {Rid}
C_C2      0 N31 {Cp}
E_EF1     N32 0 N31 0 1
.PARAM    ricm=500e6 gm=0.19m ro=75 rp=1.323e9 rid=2e6 cp=30p
.ENDS
*****741 Opamp macro model ends here *****


***** Ideal Opamp macro model begins here *****
.SUBCKT IDEAL_OPAMP_MACRO  IN+ IN- OUT
E_E1      OUT 0 IN+ IN- 10E6
.ENDS
***** Ideal Opamp macro model ends here *****

***** Analysis begins here*****
.AC DEC 1000 0.1 20K
.PROBE
.END
***** Analysis ends here*****

```
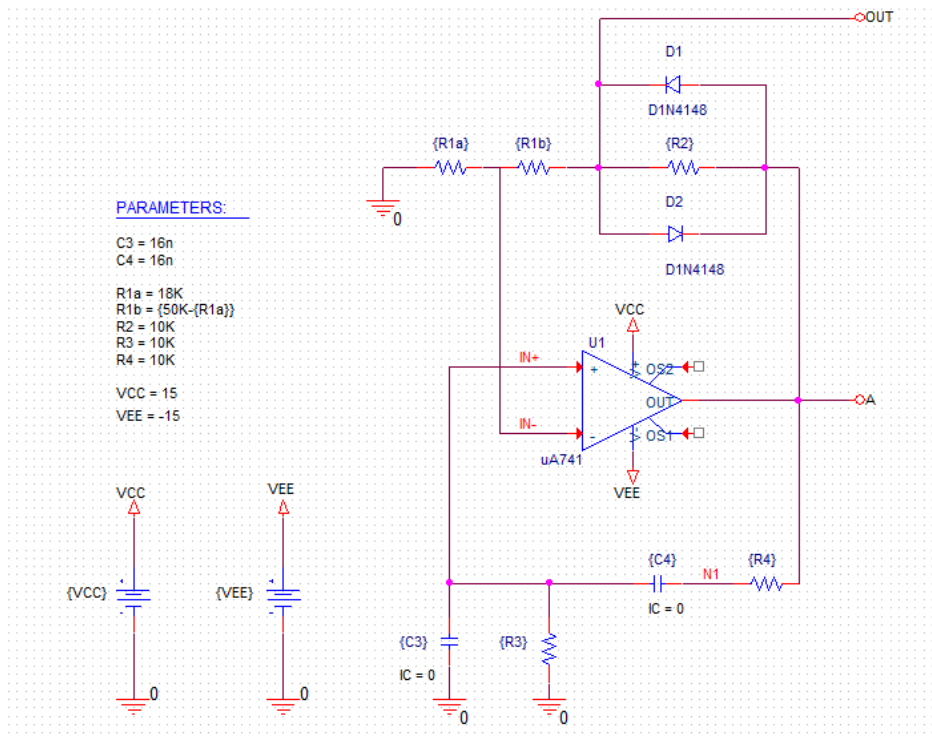
### Example S.15.1

The schematic of this example is shown below.



### Netlist:

Copy the netlist given below and paste it into a text file and save it with \*.cir extension.

```
*****Example S 15.1 *****
***** Main circuit begins here*****
X_U1      IN+  IN-  VCC  VEE  A  uA741
R_R1a    0  IN-  {R1a}
V_VCC    VCC  0  {VCC}
R_R1b    IN-  OUT  {R1b}
R_R2     OUT  A  {R2}
R_R4     N1  A  {R4}
D_D2     OUT  A  D1N4148
R_R3     0  IN+  {R3}
C_C4     N1  IN+  {C4} IC=0
C_C3     0  IN+  {C3} IC=0
D_D1     A  OUT  D1N4148
V_VEE    VEE  0  {VEE}
.PARAM   r1a=18k vee=-15 r4=10k r3=10k c3=16n r2=10k vcc=15 r1b={50k-{r1a}}
+  c4=16n
***** Main circuit ends here *****

***** Model of uA741 begins here*****
* connections:  non-inverting input
```

```

*           |   inverting input
*           | | positive power supply
*           | | | negative power supply
*           | | | | output
*           | | | | |
.subckt uA741 1 2 3 4 5
*
c1  11 12 8.661E-12
c2   6  7 30.00E-12
dc   5 53 dx
de  54  5 dx
dlp 90 91 dx
dln 92 90 dx
dp   4  3 dx
egnd 99  0 poly(2) (3,0) (4,0) 0 .5 .5
fb   7 99 poly(5) vb vc ve vlp vln 0 10.61E6 -10E6 10E6 10E6 -10E6
ga   6  0 11 12 188.5E-6
gcm  0  6 10 99 5.961E-9
iee  10  4 dc 15.16E-6
hlim 90  0 vlim 1K
q1  11  2 13 qx
q2  12  1 14 qx
r2   6  9 100.0E3
rc1  3 11 5.305E3
rc2  3 12 5.305E3
rel  13 10 1.836E3
re2  14 10 1.836E3
ree  10 99 13.19E6
ro1  8  5 50
ro2  7 99 100
rp   3  4 18.16E3
vb   9  0 dc 0
vc   3 53 dc 1
ve  54  4 dc 1
vlim 7  8 dc 0
vlp 91  0 dc 40
vln  0 92 dc 40
.model dx D(Is=800.0E-18 Rs=1)
.model qx NPN(Is=800.0E-18 Bf=93.75)
.ends
***** Model of uA741 ends here*****

***** Model of 1N4148 Diode (from EVAL library in PSpice) begins here*****
.model D1N4148 D(Is=2.682n N=1.836 Rs=.5664 Ikf=44.17m Xti=3 Eg=1.11 Cjo=4p
+
M=.3333 Vj=.5 Fc=.5 Isr=1.565n Nr=2 Bv=100 Ibv=100u Tt=11.54n)
***** Model of 1N4148 Diode (from EVAL library in PSpice) ends here*****


***** Analysis begins here*****
.TRAN 0.001mS 20mS
.PROBE
.END
***** Analysis ends here*****

```



**Example S.15.2**

The schematic of this example is shown below.

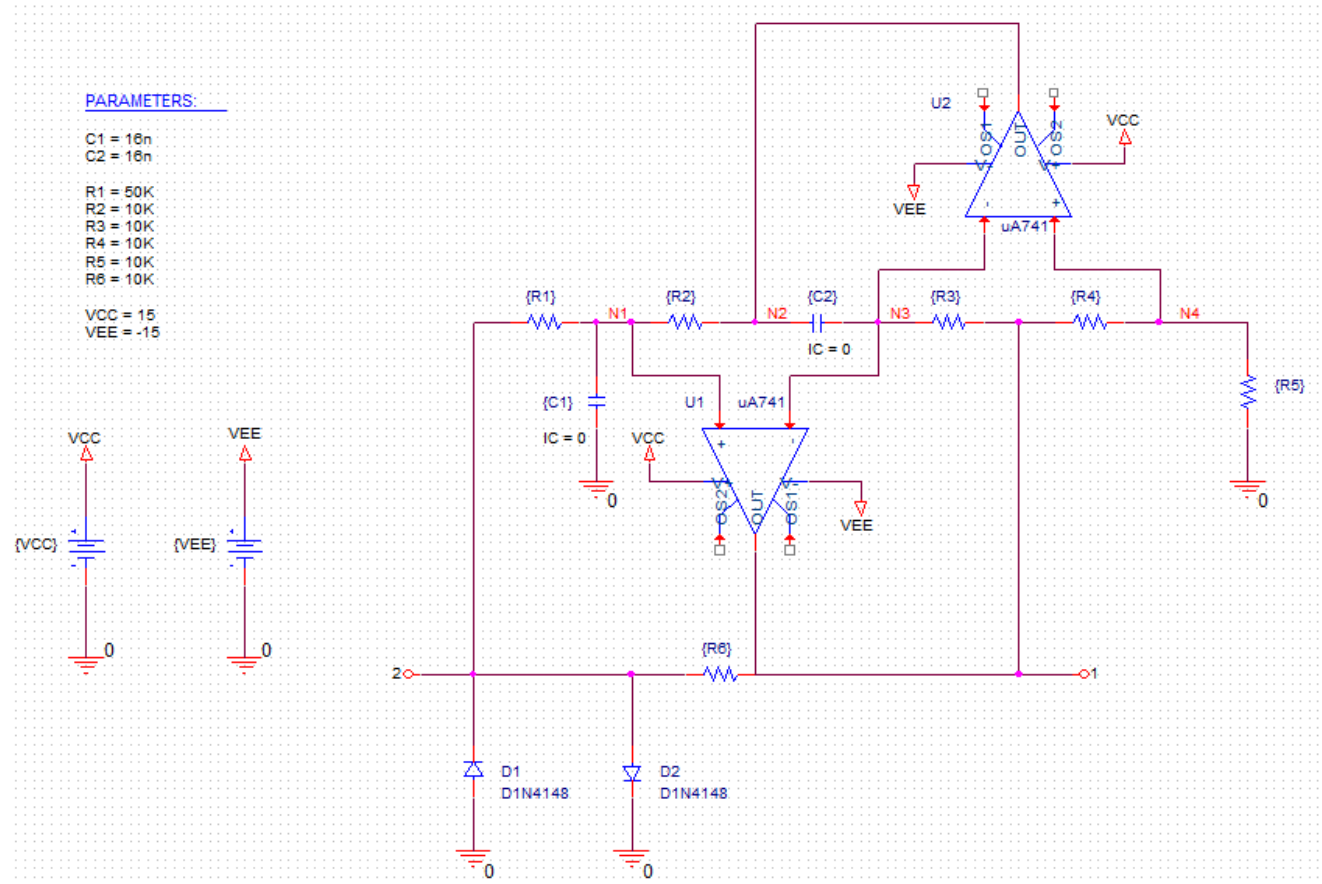**Netlist:**

Copy the netlist given below and paste it into a text file and save it with \*.cir extension.

```
*****Example S 15.2 *****
***** Main circuit begins here*****
X_U1      N1 N3 VCC VEE 1 uA741
C_C4     N3 N2 {C2} IC=0
R_R1a5   N3 1 {R3}
R_R1a6   1 N4 {R4}
V_VEE    VEE 0 {VEE}
X_U2     N4 N3 VCC VEE N2 uA741
C_C3     0 N1 {C1} IC=0
V_VCC    VCC 0 {VCC}
R_R1a4   2 1 {R6}
R_R1a7   0 N4 {R5}
D_D2     2 0 D1N4148
R_R1a    N1 N2 {R2}
```

```

R_R1      2 N1 {R1}
D_D1      0 2 D1N4148
.PARAM    vee=-15 r6=10k r5=10k c1=16n r4=10k r3=10k c2=16n vcc=15 r2=10k r1=50k
***** Main circuit ends here *****

***** Model of uA741 begins here*****
* connections:  non-inverting input
*               | inverting input
*               | | positive power supply
*               | | | negative power supply
*               | | | | output
*               | | | | |
.subckt uA741  1 2 3 4 5
*
c1  11 12 8.661E-12
c2  6 7 30.00E-12
dc  5 53 dx
de  54 5 dx
dlp 90 91 dx
dln 92 90 dx
dp  4 3 dx
egnd 99 0 poly(2) (3,0) (4,0) 0 .5 .5
fb  7 99 poly(5) vb vc ve vlp vln 0 10.61E6 -10E6 10E6 10E6 -10E6
ga  6 0 11 12 188.5E-6
gcm 0 6 10 99 5.961E-9
iee 10 4 dc 15.16E-6
hlim 90 0 vlim 1K
q1  11 2 13 qx
q2  12 1 14 qx
r2  6 9 100.0E3
rc1 3 11 5.305E3
rc2 3 12 5.305E3
re1 13 10 1.836E3
re2 14 10 1.836E3
ree 10 99 13.19E6
ro1 8 5 50
ro2 7 99 100
rp  3 4 18.16E3
vb  9 0 dc 0
vc  3 53 dc 1
ve  54 4 dc 1
vlim 7 8 dc 0
vlp 91 0 dc 40
vln 0 92 dc 40
.model dx D(Is=800.0E-18 Rs=1)
.model qx NPN(Is=800.0E-18 Bf=93.75)
.ends
***** Model of uA741 ends here*****


***** Model of 1N4148 Diode (from EVAL library in PSpice) begins here*****
.model D1N4148 D(Is=2.682n N=1.836 Rs=.5664 Ikf=44.17m Xti=3 Eg=1.11 Cjo=4p
+
M=.3333 Vj=.5 Fc=.5 Isr=1.565n Nr=2 Bv=100 Ibv=100u Tt=11.54n)
***** Model of 1N4148 Diode (from EVAL library in PSpice) ends here*****

***** Analysis begins here*****
.TRAN 0.001mS 50mS
.PROBE
.END
***** Analysis ends here*****

```

**Example S.16.1**

The schematic of this example is shown below.

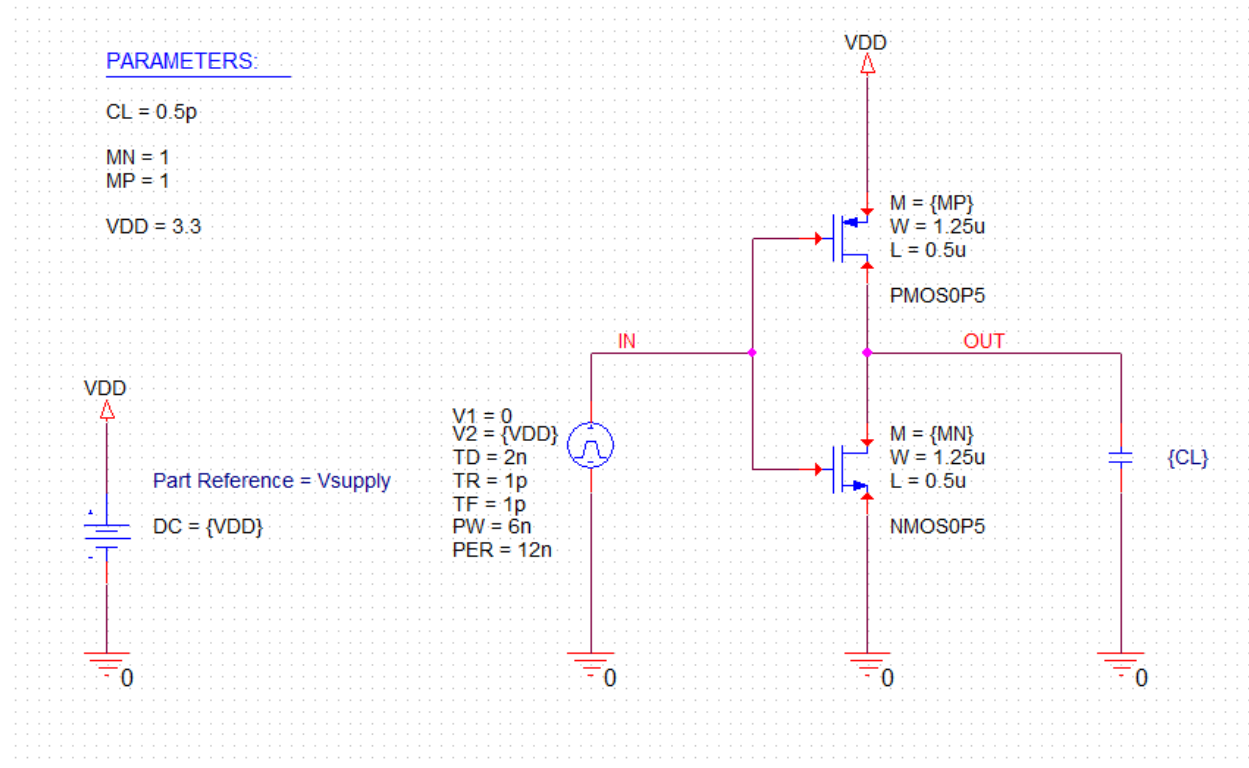**Netlist:**

Copy the netlist given below and paste it into a text file and save it with \*.cir extension.

```
*****Example S 16.1 *****
***** Main circuit begins here*****
V_Vin      IN 0
+PULSE 0 {VDD} 2n 1p 1p 6n 12n
M_M1      OUT IN VDD VDD PMOS0P5
+ L=0.5u
+ W=1.25u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M={MP}
C_C10     0 OUT {CL}
M_M2     OUT IN 0 0 NMOS0P5
+ L=0.5u
+ W=1.25u
+ AD=1.72E-12
+ AS=1.72E-12
+ PD=5.25E-6
+ PS=5.25E-6
+ M={MN}
```

```

V_Vsupply          VDD 0 {VDD}
.PARAM  cl=0.5p vdd=3.3 mp=1 mn=1
***** Main circuit ends here*****

*****Model for NMOS in 0.5um CMOS Technology begins here*****
*
  (created by Anas Hamoui & Olivier Trescases)
.model NMOS0P5 NMOS(Level=1 VTO=0.7 GAMMA=0.5 PHI=0.8
+
  LD=0.08E-06 WD=0 UO=460 LAMBDA=0.1 TOX=9.5E-9 PB=0.9 CJ=0.57E-3
+
  CJSW=120E-12 MJ=0.5 MJSW=0.4 CGDO=0.4E-9 JS=10E-9 CGBO=0.38E-9
+
  CGSO=0.4E-9)
*****Model for NMOS in 0.5um CMOS Technology ends here*****

*****Model for PMOS in 0.5um CMOS Technology begins here*****
*
  (created by Anas Hamoui & Olivier Trescases)
.model PMOS0P5 PMOS(Level=1 VTO=-0.8 GAMMA=0.45 PHI=0.8
+
  LD=0.09E-06 WD=0 UO=115 LAMBDA=0.2 TOX=9.5E-9 PB=0.9 CJ=0.93E-3
+
  CJSW=170E-12 MJ=0.5 MJSW=0.35 CGDO=0.35E-9 JS=5E-9 CGBO=0.38E-9
+
  CGSO=0.35E-9)
*****Model for PMOS in 0.5um CMOS Technology ends here*****

***** Analysis begins here*****
.DC [LIN] V_Vin 0 3.3 10m
*.TRAN 0.01nS 14nS
.PROBE
.END
***** Analysis ends here*****

```