

Microelectronic Circuits

8th Edition


A. Sedra, K.C. Smith
T. Chan Carusone, V. Gaudet

*Spice Problems Solutions
Chapter 16*


*Prepared by: Nijwm Wary
2019*

Problem: 16.29

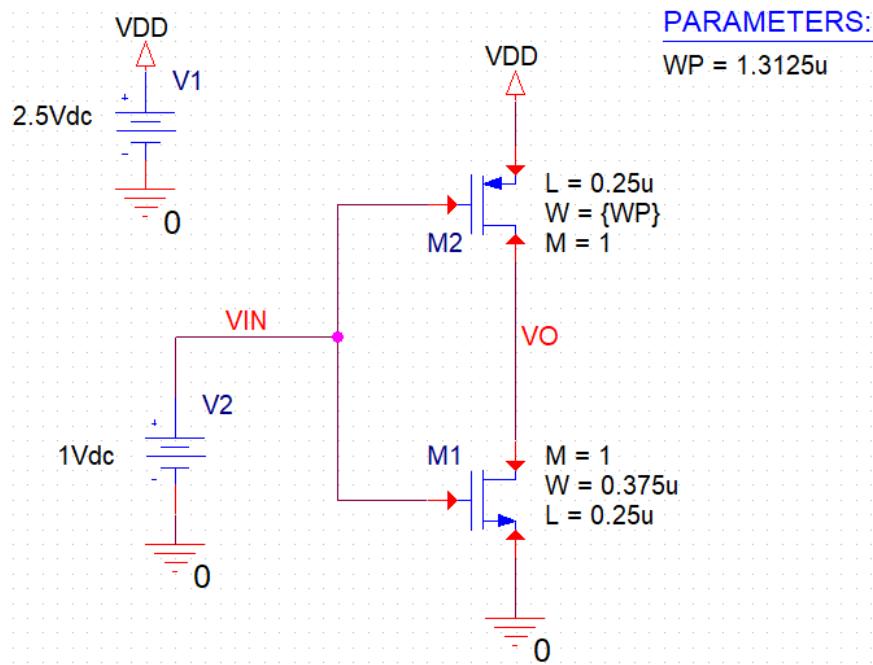
1. The schematics for this problem is shown below



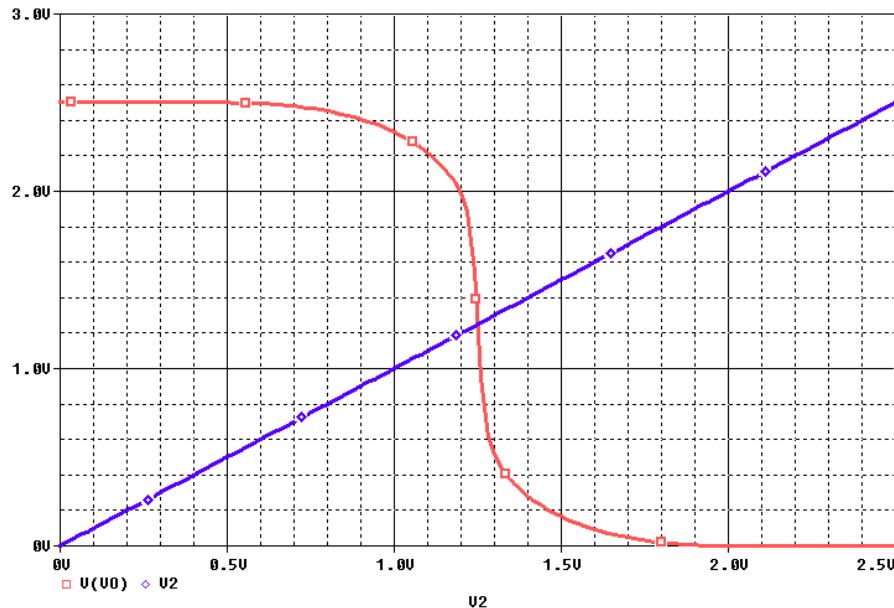
2. Run the netlist to perform a DC sweep. Plot V(VO) and V2 for WP=1.3123u (WP=3.5WN). In this case, VM=1.25V.



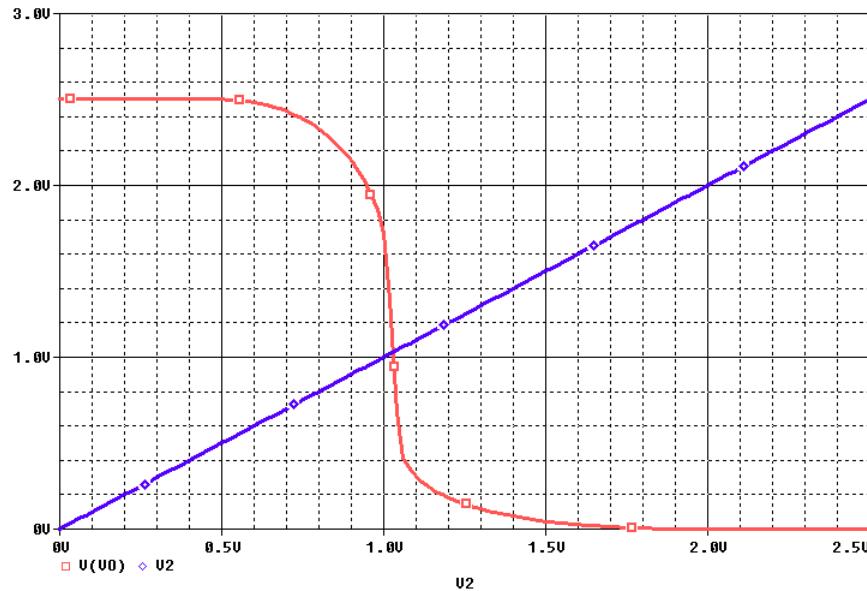3. Next, plot V(VO) for WP=0.375u (WP=WN). In this case, VM=1.03V.



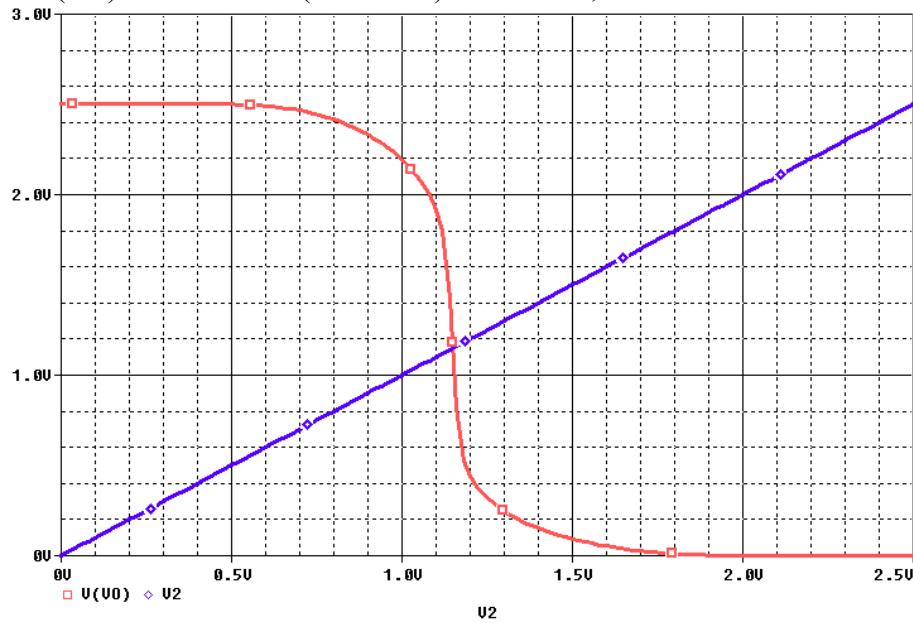4. Finally, plot $V(V_O)$ for $WP = 0.75u$ ($WP = 2WN$). In this case, $VM = 1.15V$.



Netlist:

Copy the netlist given below and paste it into a text file and save it with *.cir extension.

```
*****Problem: P16_29 ****
***** Main circuit begins here*****
M1           VO VIN 0 0 NMOSOP25
+  L=0.25u
+  W=0.375u
+  M=1
M2           VO VIN VDD VDD PMOSOP25
+  L=0.25u
+  W={WP}
+  M=1
V1           VDD 0 2.5Vdc
V2           VIN 0 1Vdc
.PARAM  wp=1.3125u
***** Main circuit ends here*****


***** PMOS model begins here ****
.model PMOSOP25      PMOS(Level=1 VTO=-0.5 GAMMA=0.5 PHI=0.8
+          LD=0 WD=0 UO=200 LAMBDA=0.1 TOX=6E-9 PB=0.9)
***** PMOS model ends here *****

***** NMOS model begins here ****
.model NMOSOP25      NMOS(Level=1 VTO=0.5 GAMMA=0.5 PHI=0.8
+          LD=0 WD=0 UO=700 LAMBDA=0.1 TOX=6E-9 PB=0.9)
***** NMOS model ends here *****

***** Analysis begins here*****
.DC [LIN] V2 0 2.5 0.02
.PROBE
.END
***** Analysis ends here*****
```