

## APPENDIX L

# ANSWERS TO SELECTED PROBLEMS

## Chapter 1

- 1.1** (a) 5 V, 25 mW; (b) 5 k $\Omega$ , 5 mW; (c) 10 mA, 1 k $\Omega$ ; (d) 10 V, 100 k $\Omega$ ; (e) 31.6 mA, 31.6 V
- 1.2** (a) 5 mA; (b) 5 k $\Omega$ ; (c) 1 V; (d) 10 mA
- 1.5** 990 k $\Omega$ , 190 k $\Omega$ , 90 k $\Omega$ , 10 k $\Omega$ ; 9.9 k $\Omega$ , 9.09 k $\Omega$ , 5 k $\Omega$
- 1.6** 2 V, 1.2 k $\Omega$ ; 1.88 V to 2.12 V; 1.26 k $\Omega$  to 1.14 k $\Omega$
- 1.9** 4.80 V, Shunt the 10-k $\Omega$  resistor with 157 k $\Omega$ ; Add a series resistance of 200  $\Omega$ .
- 1.16** 0.05 mA
- 1.17**  $I_1 = 0.75$  mA;  $I_2 = 0.5$  mA;  $I_3 = 1.25$  mA; 2.5 V
- 1.19** 2 V
- 1.22** (a)  $(1 - j 1.59)$  k $\Omega$ ; (b)  $(247.3 - j 1553)$   $\Omega$ ; (c)  $(71.72 - j 45.04)$  k $\Omega$ ; (d)  $(100 + j 628)$   $\Omega$
- 1.25** (a)  $v_s = 1$  V,  $i_s = 0.1$  mA,  $R_s = 10$  k $\Omega$ ;  
(b)  $v_s = 0.1$  V,  $i_s = 1$   $\mu$ A,  $R_s = 100$  k $\Omega$
- 1.27** (a) 2%; 9%; (b) 1%; 8%; (c) 9%; 0.4%; 0.5 mA; (d) 9%; 1%; 6.67 mA
- 1.28** 55.2  $\Omega$
- 1.29** 5 k $\Omega$
- 1.35** (a) 165 V; (b) 24 V; (c) 311 V; (d) 311 kV
- 1.37** 2% lower
- 1.42** (b)  $b_N$ ;  $b_1$ ; (c) 0.996 mA; 3.91  $\mu$ A
- 1.43**  $7.056 \times 10^5$  bits per second
- 1.44** 66
- 1.45** (a) 100 V/V; 40 dB; 1000 A/A; 60 dB;  $10^5$  W/W; 50 dB; (b)  $10^5$  V/V; 100 dB; 1000 A/A; 60 dB;  $10^8$  W/W; 80 dB; (c) 5 V/V; 14 dB; 500 A/A; 54 dB; 2500 W/W; 34 dB
- 1.46** 2.8 V<sub>rms</sub>; 14 mV<sub>rms</sub>; 6.4 V<sub>rms</sub>; 32 mV<sub>rms</sub>; 9.9 V<sub>rms</sub>; 50 mV<sub>rms</sub>
- 1.50** 412.7 V/V
- 1.51** 1.1 mA; 10 k $\Omega$
- 1.52** 4.95 A/A; 13.9 dB; 4.9 V/V; 13.8 dB; 24.3 W/W; 27.7 dB
- 1.53** 38.1 V/V
- 1.54** 38.4 dB; 71.4 dB; 85 mV; 0.1 W
- 1.55** 0.69 V; -3.2 dB; 78.4 dB; 37.6 dB
- 1.62** 0 V; 10 V
- 1.69** 4 MHz; 0.8 V/V

- 1.76**  $0.53 \text{ k}\Omega$ ;  $10.5 \text{ }\Omega$ ;  $526 \text{ }\Omega$   
**1.77**  $0.51/CR$   
**1.81**  $90 \text{ k}\Omega$ ;  $6.61 \text{ k}\Omega$ ;  $27.9 \text{ mA/V}$   
**1.85**  $2.2 \times 10^6 \text{ carriers/cm}^3$   
**1.88**  $1.5 \times 10^{18} \text{ atoms/cm}^3$   
**1.94**  $9.26 \times 10^{17}/\text{cm}^3$   
**1.95**  $0.864 \text{ A/cm}^2$   
**1.96**  $V_0 = 0.754 \text{ V}$   
 $W = 0.328 \text{ }\mu\text{m}$   
 $x_n = 0.298 \text{ }\mu\text{m}$   
 $x_p = 0.03 \text{ }\mu\text{m}$   
 $Q_J = 4.8 \times 10^{-14} \text{ C}$   
**1.100**  $59.6 \text{ mV}$   
**1.104**  $7.85 \times 10^{-17} \text{ A}$ ;  $0.3 \text{ mA}$   
**1.109**  $10.42 \text{ mA}$ ;  $41.7 \text{ mA}$   
**1.112**  $31.6 \text{ fF}$ ;  $14.16 \text{ fF}$

## Chapter 2

- 2.1**  $4004 \text{ V/V}$   
**2.4**  $8$ ;  $14$   
**2.5**  $-1.000 \text{ V}$ ;  $400 \text{ V/V}$   
**2.6**  $40,000 \text{ V/V}$   
**2.10** (a)  $-2 \text{ V/V}$ ; (b)  $-10 \text{ V/V}$ ; (c)  $-0.5 \text{ V/V}$ ; (d)  $-50 \text{ V/V}$ ; (e)  $-5 \text{ V/V}$   
**2.12**  $5 \text{ k}\Omega$   
**2.14**  $V_o = 5.1 \text{ V}$  to  $4.9 \text{ V}$   
 $V_o = 4.85 \text{ V}$  to  $5.15 \text{ V}$   
**2.17** (a)  $10.2 \text{ k}\Omega$   
**2.27**  $3 \text{ mA}$ ;  $R_1 = 2 \text{ k}\Omega$ ;  $R_2 = 20 \text{ k}\Omega$   
**2.28**  $\pm 2x\%$ ;  $-98 \text{ V/V}$  to  $-102 \text{ V/V}$   
**2.30**  $\pm 2 \text{ mV}$   
**2.37**  $-\frac{R_2}{R_1} \left( 1 + \frac{R_4}{R_3} + \frac{R_4}{R_2} \right)$   
**2.40**  $R_1 = 100 \text{ k}\Omega$ ,  $R_2 = 100 \text{ k}\Omega$ ,  $R_3 = 1.02 \text{ k}\Omega$ ;  $-2.48 \text{ V/V}$   
**2.46**  $\frac{1 + R_2/R_1}{1 + R_3/R_4}$

2.50	Case	Gain (V/V)	$R_{in}$	$R_1$	$R_2$
	a	-10	10 k $\Omega$	10 k $\Omega$	100 k $\Omega$
	b	-1	100 k $\Omega$	100 k $\Omega$	100 k $\Omega$
	c	-2	100 k $\Omega$	100 k $\Omega$	200 k $\Omega$
	d	+1	$\infty$	$\infty$	0
	e	+2	$\infty$	100 k $\Omega$	100 k $\Omega$
	f	+11	$\infty$	10 k $\Omega$	100 k $\Omega$
	g	-0.5	20 k $\Omega$	20 k $\Omega$	10 k $\Omega$

**2.51** 1980 V/V

**2.53**  $-10 \text{ V} \leq v_o \leq +10 \text{ V}$ ;  $\Delta v_o = 1 \text{ V}$

**2.55** 100 k $\Omega$ ; no

**2.58**  $2 \sin(2\pi \times 1000t)$

**2.61** 9.09 V/V; 81 k $\Omega$  in parallel with  $R_1$ ; 9.52 V/V; 10.52 V/V

**2.65** (a) 0 dB; (b)  $20 \log(1 + R_2/R_1)$

**2.72** (a) 1 V/V; 0 V/V; (b)  $-5 \text{ V} \leq v_{lcm}$ ; (c) 10 V/V; 0 V/V;  $-3 \text{ V} \leq v_{lcm} \leq +3 \text{ V}$

**2.73** 1 M $\Omega$ ; 756  $\Omega$ ; 6.8 k $\Omega$

**2.81** (a) 1.59 kHz; (c) increase by  $10\times$

**2.84**  $R = 10 \text{ k}\Omega$ ,  $C = 159 \text{ pF}$ ;  $R_F = 1 \text{ M}\Omega$ , 1 kHz; (a)  $v_o$  decreases linearly to  $-6.3 \text{ V}$ , (b)  $v_o$  decreases exponentially,  $v_o(t) = -100(1 - e^{-t/159})$ , reaching  $-6.1 \text{ V}$  at the end of the pulse.

**2.89**  $R_1 = 10 \text{ k}\Omega$ ;  $R_2 = 100 \text{ k}\Omega$ ;  $C_2 = 15.9 \text{ pF}$ ; 2 MHz

**2.92**  $R_1 = 1 \text{ k}\Omega$ ,  $R_2 = 100 \text{ k}\Omega$ ,  $C = 79 \text{ nF}$ ; 20 Hz

**2.94** 4 mV

**2.96** (a) 0.2 V; (b) 0.3 V; (c) 10 k $\Omega$ ; 20 mV; (d) 0.12 V

**2.99** (a) 0.53  $\mu\text{A}$ , into the input terminals; (b)  $-3 \text{ mV}$ ; (c)  $-60 \text{ nA}$

**2.101**  $R_1 = 1.01 \text{ k}\Omega$ ,  $R_2 = R_3 = 100 \text{ k}\Omega$ ,  $C_1 = 1.58 \mu\text{F}$ ,  $C_2 = 0.16 \mu\text{F}$

**2.103** 6 V; 3 V; 9 mV

**2.106** (a) 9.9 k $\Omega$ ; (b) 0.222 V

**2.107** 80,000 V/V, 125 Hz, 10 MHz

**2.111** (a) 50 Hz, 10 MHz; (b) 1 Hz, 2 MHz; (c) 10 kHz, 18 MHz; (d) 10 MHz, 1 GHz; (e) 24 kHz, 625 MHz

**2.113** 200 kHz; 21 kHz; 1.9 MHz

**2.115** 24 V/V

**2.116** 36.6 MHz

**2.121** 100 mV

**2.124** 40 V/ $\mu\text{s}$

**2.126** 637 kHz

**2.127** (a) 318.3 kHz; (b) 0.795 V; (c) 2 MHz; (d) 1 V

## Chapter 3

- 3.1** (a)  $-3\text{ V}$ ,  $0.6\text{ mA}$ ; (b)  $+3\text{ V}$ ,  $0\text{ mA}$   
**3.3** (a)  $0\text{ V}$ ;  $2\text{ mA}$ ; (b)  $-1.5\text{ V}$ ;  $0\text{ mA}$   
**3.4**  $4.2\text{ k}\Omega$ ;  $169.7\text{ V}$   
**3.5**  $-7\text{ V} \leq v_l \leq 8\text{ V}$   
**3.6**  $1.95\text{ A}$ ;  $10\text{ V}$   
**3.8** (a)  $V = 2\text{ V}$ ,  $I = 2.5\text{ mA}$ ; (b)  $I = 1\text{ mA}$ ,  $V = 1\text{ V}$   
**3.13**  $25\text{ mA}$ ;  $12.5\text{ mA}$   
**3.16**  $V = +3\text{ V} \Rightarrow$  red ON, green OFF;  $V = 0\text{ V} \Rightarrow$  red OFF, green OFF;  $V = -3\text{ V} \Rightarrow$  red OFF, green ON  
**3.21**  $87.7\text{ mV}$ ;  $5.16\text{ mA}$   
**3.24**  $0.230\text{ V}$ ;  $1.45 \times 10^{12} I_s$   
**3.28** Decrease by  $17.3\text{ mV}$   
**3.32**  $50^\circ\text{ C}$ ;  $6\text{ W}$ ;  $8.33^\circ\text{C/W}$   
**3.33**  $230\text{ mV}$  independent of current and temperature  
**3.35**  $0.664\text{ V}$   
**3.39** (a)  $1.3\text{ mA}$ ;  $0\text{ V}$ ; (b)  $0\text{ mA}$ ;  $-1.675\text{ V}$   
**3.40**  $4.23\text{ k}\Omega$ ;  $169.7\text{ V}$   
**3.42** (a)  $0.767\text{ mA}$ ; (b)  $5.3 \times 10^{-16}\text{ A}$ ; (c)  $0.805\text{ mA}$   
**3.47**  $14.71\text{ V}$ ;  $3.61\text{ V}$   
**3.49**  $+22.1\%$  or  $-18.1\%$ ;  $+2.38\text{ mV}$  or  $-2.63\text{ mV}$   
**3.51** (a)  $0\text{ V/V}$ ;  $0.167\text{ V/V}$ ;  $0.667\text{ V/V}$ ;  $0.952\text{ V/V}$ ;  $0.995\text{ V/V}$ ;  $0.9995\text{ V/V}$ ; (b)  $|\Delta v_D| < 2.5\text{ mV}$ ;  $I \geq 5\mu\text{ A}$ ; (c)  $1\text{ V}$ ;  $1.005\text{ V}$ ;  $i_{D1} = i_{D4} = 0.45\text{ mA}$ ;  $i_{D2} = i_{D3} = 0.55\text{ mA}$   
**3.54**  $0\text{ V/V}$ ;  $0.001\text{ V/V}$ ;  $0.01\text{ V/V}$ ;  $0.1\text{ V/V}$ ;  $0.5\text{ V/V}$ ;  $0.6\text{ V/V}$ ;  $0.9\text{ V/V}$ ;  $0.99\text{ V/V}$   
**3.58**  $R = 417\ \Omega$ ;  $7.39\text{ mA}$ ;  $6.8\text{ mV}$ ;  $-3.4\text{ mV}$ ;  $-6.8\text{ mV}$ ;  $-13.6\text{ mV}$   
**3.64** (a)  $9.825\text{ V}$ ; (b)  $207\ \Omega$ ; (c)  $33\text{ mV/V}$ ;  $\pm 1.65\%$ ; (d)  $-6.77\text{ V/A}$ ;  $-1.35\%$ ; (e)  $70.9\text{ mA}$ ;  $732\text{ mW}$   
**3.67**  $13.44\text{ V}$ ;  $48.4\%$ ;  $8.3\text{ V}$ ;  $16.6\text{ mA}$   
**3.69** (a)  $10.1:1$ ; (b)  $1.072:1$   
**3.72** (a)  $12.77\text{ V}$ ,  $13.37\text{ V}$ ; (b)  $14.2\%$ ,  $4.5\%$ ; (c)  $102.5\text{ mA}$ ,  $310\text{ mA}$ ; (d)  $192\text{ mA}$ ,  $607\text{ mA}$   
**3.76**  $0.441\text{ V}$   
**3.79** (a)  $9.7\text{ V}$ ; (b)  $542\ \mu\text{F}$ ; (c)  $25.7\text{ V}$  ( $38.5\text{ V}$  with  $1.5\times$  safety factor); (d)  $739\text{ mA}$ ; (e)  $1.42\text{ A}$   
**3.86**  $-7.07\text{ V}$   
**3.87** (a)  $80\ \Omega$ ; (b)  $120\ \Omega$   
**3.90**  $0.70\text{ V} < V_R < 2.87\text{ V}$

## Chapter 4

- 4.1** 1. Active; 2. Saturation; 3. Active; 4. Saturation; 5. Active; 6. Cutoff  
**4.2**  $4.7 \times 10^{-17}\text{ A}$ ,  $1.87 \times 10^{-16}\text{ A}$ ;  $A_2/A_1 = 4$

- 4.4 80; 0.988
- 4.6 990  $\mu\text{A}$ , 99, 0.99; 980  $\mu\text{A}$ , 49, 0.98; 950  $\mu\text{A}$ , 19, 0.95
- 4.9  $V_B = -0.616\text{ V}$ ;  $V_C = -0.9\text{ V}$ ;  $I_E = 0.51\text{ mA}$
- 4.12 0.31 V
- 4.14 0.45 mA; 0.587 V
- 4.18  $i_C = 7.2\text{ mA}$ ;  $i_B = 144\text{ }\mu\text{A}$  to  $36\text{ }\mu\text{A}$ ;  $i_E = 7.344\text{ mA}$  to  $7.236\text{ mA}$
- 4.21 437 k $\Omega$ ; 8 k $\Omega$
- 4.24 0.758 V; 0.815 V
- 4.31  $R_E = 1.62\text{ k}\Omega$ ,  $R_C = 3\text{ k}\Omega$
- 4.33 125 k $\Omega$ ; 125 V; 12.5 k $\Omega$
- 4.35 (a) 2.3 V; (b) 2.64 V; (c) 10.5 V
- 4.40 (a)  $I_E = 0.26\text{ mA}$ ,  $I_B = 0.005\text{ mA}$ ,  $I_C = 0.255\text{ mA}$ ,  $V_E = -0.8\text{ V}$ ,  $V_C = 0.81\text{ V}$ ;  
 (b)  $I_E = 0.35\text{ mA}$ ,  $I_B = 0.007\text{ mA}$ ,  $I_C = 0.343\text{ mA}$ ,  $V_E = +0.8\text{ V}$ ,  
 $V_C = -0.81\text{ V}$ ; (c)  $I_E = 0.12\text{ mA}$ ,  $I_B = 2.4\text{ }\mu\text{A}$ ,  $I_C = 0.118\text{ mA}$ ,  $V_E = +1.8\text{ V}$ ,  
 $V_C = 0.236\text{ V}$ ; (d)  $I_E = 0.15\text{ mA}$ ,  $I_B = 3\text{ }\mu\text{A}$ ,  $I_C = 0.147\text{ mA}$ ,  $V_E = 0.7\text{ V}$ ,  $V_C = 1.8\text{ V}$
- 4.43 (a) 632 mV; (b) 0.69 mA, 5.77 mA
- 4.46 0.1 mA, 0.11 mA;  $-8.16\text{ V}$ ;  $+22\text{ mV}/^\circ\text{C}$ ;  $-7.06\text{ V}$
- 4.49 100; 80; 1.18 mA
- 4.51 (a) 1.3 V, 3.7 V; (b) 1 V, 4 V; (c) 0 V, 5 V
- 4.52 0.3 V; 0.003 mA; 0.15 mA; 0.147 mA;  $-1.03\text{ V}$ ; 49; 0.98
- 4.53 1.86 V, 1.16 V, 1.85 V; 2.14 V, 1.44 V, 1.64 V; 2.4 V, 1.7 V, 1.9 V
- 4.55 (a)  $-0.915\text{ V}$ ,  $+1.218\text{ V}$ ; (b)  $+1.258\text{ V}$ , 0.49 mA; (c)  $-0.9\text{ V}$ ,  $-0.2\text{ V}$ ,  $+1.4\text{ V}$ ;  
 (d)  $+1.7\text{ V}$ ,  $-0.9\text{ V}$ ; (e)  $+1\text{ V}$ ,  $+1.7\text{ V}$ ,  $-0.9\text{ V}$
- 4.57 (a) 0 V, 0 V; (b)  $-1.8\text{ V}$ ,  $-1.1\text{ V}$ ; (c)  $+2.2\text{ V}$ ,  $+1.5\text{ V}$ ; (d)  $+3\text{ V}$ ,  $2.3\text{ V}$
- 4.61  $R_1 = 35\text{ k}\Omega$ ,  $R_2 = 15\text{ k}\Omega$ ; 0.078 mA; 4.22 V
- 4.63  $+0.41\text{ V}$ ,  $+1.11\text{ V}$ ;  $-1.15\text{ V}$ ;  $+1.2\text{ V}$ ,  $+1.9\text{ V}$ ,  $-1.9\text{ V}$ ; 204
- 4.65 50 k $\Omega$ , 4 k $\Omega$ , 4 k $\Omega$ ; 0.85 mA to 0.98 mA with 0.95 mA nominal;  $-1.6\text{ V}$  to  $-1.1\text{ V}$   
 with  $-1.2\text{ V}$  nominal.
- 4.66 1.74 k $\Omega$ ; transistor saturates and  $V_C = 2.8\text{ V}$
- 4.67 (a) 0 V,  $+0.7\text{ V}$ ,  $-0.725\text{ V}$ ,  $-1.425\text{ V}$ ,  $+1.1\text{ V}$ ; (b)  $+0.23\text{ V}$ ,  $+0.93\text{ V}$ ,  $-1\text{ V}$ ,  $-1.7\text{ V}$ ,  
 $+1.47\text{ V}$
- 4.69 (a)  $+0.8\text{ V}$ , 2.3; (b)  $+2.07\text{ V}$ , 3.2; (c)  $V_{C3} = 2.044\text{ V}$ ,  $V_{C4} = 1.54\text{ V}$ ,  $\beta_{\text{forced3}} = 0.8$ ,  
 $\beta_{\text{forced4}} = 6.4$ .

## Chapter 5

- 5.2  $0.825\text{ V} \leq v_{GS} \leq 1.8\text{ V}$
- 5.3 (a)  $8.625 \times 10^{-3}\text{ pF}/\mu\text{m}^2$ , 388  $\mu\text{A}/\text{V}^2$ ; (b) 0.2 V, 0.7 V, 0.2 V; (c) 0.39 V, 0.89 V
- 5.5 (a) 4 mA; (b) 3 mA; (c) 1 mA; (d) 5.3 mA
- 5.7 0.16 fC
- 5.8 (a) 0.5; (b) 0.5; (c) 1.0; (d) 0.5
- 5.10 1.85  $\mu\text{m}$

- 5.12** 0.5 V; 0.5 mA  
**5.14** 96.2  $\Omega$ , 19.2 mV; 80  
**5.15** 2.8 V; 500  $\Omega$ , 100  $\Omega$   
**5.17** 5 mA/V<sup>2</sup>; 0.6 V  
**5.21** 100 k $\Omega$ , 20 V, 0.05 V<sup>-1</sup>  
**5.27** 1.07  $\mu\text{m}$   
**5.29** 2.5 k $\Omega$  to 125  $\Omega$ ; (a) 5 k $\Omega$  to 250  $\Omega$ ; (b) 1.5 k $\Omega$  to 62.5  $\Omega$ ; 2.5 k $\Omega$  to 125  $\Omega$   
**5.33** (a) 3%; (b) 5%  
**5.35** 109  $\mu\text{A}$ ; 9%; double  $L$  to 2  $\mu\text{m}$   
**5.38** 50 V; 0.5  $\mu\text{m}$   
**5.39** 8  $\mu\text{A}$ ; 12  $\mu\text{A}$ ; 13.13  $\mu\text{A}$ ; 13.75  $\mu\text{A}$ ; 15  $\mu\text{A}$   
**5.45** 2.25  $\mu\text{m}$ , 0.56  $\mu\text{m}$ , 4 k $\Omega$   
**5.46** 44.4, 1.25 k $\Omega$   
**5.48** (a) 360  $\mu\text{A}$ , 1 V; (b) 160  $\mu\text{A}$ , 0.8 V; (c) 1 V, 360  $\mu\text{A}$   
**5.52** 4 k $\Omega$   
**5.54**  $W_1 = 11.1 \mu\text{m}$ ;  $W_2 = 25 \mu\text{m}$ ;  $W_3 = 4 \mu\text{m}$   
**5.55** 0.454 mA, +7.28 V; circuit is quiet tolerant to variations in device parameters.  
**5.57** (a) -0.6 V; (b) -0.816 V; (c) -1.5 V; (d) +0.6 V; (e) +1.5 V; (f) +0.6 V; (g) +1.5 V; (h) -0.6 V  
**5.62** 1 V to 1.69 V; 3.74 V  
**5.65** 488 million transistors  
**5.68** 0.3 mA, 0.416 mA, 0.424 mA, 0.48 mA; each current value is doubled; for  $v_{DS} = 2 \text{ V}$ ,  $i_D = 0.408 \text{ mA}$ , for  $v_{DS} = 3 \text{ V}$ ,  $i_D = 0.412 \text{ V}$ , for  $v_{DS} = 10 \text{ V}$ ,  $i_D = 0.44 \text{ mA}$

## Chapter 6

- 6.1** Point A:  $v_{GS} = 0.5 \text{ V}$ ,  $v_{DS} = 5 \text{ V}$ ; Point B:  $V_{GS} = 0.72 \text{ V}$ ,  $V_{DS} = 0.22 \text{ V}$   
**6.4** -160 V/V; 0.7 V; 4.4 mV  
**6.6** -40 V/V  
**6.7** (a) 108 V/V; (b) 1.5 V; (c) 3 k $\Omega$ ; (d) 0.673 V; (e) 0.3 V; (f) 0.1 sin  $\omega t$ , mA; (g) 0.005 mA, 0.001 sin  $\omega t$ , mA; (h) 5 k $\Omega$   
**6.9** 0.214 V; 0.716 V  
**6.11** 0.4 V; 8.33  
**6.15** 1.08 V; 0.78 V; -156.7 V/V  
**6.20**  $g_m = I_C/V_T = 20 \text{ mA/V}$   
**6.23** (a) 0.1 mA, 0.5 V; (b) 1 mA/V; (c) -15 V/V; (d) -0.225 sin  $\omega t$ , V, 0.275 V, 0.725 V; (e) 1.9%  
**6.26** -26.1 V/V; 1.25 V, -38.3 V/V  
**6.29** 40 mA/V; 25  $\Omega$ ; 2.5 k $\Omega$ ; 1 V  
**6.32** 1 V; 125  $\Omega$ ; 80 V/V  
**6.38** (a) 0.1 mA, 0.8 V; (b) 1 mA/V; (c) -10 V/V; (d) 100 k $\Omega$ , -9.1 V/V

- 6.39** (a) 2 mA/V, 20 k $\Omega$ ; (b) 2.9 mA/V, 10 k $\Omega$
- 6.40** 16  $\mu$ m; 0.75 V
- 6.44**  $\beta_{\min} = 90$
- 6.45** 1.04 k $\Omega$  to 4.7 k $\Omega$
- 6.55**  $-1000$  V/V;  $-5000$  V/V
- 6.59** 1000 V/V; 250 V/V
- 6.63** 5 mA/V; 4 k $\Omega$ ; 50  $\Omega$
- 6.67** 2.5 mA; 2.75 mA; 2.25 mA; 0.55 V
- 6.69** 1 V/V; 105  $\Omega$ ; 0.9 V/V
- 6.71** 79.4 V/V; 4762 A/A
- 6.74**  $-10$  V/V
- 6.75** 1 mA/V; 125  $\mu$ A;  $-7.5$  V/V
- 6.79** 0.5 k $\Omega$
- 6.82** 0.2 k $\Omega$ ; 5.6 V/V; 0.64
- 6.83** 0.5 mA; 25 V/V
- 6.84** 8 V/V; 50 mV; 0.4 V
- 6.86** (a) 20.7 k $\Omega$ , 0.67 V/V, 0.65 V/V; (b) 0.615 V, 0.4 V; (c) 1 V/V, 104  $\Omega$ , 0.59 V/V
- 6.90** 27.5 V/V, 41.2 V/V, 55.6 V/V, 57.1 V/V, 55.6 V/V; 0.325 mA
- 6.91** 22 M $\Omega$ ; 18 M $\Omega$ ; 15 k $\Omega$ ; 15 k $\Omega$ ; 2.7 V above
- 6.96** 6.2 k $\Omega$ ; 6.2 k $\Omega$ ; 100 k $\Omega$ ; 82 k $\Omega$ ; 0.5 mA; 0.49 mA; 3.8 V; 6 V
- 6.97**  $R_E = 1.5$  k $\Omega$ ;  $R_C = 2.4$  k $\Omega$ ;  $R_B = 7.5$  M $\Omega$ ;  $\beta = \infty$ : 0.52 mA, 0 V, 0.25 V;  $\beta = 50$ : 0.48 mA,  $-0.07$  V, 0.35 V
- 6.101** 5.07 V, 1.27 mA to 2.48 mA; 620  $\Omega$ ; 0.91 mA to 1.5 mA
- 6.102** 2 V; 2.4 V; 1.2 mA
- 6.106** (a) 1.25 V; (b) 1.85 V
- 6.113**  $R_C = 3.3$  k $\Omega$ ;  $R_B = 120$  k $\Omega$ ; 0.56 mA, 0.85 V
- 6.117** (a) 9.5 k $\Omega$ ; (b) 12.5 k $\Omega$ ; 10 M $\Omega$ ; (b) 2 mA/V, 100 k $\Omega$ ; (c)  $-9.6$  V/V; (d) 0.946 V/V, 473  $\Omega$ ; (e) 0.6 V
- 6.120** (a) 11.5 k $\Omega$ ; (b) 12.5 k $\Omega$ ; (c)  $-31.7$  V/V
- 6.121** 27.5 k $\Omega$ ;  $-9.8$  V/V; 20.5 mV; 0.2 V
- 6.123** (a)  $\beta = 50$ : 0.78 mA, 0.78 mA, 1.48 V;  $\beta = 200$ : 1.54 mA, 1.54 V, 2.24 V; (b)  $\beta = 50$ : 21.3 k $\Omega$ ;  $\beta = 200$ : 50.9 k $\Omega$ ; (c)  $\beta = 50$ : 0.64 V/V;  $\beta = 200$ : 0.81 V/V
- 6.130**  $-27.5$  V/V; Comparing the results above to those of Problem 7.125, we see that raising the resistance values has indeed resulted in increasing the transmission from source to transistor base, from 0.371 V/V to 0.636 V/V. However, because IC has decreased and  $g_m$  has correspondingly decreased, the gain from base to collector has decreased by a larger factor (from 97.83 V/V to 43.2 V/V), with the result that the overall gain has in fact decreased (from 36.3 V/V to 27.5 V/V). Thus, this is not a successful strategy!
- 6.131**  $R_B = 91$  k $\Omega$ ;  $R_C = 22$  k $\Omega$ ; 0.2 mA;  $-176$  V/V,  $-29.7$  V/V
- 6.135** (a) 1.7 mA, 68.4 mA/V, 0.0145 k $\Omega$ , 1.46 k $\Omega$ ; (b) 148.3 k $\Omega$ , 0.93 V/V; (c) 18.21 k $\Omega$ , 0.64 V/V
- 6.136** (a) 0.1 mA, 5 mA, 1.5 V, 0.8 V; (b) 0.995 V/V, 101.5 k $\Omega$ ; (c) 456 k $\Omega$ , 0.9975 V/V; (d) 0.82 V/V; (e) 0.814 V/V

## Chapter 7

- 7.2 66 k $\Omega$ ; 6  $\mu$ m; 0.2 V; 40 k $\Omega$ ; +5  $\mu$ A
- 7.8 1.187 V; 0.113 V; 99.98  $\mu$ A; 0.9998 mA, -0.02%; 0.3 V
- 7.9 700  $\Omega$ , 5 A/A, 10 k $\Omega$ .
- 7.11 0.2 V; 100  $\mu$ A; 0.2 V; 27 k $\Omega$ ; 81.5  $\mu$ A; 100  $\mu$ A; 118.5  $\mu$ A; 137  $\mu$ A
- 7.14 0.1 mA, 10%
- 7.17 1.013 mA; 2.28 k $\Omega$ ; 2.7 V; +0.15 mA
- 7.18 (a)  $I = 0.4$  mA; (b)  $I = 0.04$  mA; (a) and (b):  $V_1 = -0.7$  V,  $V_2 = +2$  V,  $V_3 = +0.7$  V,  $V_4 = -0.7$  V,  $V_5 = -1.7$  V
- 7.21  $\frac{I_o}{I_{REF}} \simeq \frac{1}{1 + \frac{n+1}{\beta^2}}$ ; 44
- 7.23 20  $\mu$ m; 80  $\mu$ m; 0.8  $\mu$ m; -0.6%
- 7.24  $v_o/v_i = g_{m1}R_L (W_3/W_2)$
- 7.29 0.5  $\mu$ m; 12.5; 0.1 mA
- 7.34 (a) 0.2 mA; (b) 100 k $\Omega$ , 100 k $\Omega$ , 50 k $\Omega$ ; (c) 6.25 k $\Omega$ , 8 mA/V; (d) 6.25 k $\Omega$ , -400 V/V, 50 k $\Omega$
- 7.35  $I = 10$   $\mu$ A: 0.4 mA/V, 250 k $\Omega$ , 1 M $\Omega$ , 400 V/V;  $I = 100$   $\mu$ A: 4 mA/V, 25 k $\Omega$ , 100 k $\Omega$ , 400 V/V;  $I = 1$  mA: 40 mA/V, 2.5 k $\Omega$ , 10 k $\Omega$ , 400 V/V
- 7.36 40 V/V; 0.1 mA; 5  $\mu$ m
- 7.38 0.5 mA; 4 mA/V
- 7.40 2 mA/V; 13.5 k $\Omega$ ; 27 V/V; 14  $\mu$ m
- 7.42 0.146 mA
- 7.46 0.75 V; 17.4; 69.4; -14.5 V/V
- 7.47 (a) 0.95 V, 0.475  $\mu$ A, 2.4 V; (b) -86 V/V, 1.93 V, 22 mV; (c) 33.9 k $\Omega$
- 7.48 50  $\mu$ A; 4; 16, 16
- 7.49 (a) 0.125 mA, 0.125 mA; (b) -999 V/V; (c) -74.1 V/V, 13.3 k $\Omega$ ; (d) -29.6 V/V; (e) -0.5 V to +0.5 V
- 7.50 21 k $\Omega$ ; 0.976 A/A; 840 k $\Omega$ ; 20.5 V/V
- 7.52 252 k $\Omega$
- 7.54 1.4 k $\Omega$ ; 0.98 A/A; 10.2 M $\Omega$ ; 35.7 V/V
- 7.58 40 V/V; 0.6  $\mu$ m
- 7.62 -1600 V/V
- 7.64 0.32  $\mu$ m; 39.1; 0.7 V; 0.225 mA; 0.3 V
- 7.68 1 M $\Omega$
- 7.70 5 V; 1  $\mu$ m
- 7.74 0.2 V; 0.5 V to 0.8 V
- 7.78  $-10^5$  V/V
- 7.81 0.68 V; 1.1 M $\Omega$
- 7.83 0.56 V; 1.12 V; 0.72 V
- 7.88 1.5 V
- 7.93 (a) 58.5 k $\Omega$ ; (b) 79.9 M $\Omega$ ,

## Chapter 8

- 8.1** (a) 0.2 V, 0.6 V; (b) -0.6 V, 0.08 mA, 0.08 mA, +0.6 V, +0.6 V, 0 V; (c) -0.2 V, 0.08 mA, 0.08 mA, +0.6 V, +0.6 V, 0 V; (d) -0.7 V, 0.08 mA, 0.08 mA, +0.6 V, +0.6 V, 0 V; (e) 1.0 V; (f) -0.8 V, -0.2 V; (g) -0.2 V to 1.0 V
- 8.4**  $I = 0.25 \text{ mA}$ ;  $\frac{W}{L} = 10$
- 8.5** 0.25 V; 0.5 mA; 5 k $\Omega$ ; 40
- 8.6** 0.14 V; 0.25 mA; 4.4 k $\Omega$ ; 25.5
- 8.11** (a)  $0.1V_{OV}$ ; (b) 0 V,  $0.338V_{OV}$ ,  $0.05V_{OV}$ ,  $0.005V_{OV}$ ;  $1.072V_{OV}$
- 8.15** 0.212 V; 554.5  $\mu\text{A}$
- 8.16** (a)  $0.1V_{OV}$ ; (b) 0 V,  $0.338V_{OV}$ ,  $0.05V_{OV}$ ,  $0.005V_{OV}$ ;  $1.072V_{OV}$
- 8.19** (a) 0.426 mA/V; (b) 85  $\mu\text{A}$ ; (c) 2 V; (d) 0.1 V; (e) 2.11 V
- 8.21**  $2\times$
- 8.26**  $V_{E1} = V_{E2} = -1.66 \text{ V}$ ;  $V_{C1} = V_{C2} = +1.51 \text{ V}$
- 8.27** (a) -0.574 V, +0.4 V, +0.4 V; (b) -0.326 V to +0.674 V; (c) 5 mV
- 8.29** 8 mA/V; 40 k $\Omega$
- 8.32** Differential amplifier with a resistance  $R_e$  in each emitter;  $I = 0.5 \text{ mA}$ ;  $R_e = 1.9 \text{ k}\Omega$ ;  $R_C = 20 \text{ k}\Omega$
- 8.35** 16 V/V
- 8.36** 25 V/V; 101 k $\Omega$
- 8.41** (a)  $V_{CC} - (I/2)R_C$ ; (b) 2 V; (c) 0.4 mA, 5 k $\Omega$
- 8.44** 0.5 mA, 1.0 mA; 17.3 mV
- 8.47** (a) 0.2 mA, 15 k $\Omega$ , +1 V; (b) 50 k $\Omega$ ; (c)  $\pm 0.3 \text{ V}$ ; (d) 1.1 V
- 8.50** 400 V/V
- 8.55** 12 V/V;  $6 \times 10^{-4} \text{ V/V}$ ; 86 dB
- 8.57** (a) 20 V/V; (b) 0.23 V/V; (c) 86.5; (d)  $-0.023 \sin 2\pi \times 60t + 0.2 \sin 2\pi \times 1000t$ , V
- 8.61** (a) 0.94 V; (b) 107 k $\Omega$ ; (c) 0.93 V; (d) -2.26 V/V; (e) 0.12 V
- 8.65** (a) 40 V/V; (b)  $5 \times 10^{-3} \text{ V/V}$ , 78 dB; (c)  $1 \times 10^{-4} \text{ V/V}$ ; 112 dB
- 8.68** 1%
- 8.69**  $\frac{2}{3}I$  in  $Q_1$  and  $\frac{1}{3}I$  in  $Q_3$ ; 0.0125 V/V
- 8.72** 2.5 mV
- 8.76**  $I_{B\max} \simeq 2.5 \mu\text{A}$ ;  $I_{B\min} = 1 \mu\text{A}$ ;  $I_{OS\max} \simeq 1.5 \mu\text{A}$
- 8.78** Worst-case  $V_{os} = 14 \text{ mV}$   
If the three components are independent,  $V_{os} = 8.1 \text{ mV}$
- 8.81** 1.25 mV
- 8.84** 1.6 k $\Omega$ ; 0.8 k $\Omega$ ; 2 k $\Omega$
- 8.85** 10 V/V
- 8.86** 1.25 mA/V; 30 k $\Omega$ ; 30 k $\Omega$ ; 18.8 V/V
- 8.88** 1 mA/V; 75 k $\Omega$ ; 75 V/V; 75 k $\Omega$
- 8.91** (a) 17.8, 17.8, 71.1, 71.1; (b) 0.6  $\mu\text{m}$ ; (c) -0.4 V to +0.65 V; (d) 77 dB

- 8.92** 1 mA/V; 30 k $\Omega$ ; 30 V/V; 30 k $\Omega$ ; 0.984 k $\Omega$ ; 0.9836 A/A;  $5.56 \times 10^{-4}$  mA/V; 0.0167 V/V; 65.1 dB
- 8.93** 20 k $\Omega$ ; 40 V/V
- 8.98** (a) +4 V; (b) +2.5 V; (c) +1.4 V; (d) +1.1 V
- 8.103** 81 k $\Omega$
- 8.105** 120  $\mu$ A; 455 mV; 0.73 mV
- 8.107** 25 V/V; 20 k $\Omega$ ; 5000 A/A
- 8.109** (a) 0.52 mA, 1.04 mA, 2.1 mA, 0 V; (b) 4 k $\Omega$ , 65.5  $\Omega$ ; (c) 8770 V/V
- 8.111** (a)  $|V_{OV}|$  is reduced by a factor of 2 and  $g_m$  increases by a factor of 20; (b) Both increase by a factor of 20; (c) increases by a factor 2 (except for  $V_{OS}$  due to  $\Delta V_t$ ).
- 8.115**  $R_5$ ; 7.37 k $\Omega$ ; reduced by a factor of 2; reduce  $R_4$  to 1.085 k $\Omega$ .

## Chapter 9

- 9.1**  $g_m = 2.6$  mA/V;  $g_{mb} = 0.6$  mA/V;  $r_o = 50$  k $\Omega$ ;  $C_{gs} = 23.7$  fF;  $C_{gd} = 3.1$  fF;  $C_{sb} = 4.2$  fF;  $C_{db} = 3.4$  fF;  $f_T = 15.4$  GHz
- 9.2** 7.1 GHz
- 9.3**  $f_T = 353.7$  MHz;  $f_\beta = 3.54$  MHz
- 9.5**  $C_\pi = 0.54$  pF;  $g_m = 40$  mA/V
- 9.9** 265.3 MHz
- 9.14** -40 V/V; 34.6 MHz; 127.3 GHz
- 9.18** 61 pF; 522 kHz
- 9.19** -29.3 V/V; 988 kHz
- 9.20** 1 M $\Omega$
- 9.22** 3.18 MHz
- 9.27** -25 V/V; 49.7 MHz; 31.8 GHz
- 9.28** 31.83 fF; 286.5 fF; 20 MHz
- 9.30** -81.4 V/V; 21.4 MHz; 11.2 GHz
- 9.39**  $f_H = 52.2$  MHz;  $f_Z = 63.7$  GHz
- 9.40** -80 V/V; 10.1 pF; 788 kHz; 652 kHz; the second estimate is more appropriate as it takes  $C_L$  into account.
- 9.42** -143 V/V; 3.2 MHz; 2.47 MHz; the second estimate as it takes  $C_L$  into account.
- 9.44** -41.7 V/V; 140 kHz
- 9.46** 118 fF
- 9.49** -50 V/V; 479 kHz
- 9.52** -913 V/V; 5.76 MHz
- 9.53** 0.2 V; 0.2 mA; 289.4 MHz; 57.9 MHz; -99 V/V; 2.9 MHz; 287.1 MHz
- 9.57** 11.1 fF
- 9.64** 0.9 V/V; 200  $\Omega$ ; 398 MHz; 33.4 MHz, 90.7 MHz; 31.6 MHz
- 9.66** 0.96 V/V; 2 GHz; 740 MHz, 4.6 GHz; 740 MHz
- 9.69** 27 k $\Omega$ ; 884 kHz; 0.33 mA/V

- 9.71** 1.59 MHz  
**9.72** 50 V/V; 15.9 MHz; 1.59 GHz; 3.18 GHz  
**9.74**  $f_{P1} = 159 \text{ kHz}$ ;  $f_{P2} = 2 \text{ MHz}$   
**9.79** (a)  $-100 \text{ V/V}$ , 603 kHz, 60.3 MHz; (b)  $-50 \text{ V/V}$ , 1.02 MHz, 51.2 MHz  
**9.82**  $V_o/V_{\text{sig}} = 25 \text{ V/V}$ ;  $f_{P1} = 637 \text{ kHz}$ ,  $f_{P2} = 6.37 \text{ MHz}$ ;  $f_H = 637 \text{ kHz}$   
**9.86** (a)  $2.5 \text{ M}\Omega$ ,  $-4000 \text{ V/V}$ ; 107.6 MHz  
**9.88** 50 V/V; 4.6 MHz  
**9.89** (a) 2500 V/V; (b) 9.1 MHz  
**9.93**  $-15.8 \text{ V/V}$ ; 1.9 Hz; 87.5 Hz; 8 Hz; 10.8 Hz; 87.5 Hz  
**9.95**  $C_E = 5 \text{ }\mu\text{F}$ ;  $C_{C1} = 0.5 \text{ }\mu\text{F}$ ;  $C_{C2} = 0.5 \text{ }\mu\text{F}$ ; 92.2 Hz; 6  $\mu\text{F}$   
**9.98** 0.8  $\mu\text{F}$   
**9.99** 10  $\mu\text{F}$ ; 88.4 Hz; 8.84 Hz  
**9.103** 141.4

## Chapter 10

- 10.1**  $4.9 \times 10^{-3}$ ; 169.5;  $-15.3\%$   
**10.2** 0.01; 100;  $10^4$   
**10.5** 0.1; 990; 9.9  
**10.6** 500 V/V; 0.198 V/V  
**10.8** 2500 V/V; 0.0196 V/V; 49; 50 V/V; 34 dB  
**10.10** 99; 4  
**10.12** 1000 V/V; 0.099 V/V  
**10.13** 1135; 0.0395  
**10.15** 100 kHz; 0.099 V/V  
**10.21**  $A_{Mf} = \frac{A_M}{1 + A_M\beta}$   
 $\omega_{Lf} = \frac{\omega L}{1 + A_M\beta}$   
 Both the midband gain and the 3-dB frequency are lowered by the amount of feedback,  $(1 + A_M\beta)$ .  
**10.22** Three stages each with a closed-loop gain of 10 V/V and  $\beta = 0.099 \text{ V/V}$   
**10.25** (a) 0.9 k $\Omega$ ; (b) 31.33, 9.7 V/V,  $-3\%$ , make  $R_F = 933 \text{ }\Omega$   
**10.27** 90 k $\Omega$ ; 100; 9.9 V/V; 91 k $\Omega$   
**10.30** (a)  $1 + \frac{R_2}{R_1} = 11 \text{ V/V}$ ; (b) 0.1 mA, 0.3 mA, +7.7 V; (c) 23.2; (d) 10.55 V/V  
**10.32** 9.9 V/V; 202 k $\Omega$ ; 19.8  $\Omega$   
**10.34** (a)  $1 + \frac{R_2}{R_1} = 11 \text{ V/V}$ ; (b) 0.1 mA, 0.3 mA, +7.7 V; (c)  $A = \beta \frac{R_L \parallel (R_1 + R_2)}{R_s + r_{e1} + \frac{R_1 \parallel R_2}{\beta + 1}} =$   
 $255.3 \text{ V/V}$ ,  $R_i = R_s + r_{e1} + \frac{R_1 \parallel R_2}{\beta + 1} = 0.359 \text{ k}\Omega$ ,  $R_o = R_L \parallel (R_1 + R_2) = 0.917 \text{ k}\Omega$ ; (d)

- $$\beta = \frac{R_1}{R_1 + R_2} = 1/11; \text{ (e) } 10.55 \text{ V/V, } 8.59 \text{ k}\Omega, 39.4 \text{ }\Omega, 4\% \text{ less}$$
- 10.36** (b) 0 V, 0 V; (c)  $A = g_{m1,2} (r_{o2} \| r_{o4} \| R_{22}) = 47.62 \text{ V/V}$ ; (d) 821 k $\Omega$ , 179 k $\Omega$ ; (e) 5 k $\Omega$ ; (f) 3.33 V/V; (g) 3.33 V/V
- 10.39** 100 V/V; 1.001 M $\Omega$
- 10.42** (b) 80 k $\Omega$ ; (d) 928.5 V/V; (e) 0.2 V/V, 186.7; (f) 4.97 V/V; (g) 19.98 M $\Omega$ ; (h) 2.66  $\Omega$ ; (i) 18.67 kHz; (j)  $-0.47\%$
- 10.44** 0.1 V/mA; 9.9 mA/V; 1.01 M $\Omega$ ; 0.99  $\Omega$
- 10.45** (a)  $1/R_F$ ; (b) 100  $\Omega$ ; (c)  $\frac{\mu R_F}{\frac{1}{g_m} + R_F}$ ; (d) 166.7, 1667 mA/V; 9.94 mA/V
- 10.48** 4.87 mA/V; 1.11 M $\Omega$ ; 4.1 M $\Omega$
- 10.49** 100  $\Omega$ ; 497 V/V; 9.94 mA/V
- 10.51** (a) 0 V, +0.6 V, +0.6 V; (b)  $1/R_F$ , 0.1 mA/V; (c) 0.099 mA/V; (d) 202 M $\Omega$ ; (e) 0.99 V/V, 1.26  $\Omega$
- 10.53** (a)  $A_f|_{\text{ideal}} = \frac{1}{R_{S1}} + \frac{1}{R_{S2}} + \frac{R_F}{R_{S1}R_{S2}}$ , 800  $\Omega$ ; (b) 0.01 V/mA, 90  $\Omega$ , 90  $\Omega$ ; (c) 5951 mA/V; (d) 60.51, 98.3 mA/V, 1.7% lower, increase  $R_F$ ; (e) 29.1 k $\Omega$ , 1.76 M $\Omega$
- 10.54** (a) 800  $\Omega$ ; (b) 0.01 V/mA; (c) 90  $\Omega$ , 90  $\Omega$ ; (d) 1.687  $\mu$  mA/V; (e) 5868 V/V; (f) 99 mA/V; (g) 10 M $\Omega$ , 2.37 M $\Omega$
- 10.60** 0.94 V/mA; 28.3  $\Omega$ ; 21.1  $\Omega$
- 10.64** 10 k $\Omega$ ;  $-9.52 \text{ k}\Omega$ ; 11.9  $\Omega$ ; 244  $\Omega$
- 10.69** (a) 100  $\mu$ A, 60 k $\Omega$ , 30 k $\Omega$ , 12.5 12.5, (b)  $-R_2/R_s$ ,  $-1/R_2$ ; (c) 6 k $\Omega$ ; (d)  $-404 \text{ k}\Omega$ , 4.62 k $\Omega$ , 875  $\Omega$ ; (e)  $-4.65 \text{ V/V}$ ; (f) 337  $\Omega$ , 61  $\Omega$
- 10.72** (a) +0.7 V; (b)  $-5 \text{ A/A}$ ,  $-0.2 \text{ A/A}$ ; (c) 2 mA/V, 50 k $\Omega$ ; (d) 17.5 k $\Omega$ ,  $-525.8 \text{ A/A}$ , 332.8 k $\Omega$ ; (e) 105.16,  $-4.95 \text{ A/A}$ ; (f) 164.8  $\Omega$ , 35.3 M $\Omega$
- 10.79** (a) 0.865 mA, 0.77 mA; (c) 3.94 A/A, 3.47 A/A; (d)  $-0.254 \text{ A/A}$ ; (e)  $-216.3 \text{ A/A}$ , 1.68 k $\Omega$ , 2.67 k $\Omega$ ; (e) 54.9, 55.9,  $-3.87 \text{ A/A}$ , 30.1  $\Omega$ , 149.2 k $\Omega$ ; (g) 30.2  $\Omega$ ,  $-3.41 \text{ A/A}$ , 9.17 M $\Omega$
- 10.80**  $10^4 \text{ rad/s}$ ; 0.02; 50
- 10.82**  $1.095 \times 10^5 \text{ rad/s}$ ;  $2.42 \times 10^{-3}$
- 10.86** 0.099; 198 kHz; 140.7 kHz
- 10.88** 2; 173.2 kHz
- 10.89**  $3.085 \times 10^3 \text{ Hz}$ ;  $18.15^\circ$ ;  $10^{-3}$ ; 60 dB
- 10.93**  $2.4 \times 10^4 \text{ V/V}$  or 87.6 dB;  $9.09 \times 10^3 \text{ V/V}$  or 79.2 dB.
- 10.95** (a) 10 kHz; 100 Hz
- 10.97** 100 Hz

## Chapter 11

- 11.2** 163  $\Omega$ ; The incremental gain changes by  $0.998 - 0.966 = 0.032$ , or about 3% over the range of  $v_o$ .

- 11.4**  $\hat{V}; \hat{V}/R_L; 25\%$   
**11.5**  $-1.1 \text{ V} < v_o < 1.91 \text{ V}; -1.6 \text{ V} < v_i < 3 \text{ V};$   
**11.8**  $V_{CC}I$   
**11.10**  $5 \text{ V}$   
**11.12**  $10 \text{ V}; 6.37 \text{ V}; 6.85 \Omega, 7.3 \text{ W}; 9.62 \Omega, 1.3 \text{ W}$   
**11.14**  $4.5 \text{ V}; 6.4\%; 625 \Omega$   
**11.15**  $33 \text{ V}; 3.54 \text{ A}; 74.4 \text{ W}; 67.2\%; 13.8 \text{ W}$   
**11.18**  $1.266 \text{ V}; 12.5 \Omega; 0.889 \text{ V/V}; 0.998 \text{ V/V}$   
**11.21**  $2.15 \text{ mA}$   
**11.23**  $1 \text{ mA}; -1.06 \text{ V}; +4 \text{ V}; -6 \text{ V}$   
**11.24**  $7.8$   
**11.28** (a)  $0.99 \text{ mA}, 0 \text{ A}, 0 \text{ V};$  (b)  $1.15 \text{ M}\Omega, 0.89 \text{ V/V}, 12.6 \Omega$   
**11.31**  $-g_{m3}\beta R_L$   
**11.34** (a)  $1.365 \text{ k}\Omega, 1.365 \text{ k}\Omega, 1.365 \text{ V};$  (b)  $1.420;$  (c)  $1.512 \text{ V};$  (d)  $1.641 \text{ V}$   
**11.38** (a)  $0.0164 \text{ mA}, 1.64 \text{ mA};$  (b)  $32.8 v_i, -66.2 \text{ V/V};$  (c)  $27.2 \text{ k}\Omega$   
**11.41** (a)  $30.5 \text{ V};$  (b)  $246.8/R_L; 881.8/R_L$   
**11.43**  $6.5 \Omega; 487.5 \text{ mV}; 2.9 \mu\text{A}$   
**11.45**  $35 \text{ mA}; 5 \text{ mA}$   
**11.46**  $\pm 2.05 \text{ V}$   
**11.47**  $5\Omega$   
**11.50** (a)  $533.3; 1333.3;$  (b)  $10 \text{ V/V};$  (c)  $5\%;$  (d)  $\pm 1.85 \text{ V};$  (e)  $+0.3 \text{ V}; -0.3 \text{ V};$  (f)  $-1.77 \text{ V} \leq v_o \leq +1.77 \text{ V}$   
**11.52**  $+3 \text{ V}; -3 \text{ V}$   
**11.54**  $2 \text{ W}; +5 \text{ V}; 3 \text{ W}; +5 \text{ V}; 600 \text{ mA}; 30 \text{ V}$

## Chapter 12

- 12.1**  $-0.8 \text{ V} \leq V_{ICM} \leq +0.2 \text{ V}; -0.8 \text{ V} \leq v_o \leq +0.8 \text{ V}$   
**12.3**  $0.15 \text{ V}$   
**12.5**  $1.06 \text{ pF}, 318.3 \text{ MHz}, 360 \text{ MHz}$   
**12.8**  $5.67 \text{ MHz}$   
**12.9**  $180 \text{ Hz}; 0.7 \text{ pF}$   
**12.11** (a)  $2 \text{ pF};$  (b)  $1.51 \text{ pF}$   
**12.15**  $3.2 \text{ pF}; 30 \text{ MHz}$   
**12.18**  $11.4 \text{ MHz}$   
**12.19**  $636 \text{ k}\Omega$   
**12.21**  $159.2 \text{ kHz}; 10^8 \text{ rad/s}$  or  $15.9 \text{ MHz}$   
**12.23** (a)  $0.16 \text{ V};$  (b)  $2 \text{ pF};$  (c)  $78.1$   
**12.25** (b)  $0.45 \mu\text{m}$   
**12.27**  $+0.3 \text{ V}; +0.45 \text{ V}; -0.45 \text{ V}; -0.3 \text{ V} \leq V_{ICM} \leq +1.25 \text{ V}; -0.3 \text{ V} \leq v_o \leq +0.7 \text{ V}$

- 12.29 (a)  $-0.25 \text{ V} \leq V_{ICM} + 1.3 \text{ V}$ ; (b)  $-1.3 \text{ V} \leq V_{ICM} + 0.25 \text{ V}$ ; (c)  $-0.25 \text{ V} \leq V_{ICM} + 0.25 \text{ V}$ ; (d)  $-1.3 \text{ V} \leq V_{ICM} + 1.3 \text{ V}$
- 12.32  $I/C_L$
- 12.37  $0.75 \text{ V}$ ,  $2 V_{OV}$ ,  $14.8 \text{ M}\Omega$
- 12.38  $0.176C_L$
- 12.41  $A_7 = 3A_3$ ;  $A_8 = 10A_3$ ;  $R_3 = R_4 = 6.67 \text{ k}\Omega$ ;  $R_7 = 2.22 \text{ k}\Omega$ ;  $R_8 = 667\Omega$
- 12.44  $12.5 \text{ k}\Omega$ ;  $0.8 \text{ V}$  to  $3.35 \text{ V}$ ;  $100 \text{ k}\Omega$ ;  $10 \mu\text{A}$ ,  $50 \text{ k}\Omega$
- 12.46 2
- 12.47  $50 \mu\text{A}$
- 12.52  $1.8 \text{ k}\Omega$
- 12.54 (a)  $0.1 \text{ V} \leq V_{ICM} \leq 2.2 \text{ V}$ ; (b)  $0.8 \text{ V} \leq V_{ICM} \leq 2.9 \text{ V}$
- 12.55  $125 \text{ k}\Omega$ ;  $95.4 \text{ V/V}$
- 12.57 (b)  $367.3$ ; (c)  $6.75 \text{ mV}$
- 12.61  $152 \leq \beta_N \leq 165$
- 12.63  $105.3 \text{ dB}$
- 12.64  $R = 18.2 \text{ k}\Omega$ ;  $15.55 \text{ M}\Omega$
- 12.67 (a)  $0.1 \text{ V} \leq v_O \leq 2.9 \text{ V}$ ; (b)  $20 \text{ k}\Omega$ ; (c)  $0.2 \Omega$ ; (d)  $12.3 \text{ mA}$ ;  $0.3 \text{ mA}$ ;  $1.6 \text{ k}\Omega$ ; (e)  $12.3 \text{ mA}$ ;  $0.3 \text{ mA}$ ;  $2.4 \text{ k}\Omega$
- 12.68  $10.6 \mu\text{A}$ ; minimum current is  $0.3 \text{ mA}$

## Chapter 13

- 13.2  $1 \text{ V/V}$ ;  $0.977 \text{ V/V}$ ;  $0.001 \text{ V/V}$
- 13.3  $0.42 \text{ dB}$ ,  $66 \text{ dB}$ ,  $1.25$
- 13.6 (a)  $0.995 \text{ V}$ ,  $-5.7^\circ$ ; (b)  $0.707$ ,  $-45^\circ$ ; (c)  $0.1 \text{ V}$ ,  $-84.3^\circ$ ; (d)  $0.01 \text{ V}$ ,  $-89.4^\circ$
- 13.8  $0.765 \text{ rad/s}$ ,  $3.85 \text{ rad/s}$ ,  $5$
- 13.10 3; low-pass;  $\frac{0.3125(s^2 + 4)}{(s + 1)(s^2 + s + 1.25)}$
- 13.12 4;  $\frac{4.512 \times 10^5 s^2}{(s^2 + s 10^3 + 10^6)(s^2 + s 10^2 + 1.44 \times 10^6)}$
- 13.15  $10^9/(s^2 + s 1.414 \times 10^4 + 10^8)$
- 13.18  $\frac{0.64(s^2 + 1.5625 \times 10^8)}{s^2 + 5 \times 10^3 s + 10^8}$ ;  $0.64$
- 13.20  $T(s) = 0.2656 (s^2 + 4)/(s^2 + 0.5s + 1.0625)$ ;  $0.2656$
- 13.22  $1/(s^3 + 2s^2 + 3s + 2)$ ; All zeros at  $s = \infty$ ; Poles:  $s = -1$ ,  $s = -0.5 \pm j1.323$
- 13.25  $\frac{10^8}{s^2 + 5000s + 10^8}$ ;  $9354 \text{ rad/s}$ ;  $2,066$
- 13.26 (a)  $1 \text{ rad/s}$ ,  $1/\sqrt{2}$ ,  $12.3 \text{ dB}$ ; (b)  $0.8427 \text{ rad/s}$ ,  $1.3$ ,  $17 \text{ dB}$
- 13.28  $\frac{s^2}{s^2 + s + 1}$ ;  $1 \text{ rad/s}$ ;  $1$

**13.32** 35.7 dB

**13.33**  $1.234 \times 10^3(0.309 \pm j0.951)$ ,  $1.234 \times 10^3(-0.809 \pm j0.588)$ ,  $-1.234 \times 10^3$

**13.34**  $N = 4$ ;  $2\pi \times 10^4(-0.383 \pm j0.924)$ ,  $2\pi \times 10^4(-0.924 \pm j0.383)$ ;  $\omega_0^4/(s^2 + 0.765\omega_0s + \omega_0^2) \times (s^2 + 1.848\omega_0s + \omega_0^2)$  where  $\omega_0 = 2\pi \times 10^4$  rad/s; 38.2 dB

**13.37** 45.3 dB

**13.38** (a) 10, 4 dB;

$$(b) p_{1,10} = \omega_p(-0.0224 \pm j0.9978),$$

$$p_{2,9} = \omega_p(-0.0651 \pm j0.9001),$$

$$p_{3,8} = \omega_p(-0.1013 \pm j0.7143),$$

$$p_{4,7} = \omega_p(-0.1277 \pm j0.4586),$$

$$p_{5,6} = \omega_p(-0.1415 \pm j0.1580);$$

$$\frac{7.60 \times 10^{40}}{(s^2 + s 0.0448 \omega_p + 0.9961 \omega_p^2)(s^2 + s 0.1302 \omega_p + 0.8144 \omega_p^2)} \times \frac{1}{(s^2 + s 0.2026 \omega_p + 0.5205 \omega_p^2)(s^2 + s 0.2554 \omega_p + 0.2266 \omega_p^2)} \times \frac{1}{(s^2 + s 0.2830 \omega_p + 0.0450 \omega_p^2)}$$

**13.39** 7; 23.15 dB, 0.25 dB

**13.41** Peaks:  $0.95 \omega_p$ ,  $0.59 \omega_p$ , 0; Valleys:  $\omega_p$ ,  $0.81 \omega_p$ ,  $0.31 \omega_p$

**13.48** (a)  $-0.5\%$ ; (b)  $-0.5\%$ ; (c) no change

**13.49** (a)  $C_1/(C_1 + C_2)$ ,  $C_1/(C_1 + C_2)$ , no zeros; (b) 0,  $C_1/(C_1 + C_2)$ , zero at  $s = 0$ ; (c)  $L_2/(L_1 + L_2)$ ,  $L_2/(L_1 + L_2)$ , no zeros; (d) 0,  $L_2/(L_1 + L_2)$ , zero at  $s = 0$

$$\mathbf{13.51} \quad V_o = \frac{s^2 V_y + s \left( \frac{\omega_0}{Q} \right) V_z + \omega_0^2 V_x}{s^2 + s \left( \frac{\omega_0}{Q} \right) + \omega_0^2}$$

**13.56**  $R = 2 \text{ k}\Omega$ ,  $C = 796 \text{ pF}$ ,  $R_6 = 200 \text{ k}\Omega$

$$\mathbf{13.59} \quad \frac{V_o}{V_i} = \frac{K R_2 / C_4 C_6 R_1 R_3 R_5}{s^2 + s \frac{1}{C_6 R_6} + \frac{R_2}{C_4 C_6 R_1 R_3 R_5}}$$

$$\mathbf{13.60} \quad (a) T(s) = \frac{0.4508 \times 10^5 (s^2 + 1.6996 \times 10^{10})}{(s + 0.7294 \times 10^5)(s^2 + s 0.2786 \times 10^5 + 1.0504 \times 10^{10})}$$

(b) First-order section:  $R_1 = R_2 = 13.71 \text{ k}\Omega$ ,  $C = 1 \text{ nF}$ , Second-order section:  $R_1 = R_2 = R_3 = R_5 = 9.76 \text{ k}\Omega$ ,  $C_{61} = 618 \text{ pF}$ ,  $C_{62} = 382 \text{ pF}$ ,  $R_6 = 35.9 \text{ k}\Omega$ ,  $K = 1$

**13.63**  $R = 1/\omega_0 C$ ;  $R_1 = \infty$ ,  $C_1 = GC$ ,  $R_2 = \left( \frac{R}{G} \right) \left( \frac{\omega_0}{\omega_n} \right)^2$ ,  $R_3 = \infty$

$$\mathbf{13.64} \quad \frac{V_o}{V_i} = \frac{s^2 \left( \frac{C_1}{C} \right) + s \frac{1}{C} \left( \frac{1}{R_1} - \frac{r}{RR_3} \right) + \frac{1}{C^2 RR_2}}{s^2 + s \frac{1}{QCR} + \frac{1}{C^2 R^2}}$$

**13.72** Second-order section:  $R_1 = R_2 = 10 \text{ k}\Omega$ ,  $C_3 = 492 \text{ pF}$ ,  $C_4 = 5.15 \text{ nF}$ ; Second order section:  $R_1 = R_2 = 10 \text{ k}\Omega$ ,  $C_3 = 1.29 \text{ nF}$ ,  $C_4 = 1.97 \text{ nF}$ ; First-order section:  $R_1 = R_2 = 10 \text{ k}\Omega$ ,  $C = 1.59 \text{ nF}$

- 13.73 100 M $\Omega$ ; 20 M $\Omega$ ; 10 M $\Omega$ ; 2 M $\Omega$ ; 1 M $\Omega$   
 13.78 (a) 100 pF; (b) 50 k $\Omega$ ; (c) 0.001  
 13.80 0.125%; 0.042%  
 13.82  $\omega_0$ ; 1/A  
 13.85 0.6 mA/V; 15.92 MHz  
 13.87  $s^2 + s \frac{1}{CR} \left(2 - \frac{r_2}{r_1}\right) + \frac{1}{C^2 R^2}$ ; 2; 1/CR  
 13.89 2.55 V  
 13.93 3.36 nF, 560 k $\Omega$   
 13.94  $C = 1.59$  nF;  $R_f$  slightly smaller than 20 k $\Omega$ ;  $R_3 = 2.74$  k $\Omega$ ;  $R_4 = 10$  k $\Omega$   
 13.96  $\omega_0 = \frac{0.925}{CR}$   
 13.99 7.88 V  
 13.100  $C = 1.59$  nF; 8.6 kHz; change the shunt resistor to 7.5 k $\Omega$  and  $R_2/R_1$  to 2.35.  
 13.107  $j\omega[-\omega^2 LC_1 C_2 + (C_1 + C_2)] + \left(g_m + \frac{1}{R_L} - \omega^2 \frac{LC_2}{R_L}\right) = 0$ ;  

$$\omega_0 = 1/\sqrt{L\left(\frac{C_1 C_2}{C_1 + C_2}\right)}; g_m R_L = \frac{C_2}{C_1}$$
  
 13.108  $L_1 = 2.41$   $\mu$ H;  $L_2 = 0.12$   $\mu$ H  
 13.109 2.0165 MHz to 2.0173 MHz, an 800 Hz range.  
 13.116 (a) Output will be either +12 V or -12 V; (b) The output is a symmetric square wave ( $\pm 12$  V) of frequency  $f$  and it lags the sine wave by an angle of 65.4 $^\circ$ ; 0.1 V.  
 13.117 1989 Hz  
 13.119 (a)  $V_{TH} = \left(\frac{L_+}{R_2} + \frac{V}{R_3}\right) (R_1 \parallel R_2 \parallel R_3)$ ;  $V_{TL} = \left(\frac{L_-}{R_2} + \frac{V}{R_3}\right) (R_1 \parallel R_2 \parallel R_3)$ ;  
 (b)  $R_2 = 656.7$  k $\Omega$ ,  $R_3 = 19.7$  k $\Omega$

## Chapter 14

- 14.1 (a) 2.18 k $\Omega$ ; (b) 5.40 k $\Omega$ ; (c) 3.71  
 14.6 (a) 6.0 (b) 1.67 k $\Omega$   
 14.18  $V_M = V_{IL} = V_{IH} = 0.9$  V;  $V_{OL} = 0$  V;  $V_{OH} = 1.8$  V;  $NM_L = NM_H = 0.9$  V; gain =  $\infty$   
 14.19  $V_{DD} = 1.0$  V;  $R_D = 31.6$  k $\Omega$ ;  $W/L = 1.7$ ;  $P_D$  (high output) = 30  $\mu$ W;  $P_D$  (low output) = 0  
 14.22  $NM_H = 0.5$  V;  $NM_L = 0.4$  V  
 14.23  $NM_H = 0.2V_{DD}$ ;  $NM_L = 0.3V_{DD}$ ; transition region width = 0.2  $V_{DD}$ ;  $V_{DD} = 1.25$  V  
 14.26  $V_{DD} = 1.2$  V;  $R_D = 27.6$  k $\Omega$ ;  $W/L = 2.1$ ;  $V_{IL} = 0.435$  V;  $V_M = 0.6$  V;  $V_{IH} = 0.7$  V;  $NM_L = 0.385$  V;  $NM_H = 0.5$  V  
 14.32 3.5 mV; 15.4 mV  
 14.33 135  
 14.34 (a) 84 nm (b)  $V_{OH} = 0.9$  V;  $V_{OL} = 0$  V;  $V_{IH} = 0.49$  V;  $V_{IL} = NM_H = NM_L = 0.41$  V  
 (c)  $r_{DSP} = r_{DSN} = 1.11$  k $\Omega$  (d)  $r = 0.816$ ;  $V_M = 0.43$  V

## Chapter 15

- 15.4** (a)  $V_{OL} = 0$  V;  $V_{OH} = 1.2$  V;  $NM_L = NM_H = 0.6$  V (b)  $t_{PHL} = 138$  ps;  $t_{THL} = 440$  ps  
(c)  $t_{PLH} = 138$  ps;  $t_{TLH} = 440$  ps
- 15.6** 293.3 ps
- 15.7**  $t_{PLH} = 27.6$  ps;  $t_{PHL} = 13.8$  ps;  $t_p = 20.7$  ps
- 15.9** (a) 475 ps (b) 400 ps;  $t_p = 175$  ps
- 15.10**  $(W/L)_n \geq 1.95$ ;  $(W/L)_p \geq 7.8$
- 15.13**  $t_{PHL} = 34.4$  ps;  $t_{PLH} = 42.6$  ps;  $t_p = 38.5$  ps;  $f_{max} = 13$  GHz
- 15.15**  $t_{PHL} = t_{PLH} = t_p = 7.7$  ps; 3.16 fF
- 15.17**  $S = 3$ . This is the factor by which  $(W/L)_n$  and  $(W/L)_p$  must be scaled. The inverter area will be increased by the same ratio, that is, 3.
- 15.23** (a) 0.54 V (b) 0.47 V
- 15.25** (a)  $x = 6.32$ ;  $t_p = 25.3$  CR (b)  $n = 7$ ;  $x = 2.87$ ;  $t_p = 20.1$  CR
- 15.28** 0.36 pF
- 15.31** 0.188 pJ
- 15.35** (a) 0.184 to 0.216 mA (b) 46.3 to 54.3 ps

## Chapter 16

- 16.2** (a)  $V_{DD}$  (b)  $|V_m|$  (c) 178 ps
- 16.4** 0.834 V
- 16.6** 25.8 ps
- 16.8**  $V_{OH} = 0.59$  V;  $V_{OL} = 0$  V;  $i_{DP}(V_{OH}) = 1.08$   $\mu$ A;  $t_{PLH} = 51.6$  ps;  $t_{PHL} = 27.0$  ps
- 16.11** 64.3 ps
- 16.19**  $V_M = 0.46$  V;  $(W/L)_{5-8} = 1.42$
- 16.23** (a) (1.64, 0.385) (b) (3, 0.5) (c) (3.69, 0.538)
- 16.26** 1024 cells; 10 address rows; 12 bits
- 16.27** 4.5
- 16.28**  $(W/L)_5 / (W/L)_1 \leq 0.397$ ;  $W_5 = 65$  nm;  $W_1 = 164$  nm
- 16.31** (a) 3 (b) 4.93 ns (c) 3.33 ns
- 16.33**  $(W/L)_p \leq 3(W/L)_a$
- 16.37** 222 ps; 200 MHz
- 16.41** 10 address bits; 1024 output lines; 20 input lines; 11,264 transistors
- 16.43** 10 address bits; 10 levels of pass gates; 2046 transistors