

Microelectronic Circuits International 8th Edition


A. Sedra, K.C. Smith
T. Chan Carusone, V. Gaudet

*Spice Problems Solutions
Chapter 9*


*Prepared by: Nijwm Wary
2019*

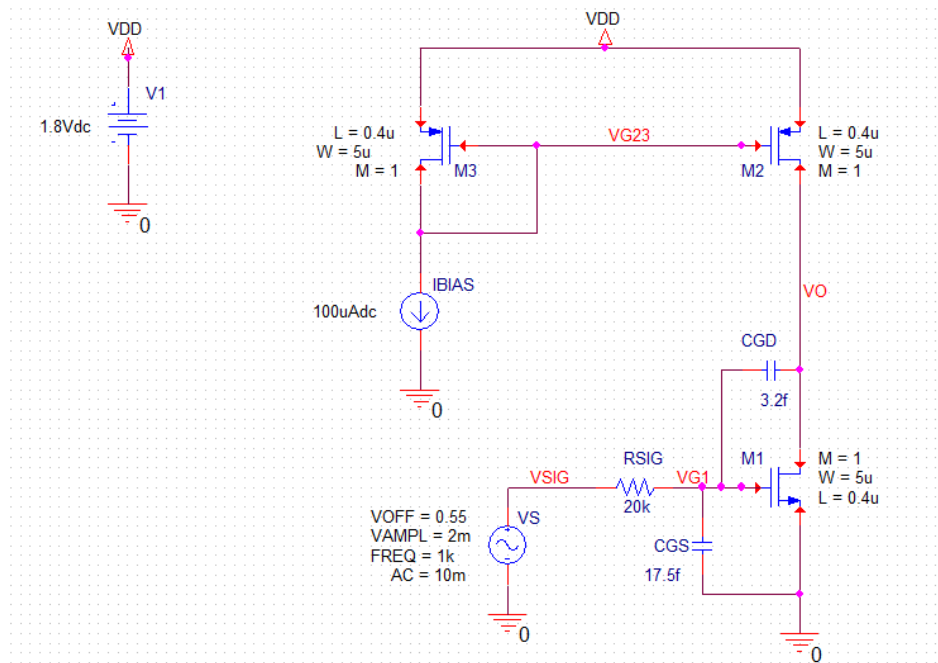Problem: 9.27

- The schematic for this problem is shown below.



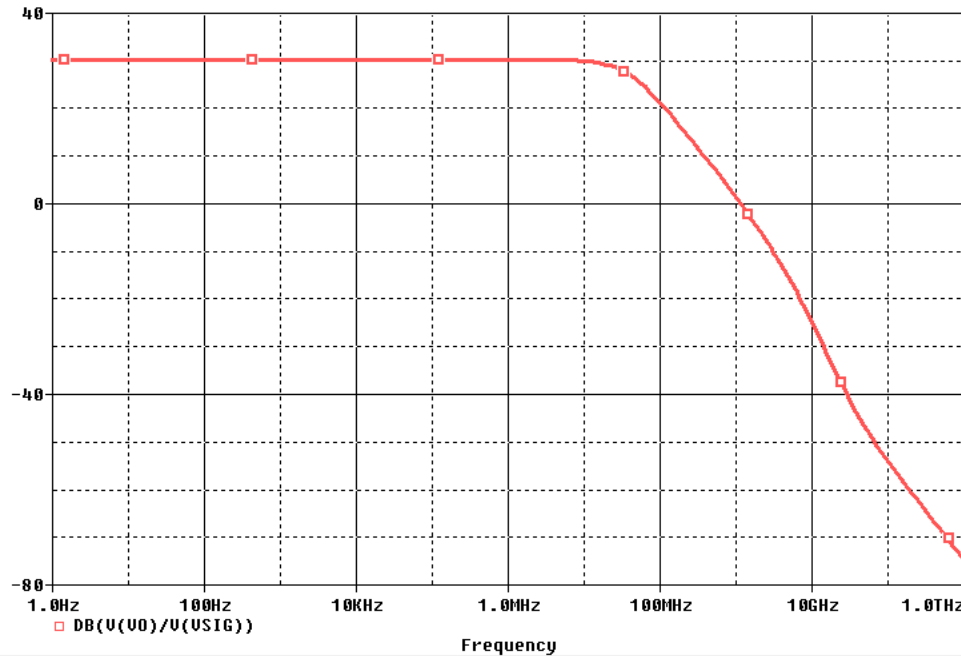- Note that external capacitances are added to match the transistor capacitances given in the problem. The parasitic capacitances from the device are $CGS=12.5fF$ and $CGD=1.8fF$.
- Run the netlist and perform AC analysis and plot $DB(V(VO)/V(VSIG))$.



4. The two frequencies are $f_H=38$ MHz and $f_Z=40$ GHz.

Netlist:

Copy the netlist given below and paste it into a text file and save it with *.cir extension.

```


*****Problem: P10_22 *****
***** Main circuit begins here*****
IBIAS          VG23 0 DC 100uAdc
RSIG           VSIG VG1 20k TC=0,0
VS             VSIG 0 AC 10m
+SIN 0.58 2m 1k 0 0 0
V1             VDD 0 1.8Vdc
M1             VO VG1 0 0 NMOS0P18
+ L=0.4u
+ W=5u
+ M=1
M2             VO VG23 VDD VDD PMOS0P18
+ L=0.4u
+ W=5u
+ M=1
M3             VG23 VG23 VDD VDD PMOS0P18
+ L=0.4u
+ W=5u
+ M=1
CGS            0 VG1 17.5f
CGD            VO VG1 3.2f
***** Main circuit ends here*****
***** PMOS model begins here *****
.model PMOS0P18 PMOS(Level=1 VTO=-0.4 GAMMA=0.3 PHI=0.8
+ LD=0 WD=0 UO=118 LAMBDA=0.2 TOX=4.08E-9 PB=0.9 CJ=1E-3
+ CJSW=2.04E-10 MJ=0.45 MJSW=0.29 CGDO=3.43E-10 JS=4.0E-7 CGBO=3.5E-10
+ CGSO=3.43E-10)
***** PMOS model ends here *****
***** NMOS model begins here *****
.model NMOS0P18 NMOS(Level=1 VTO=0.4 GAMMA=0.3 PHI=0.84
+ LD=0 WD=0 UO=473 LAMBDA=0.2 TOX=4.08E-9 PB=0.9 CJ=1.6E-3
+ CJSW=2.04E-10 MJ=0.5 MJSW=0.11 CGDO=3.67E-10 JS=8.38E-6 CGBO=3.8E-10
+ CGSO=3.67E-10)
***** NMOS model ends here *****

***** Analysis begins here*****
.OP
.AC DEC 20 1 1T
.PROBE
.END
***** Analysis ends here*****


```

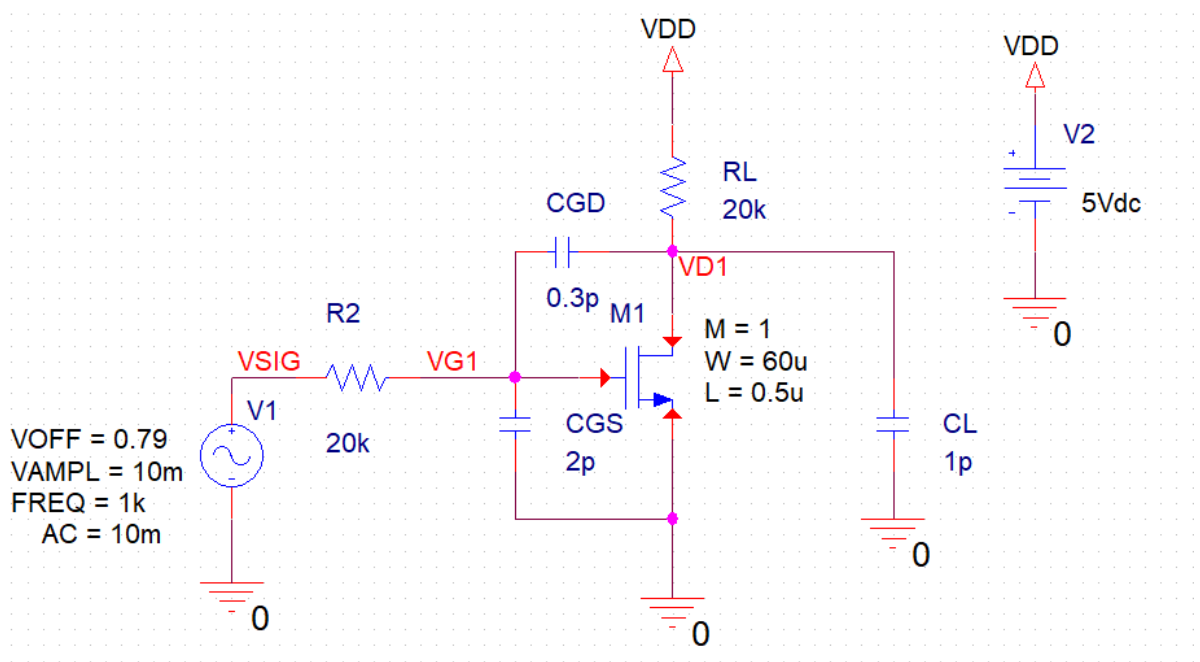Problem: 9.59


- The schematic for part (a) of this problem is shown below.



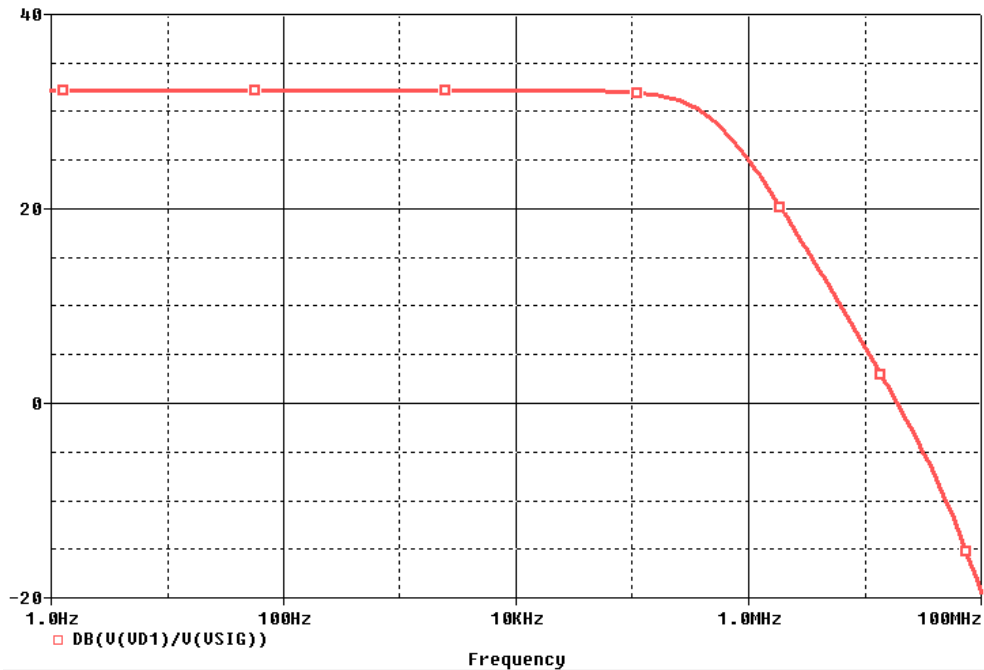
- For the transistor models used, $k'_n = 167 \mu\text{A}/\text{V}^2$. So, the W/L is 120 to get the specified g_m .
- Run AC simulation and plot $\text{DB}(V(\text{VD1})/V(\text{VSIG}))$. The gain is 40.55 V/V. The unity-gain frequency is at 19.27 MHz.



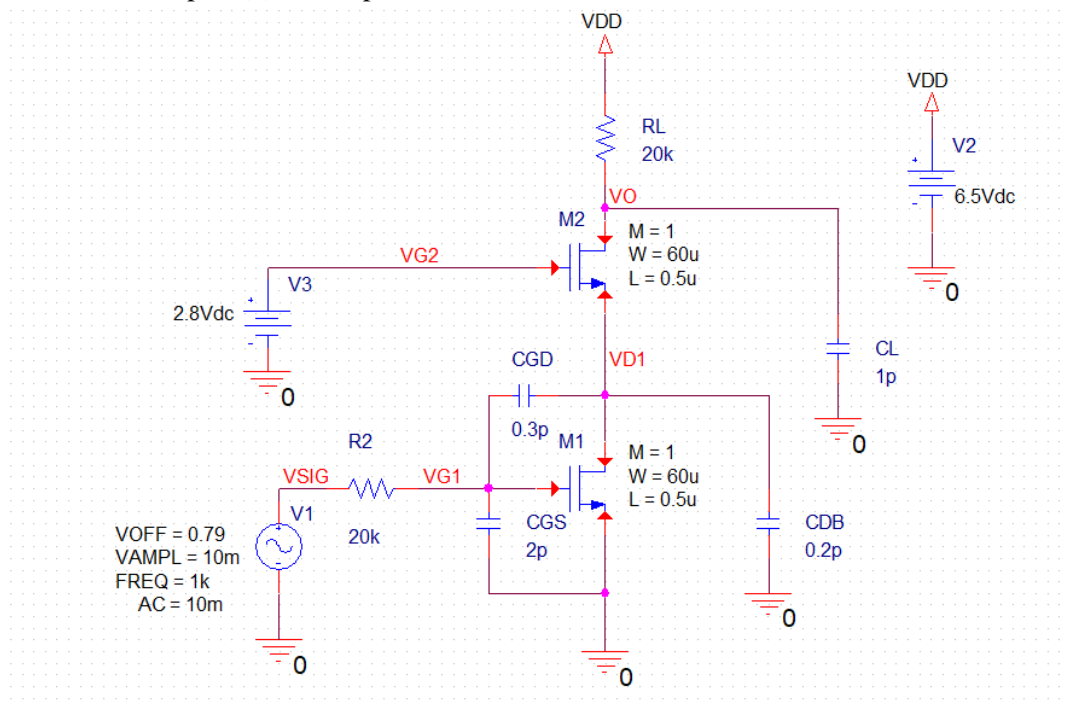4. The schematic for part (b) of this problem is shown below.



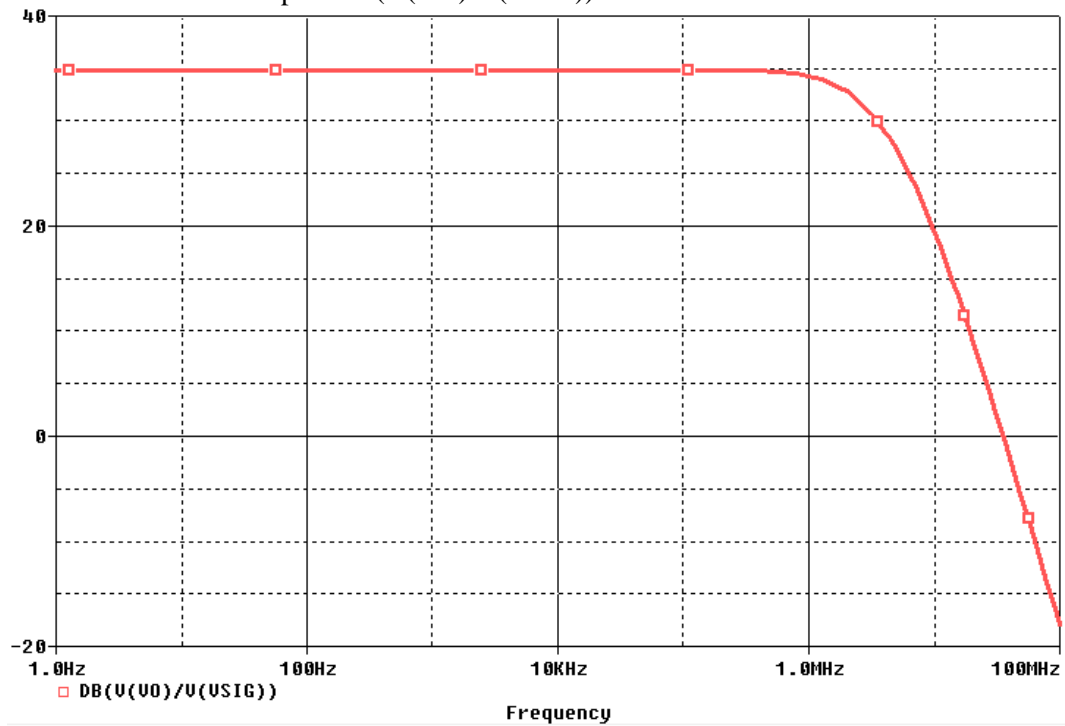5. Run an AC simulation and plot $DB(V(VO)/V(VSIG))$.



6. The unity gain frequency is at 35.5 MHz. This is significantly lower than the gain-bandwidth product because the AC response is decreasing faster than -20 dB/decade between 10 and 100 MHz.

Netlist:

For part (a), copy the netlist given below and paste it into a text file and save it with *.cir extension.

```

*****Problem: P10_57 (a) *****
***** Main circuit begins here*****
V1      VSIG 0 AC 10m
+SIN 0.79 10m 1k 0 0
RL      VD1 VDD 20k TC=0,0
R2      VG1 VSIG 20k TC=0,0
V2      VDD 0 5Vdc
M1      VD1 VG1 0 0 NMOS0P5
+ L=0.5u
+ W=60u
+ M=1
CGS     0 VG1 2p TC=0,0
CGD     VD1 VG1 0.3p TC=0,0
CL      0 VD1 1p TC=0,0
***** Main circuit ends here*****

***** NMOS model begins here *****
.model NMOS0P5 NMOS(Level=1 VTO=0.7 GAMMA=0.5 PHI=0.8
+          LD=0 WD=0 UO=460 LAMBDA=0.33 TOX=9.5E-9 PB=0.9 CJ=0.57E-3
+          CJSW=120E-12 MJ=0.5 MJSW=0.4 CGDO=0.4E-9 JS=10E-9 CGBO=0.38E-9
+          CGSO=0.4E-9)
***** NMOS model ends here *****

***** Analysis begins here*****
.OP
.AC DEC 20 1 100MEG
.PROBE
.END
***** Analysis ends here*****

```

For part (b), copy the netlist given below and paste it into a text file and save it with *.cir extension.

```

*****Problem: P10_57 (b) *****
***** Main circuit begins here*****
V2      VDD 0 6.5Vdc
RL      VO VDD 20k TC=0,0
M2      VO VG2 VD1 0 NMOS0P5
+ L=0.5u
+ W=60u
+ M=1
V3      VG2 0 2.8Vdc
V1      VSIG 0 AC 10m
+SIN 0.79 10m 1k 0 0
R2      VG1 VSIG 20k TC=0,0
CGS     0 VG1 2p TC=0,0
CDB     0 VD1 0.2p TC=0,0
CGD     VD1 VG1 0.3p TC=0,0
M1      VD1 VG1 0 0 NMOS0P5
+ L=0.5u
+ W=60u
+ M=1
CL      0 VO 1p TC=0,0
***** Main circuit ends here*****

***** NMOS model begins here *****
.model NMOS0P5 NMOS(Level=1 VTO=0.7 GAMMA=0.5 PHI=0.8
+          LD=0 WD=0 UO=460 LAMBDA=0.33 TOX=9.5E-9 PB=0.9 CJ=0.57E-3
+          CJSW=120E-12 MJ=0.5 MJSW=0.4 CGDO=0.4E-9 JS=10E-9 CGBO=0.38E-9
+          CGSO=0.4E-9)
***** NMOS model ends here *****

***** Analysis begins here*****
.OP
.AC DEC 20 1 100MEG
.PROBE

```

```
.END  
***** Analysis ends here*****
```