

Microelectronic Circuits International 8th Edition


A. Sedra, K.C. Smith
T. Chan Carusone, V. Gaudet

*Spice Problems Solutions
Chapter 11*


*Prepared by: Nijwm Wary
2019*

Problem: 11.14

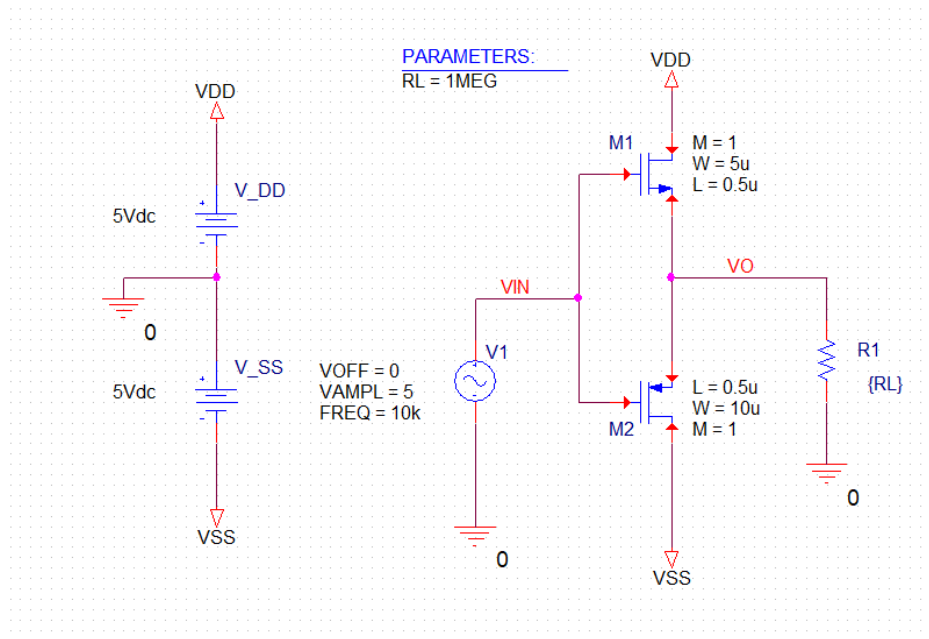
1. The schematic for this problem is shown below.



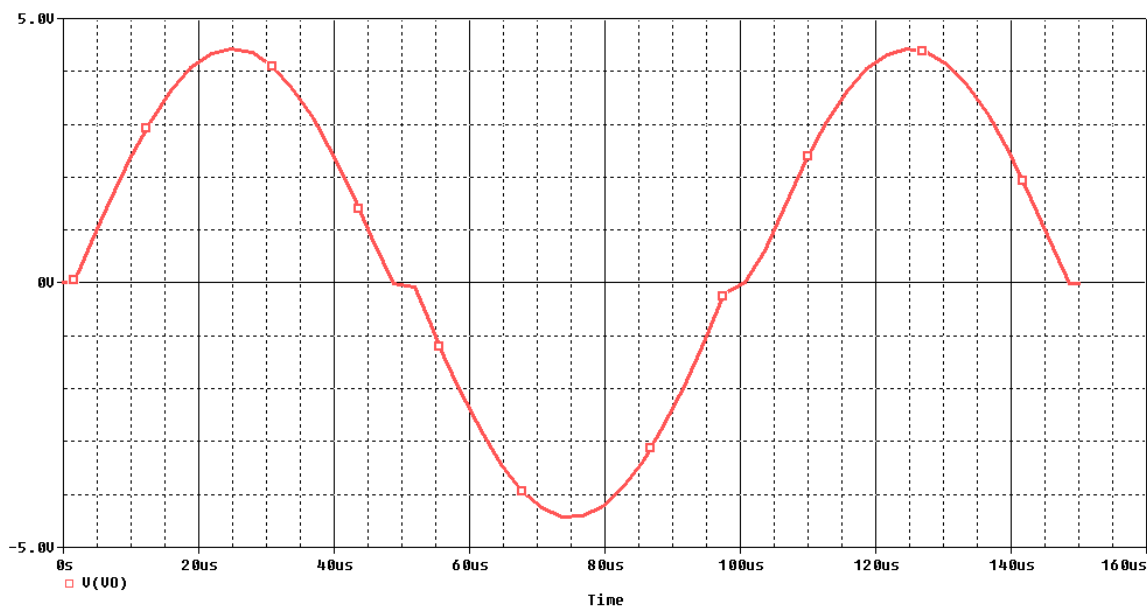2. Run the netlist and perform a transient analysis. Plot V(VIN) and V(VO) as shown below.



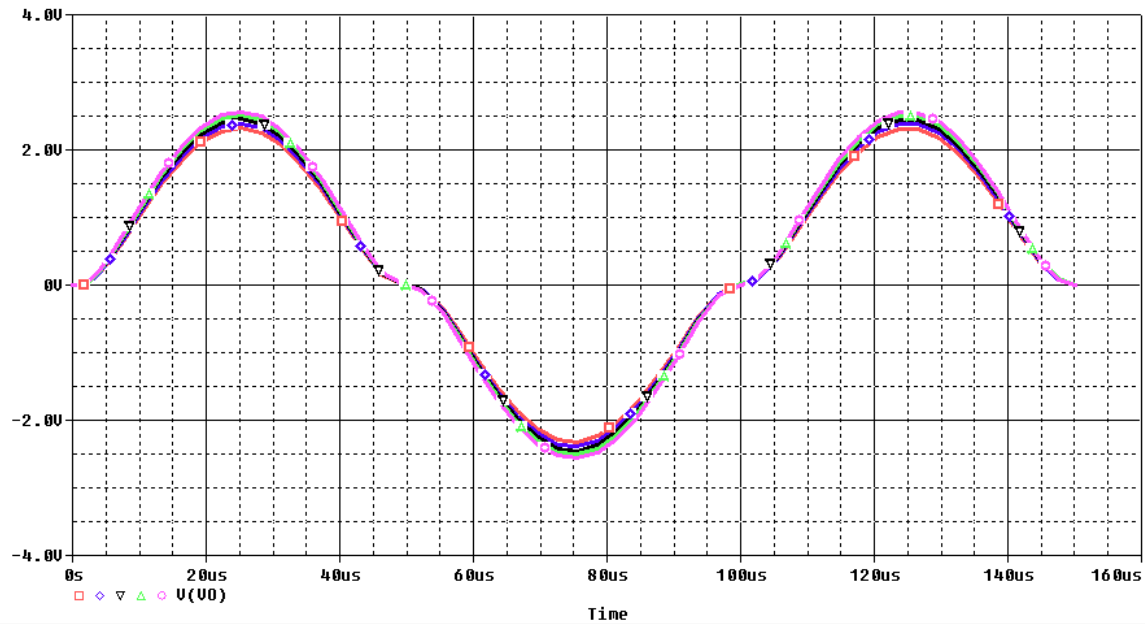3. The output V(VO) swings from 4.42 V to -4.41 V.
4. The cross over interval is $2 \times 2.9 \mu\text{s} = 5.8 \mu\text{s}$. So, it is 5.8 %.
5. Run the parametric analysis and sweep RL from 500Ω to 700Ω in steps of 50Ω or smaller. Plot V(VO) as shown below.



6. The output voltage is half of the input voltage when $R_L = 650 \Omega$.

Netlist:

Copy the netlist given below and paste it into a text file and save it with *.cir extension.

```

*****Problem: P12_12 *****
***** Main circuit begins here*****
V_DD      VDD 0 5Vdc
V1        VIN 0
+SIN 0 5 10k 0 0 0
R1        0 VO {RL}
V_SS      0 VSS 5Vdc
M2        VSS VIN VO VO PMOS0P5
+ L=0.5u
+ W=10u
+ M=1
M1        VDD VIN VO VO NMOS0P5
+ L=0.5u
+ W=5u
+ M=1
.PARAM   rl=1MEG
***** Main circuit ends here*****


***** NMOS and PMOS models begins here *****
.model NMOS0P5  NMOS(Level=1 VTO=0.5 GAMMA=0.5 PHI=0.8
+             LD=0 WD=0 UO=550 LAMBDA=0 TOX=9.5E-9 PB=0.9 CJ=0.57E-3
+             CJSW=120E-12 MJ=0.5 MJSW=0.4 CGDO=0.4E-9 JS=10E-9 CGBO=0.38E-9
+             CGSO=0.4E-9)
.model PMOS0P5  PMOS(Level=1 VTO=-0.5 GAMMA=0.45 PHI=0.8
+             LD=0 WD=0 UO=275 LAMBDA=0 TOX=9.5E-9 PB=0.9 CJ=0.93E-3
+             CJSW=170E-12 MJ=0.5 MJSW=0.35 CGDO=0.35E-9 JS=5E-9 CGBO=0.38E-9
+             CGSO=0.35E-9)
***** NMOS and PMOS model ends here *****

***** Analysis begins here*****
.TRAN     10uS 0.15mS
*.STEP    LIN      PARAM      RL      500 700 50
.PROBE
.END
***** Analysis ends here*****

```

Problem: 11.39

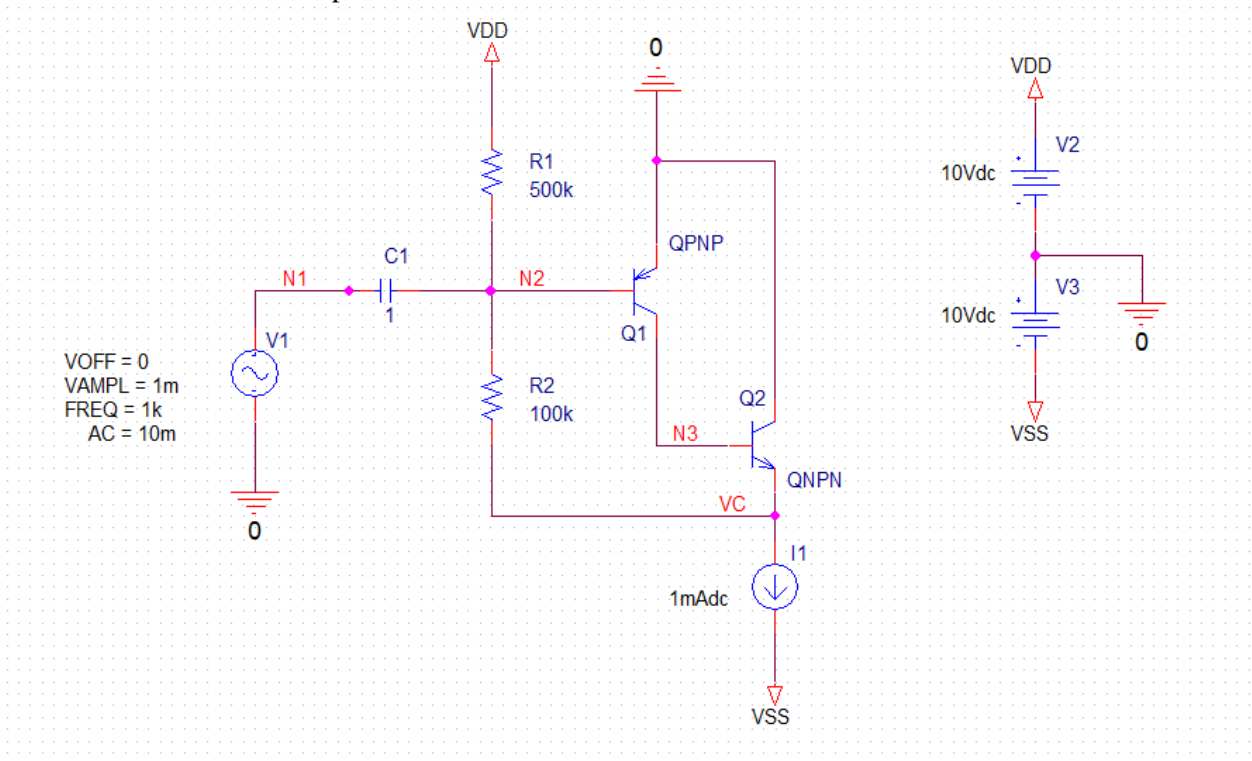1. The schematic for this problem is shown below




2. Run the netlist and perform an operating point analysis. The node voltages are

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(N1)	0.0000	(N2)	-.5957	(N3)	-2.1924	(VC)	-2.8567
(VDD)	10.0000	(VSS)	-10.0000				


3. The dc currents of the transistors are

NAME	Q1	Q2
MODEL	QPNP	QPNP
IB	-1.42E-06	1.44E-05
IC	-1.44E-05	9.63E-04

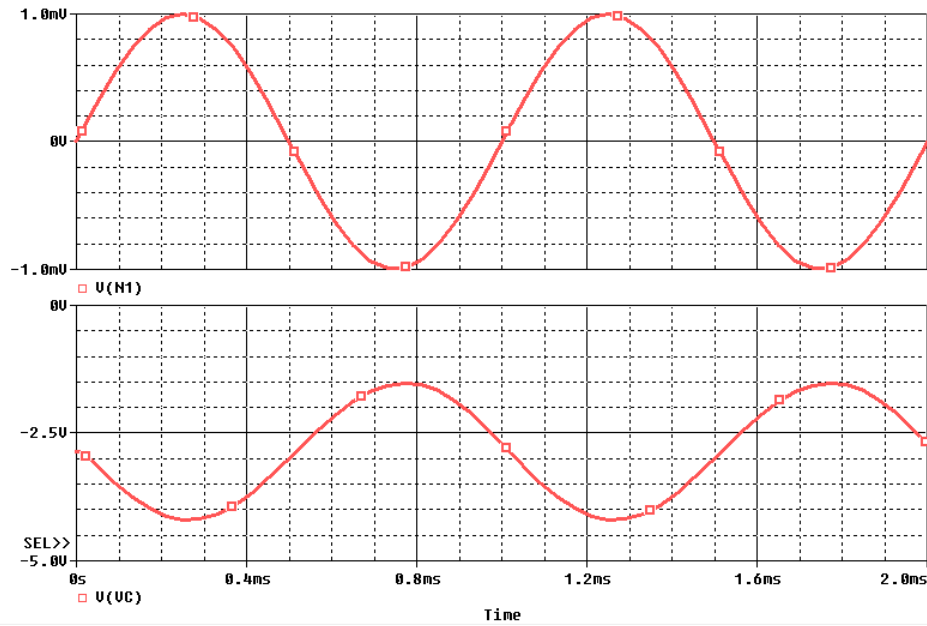4. Run the netlist and perform a transient analysis. Plot the voltages at the input V(N1) and output node V(VC) and find the gain.



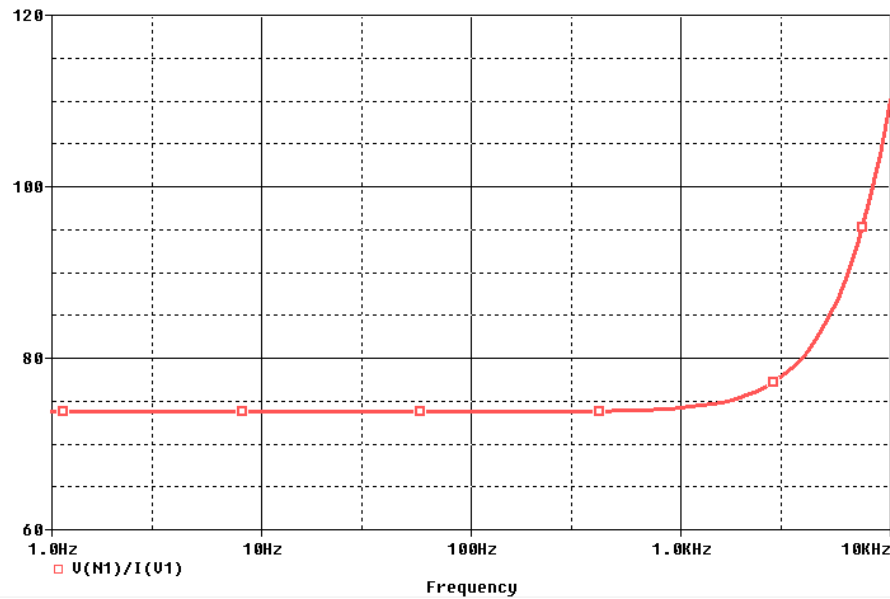5. The gain from this simulation is 1335 V/V.
6. Perform an AC simulation and calculate the input impedance by plotting the expression $V(N1)/I(V1)$.



7. The input impedance is 74 Ω .

Netlist:

Copy the netlist given below and paste it into a text file and save it with *.cir extension.

```

*****Problem: P12_39 *****
***** Main circuit begins here*****
R1      N2 VDD 500k TC=0,0
R2      VC N2 100k TC=0,0
I1      VC VSS DC 1mAdc
C1      N1 N2 1 TC=0,0
V1      N1 0 AC 10m
+SIN 0 1m 1k 0 0 0
V2      VDD 0 10Vdc
V3      0 VSS 10Vdc
Q1      N3 N2 0 QPNP
Q2      0 N3 VC QNPN
***** Main circuit ends here*****
***** Q2N3906 model begins here *****
.model QPNP PNP(Is=1.41f Xti=3 Eg=1.11 Vaf=100 Bf=10 Ne=1.5 Ise=0
+           Ikf=80m Xtb=1.5 Br=4.977 Nc=2 Isc=0 Ikr=0 Rc=2.5 Cjc=9.728p
+           Mjc=.5776 Vjc=.7 Fc=.5 Cje=8.063p Mje=.3677 Vje=.7 Tr=33.42n
+           Tf=179.3p Itf=.4 Vtf=4 Xtf=6 Rb=10)
***** Q2N3906 model ends here *****

***** Q2N3904 model begins here *****
.model QNPN NPN(Is=6.734f Xti=3 Eg=1.11 Vaf=100 Bf=100 Ne=1.259
+           Ise=6.734f Ikf=66.78m Xtb=1.5 Br=.7371 Nc=2 Isc=0 Ikr=0 Rc=1
+           Cjc=3.638p Mjc=.3085 Vjc=.7 Fc=.5 Cje=4.493p Mje=.2593 Vje=.7
+           Tr=239.5n Tf=301.2p Itf=.4 Vtf=4 Xtf=2 Rb=10)
***** Q2N3904 model ends here *****

***** Analysis begins here*****
.OP
*.TRAN 10uS 2mS
*.AC DEC 20 1 10K
.PROBE
.END
***** Analysis ends here*****

```