

Microelectronic Circuits International 8th Edition


A. Sedra, K.C. Smith
T. Chan Carusone, V. Gaudet

*Spice Problems Solutions
Chapter 10*

*Prepared by: Nijwm Wary
2019*

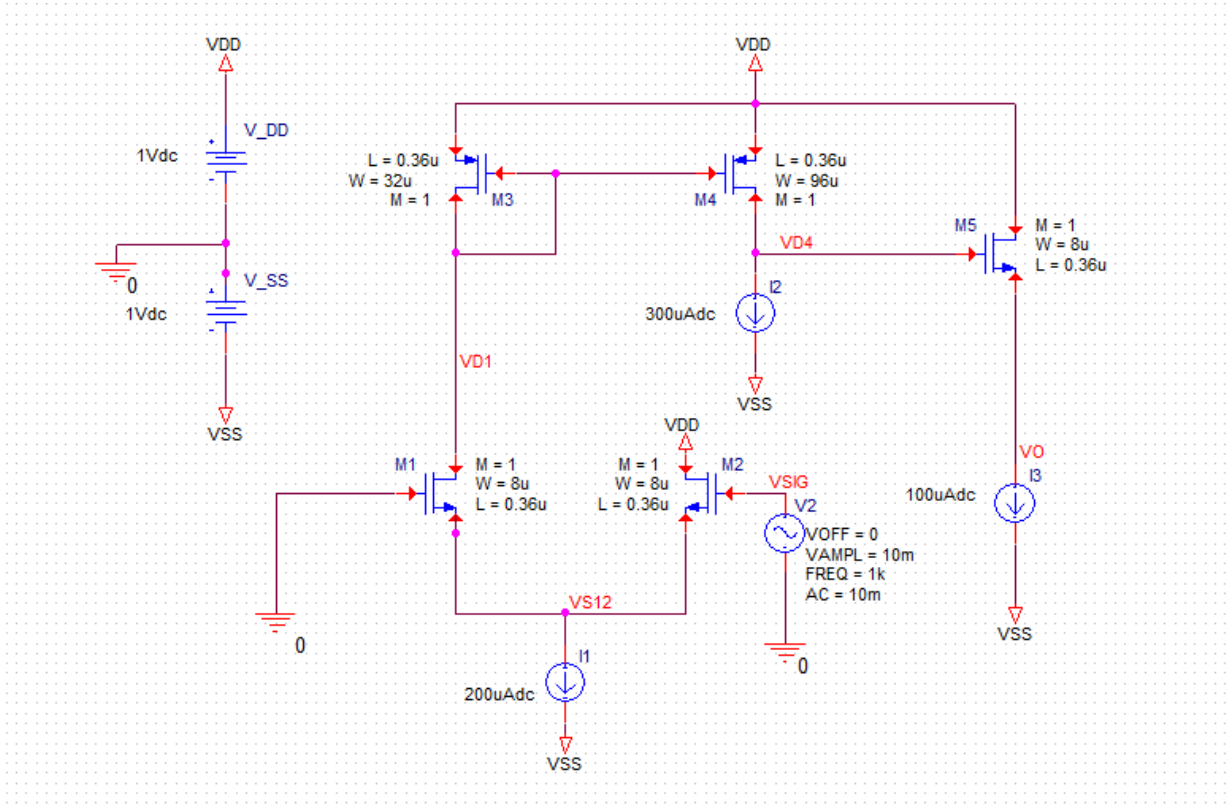Problem: 10.33

- The schematic with the feedback loop opened at the gate of Q_2 is shown below.




- Run the netlist and perform operating point analysis. The node voltages are given below.

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(V0)	-.1639	(VD1)	.5129	(VD4)	.2895	(VDD)	1.0000
(VSS)	-1.0000	(VS12)	-.4126	(VSIG)	0.0000		


- The currents, overdrive voltage (V_{DSAT}), g_m , and r_o ($1/g_{ds}$) of the transistors are tabulated by the operating point analysis below.

NAME	M1	M2	M3	M4	M5
MODEL	NMOS0P18	NMOS0P18	PMOS0P18	PMOS0P18	NMOS0P18
ID	9.48E-05	1.05E-04	-9.48E-05	-3.00E-04	1.00E-04
VGS	4.13E-01	4.13E-01	-4.87E-01	-4.87E-01	4.53E-01
VDS	9.25E-01	1.41E+00	-4.87E-01	-7.11E-01	1.16E+00
VBS	4.13E-01	4.13E-01	0.00E+00	0.00E+00	1.64E-01
VTH	2.82E-01	2.82E-01	-3.50E-01	-3.50E-01	3.23E-01
VDSAT	1.30E-01	1.30E-01	-1.37E-01	-1.37E-01	1.30E-01
GM	1.46E-03	1.62E-03	1.38E-03	4.38E-03	1.54E-03
GDS	2.11E-05	2.11E-05	2.34E-05	7.01E-05	2.11E-05

 
- Plot $V(VSIG)$ and $V(VO)$ as shown below and find the gain.



5. The gain is -28.7 V/V. This confirms that the feedback is negative.
6. The value of R_o can be calculated from g_{m5} and g_{ds5} . It is $1/g_{m5} || 1/g_{ds5} = 640 \Omega$.
7. The schematic for part (e) of this problem is shown below

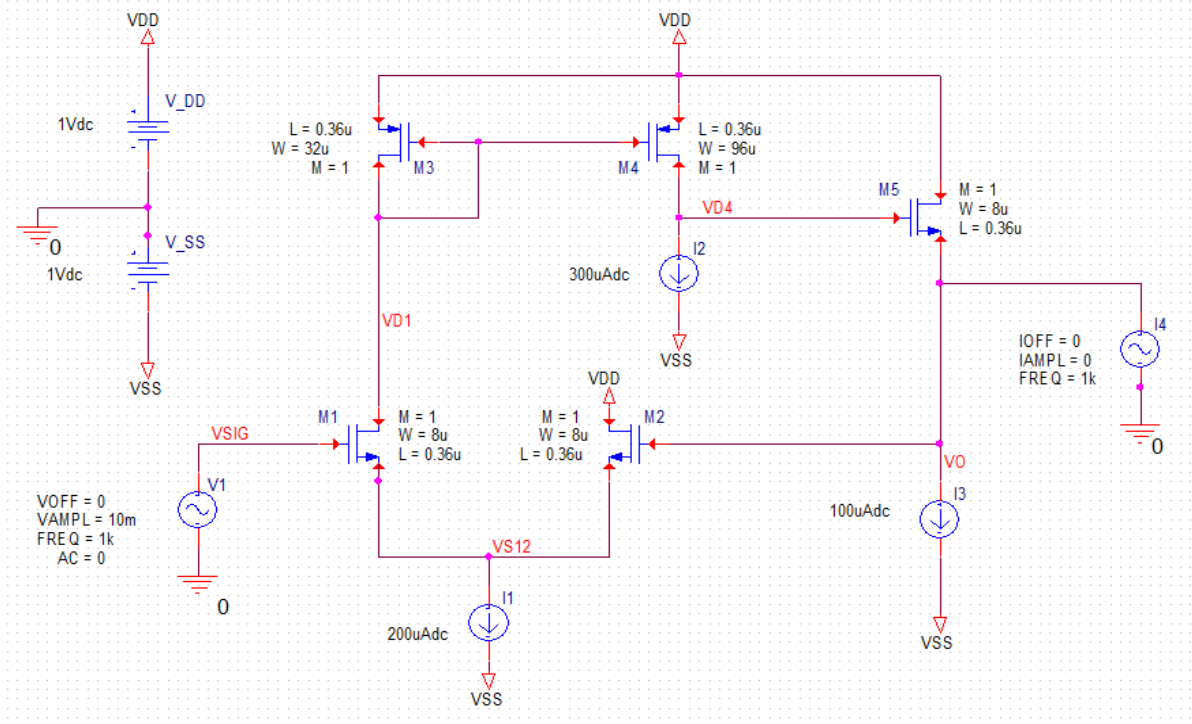


 8. Perform a transient analysis and plot $V(VO)$ and $V(VSIG)$ to find the gain. Note that in this case $I4$ has zero current amplitude.




9. The gain is 0.96 V/V.

 10. To calculate the output impedance, make the AC amplitude of $I4$ 1Aac and run an AC simulation. Plot $V(VO)/I(I4)$, as shown below




11. The output impedance is 20.66Ω

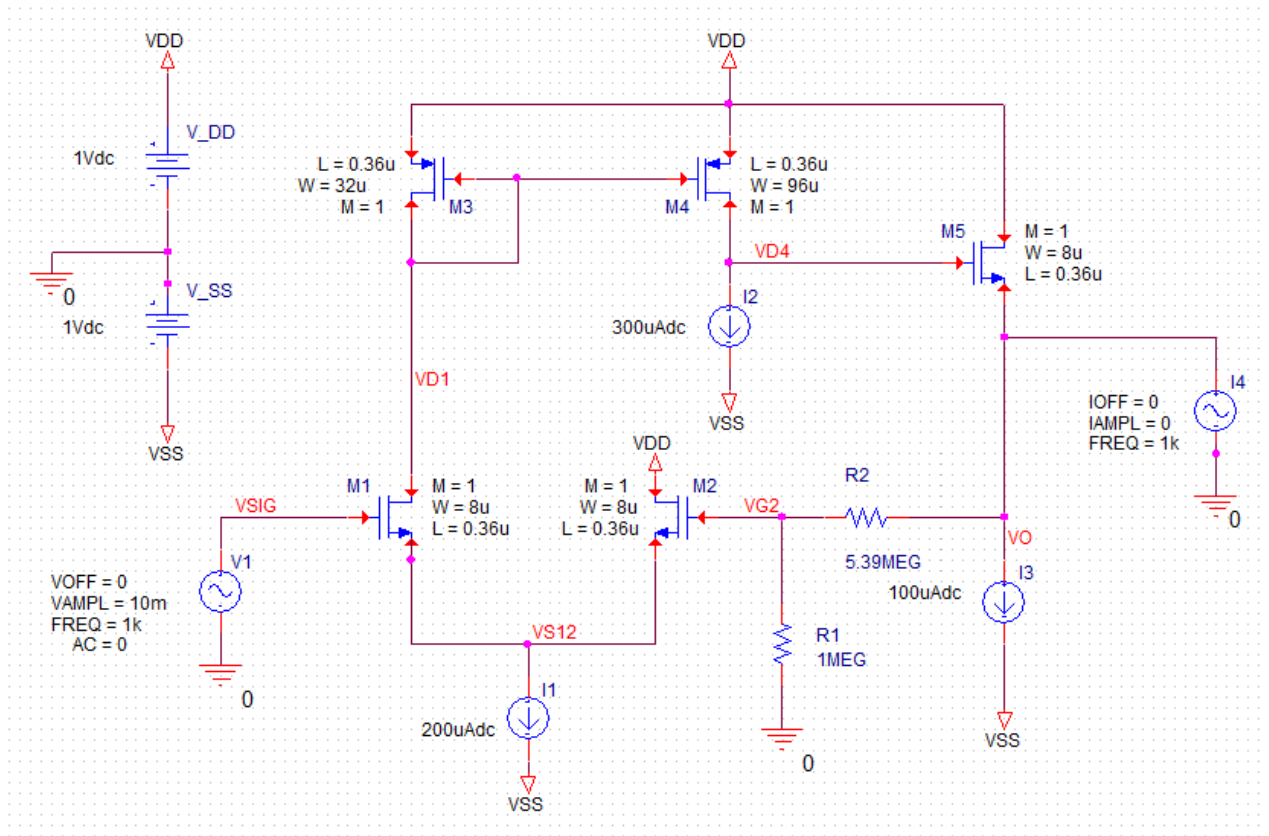12. The schematic for part (f) of this problem is shown below




 13. Perform the transient analysis and plot V(VO) and V(VSIG) and find out the new gain.



14. The gain is 5.13 V/V.

 15. To calculate the output impedance, run the AC simulation and plot $V(VO)/I(I4)$



16. The output impedance is 108.57 Ω .

Netlist:

For part (b) and (c), copy the netlist given below and paste it into a text file and save it with *.cir extension.

```
*****Problem: P11_37(b), (c) and (d) *****
***** Main circuit begins here*****
V_DD      VDD 0 1Vdc
I3        VO VSS DC 100uAdc
I2        VD4 VSS DC 300uAdc
I1        VS12 VSS DC 200uAdc
V_SS      0 VSS 1Vdc
M1        VD1 0 VS12 0 NMOS0P18
+ L=0.36u
+ W=8u
+ M=1
M2        VDD VSIG VS12 0 NMOS0P18
+ L=0.36u
+ W=8u
+ M=1
M3        VD1 VD1 VDD VDD PMOS0P18
+ L=0.36u
+ W=32u
+ M=1
M4        VD4 VD1 VDD VDD PMOS0P18
+ L=0.36u
+ W=96u
+ M=1
M5        VDD VD4 VO 0 NMOS0P18
+ L=0.36u
```

```

+ W=8u
+ M=1
V2      VSIG 0 AC 10m
+SIN 0 10m 1k 0 0 0
***** Main circuit ends here*****

***** PMOS model begins here *****
*          Level-1 Model for PMOS in model 0.18um CMOS Technology
.model PMOS0P18      PMOS(Level=1 VTO=-0.35 GAMMA=0.3 PHI=0.8
+          LD=0 WD=0 UO=118 LAMBDA=0.28 TOX=4.08E-9 PB=0.9)
***** PMOS model ends here *****

***** NMOS model begins here *****
*          Level-1 Model for NMOS in model 0.18um CMOS Technology
.model NMOS0P18      NMOS(Level=1 VTO=0.35 GAMMA=0.3 PHI=0.84
+          LD=0 WD=0 UO=473 LAMBDA=0.28 TOX=4.08E-9 PB=0.9)
***** NMOS model ends here *****

***** Analysis begins here*****
.OP
.TRAN  0.01ms  2ms
.PROBE
.END
***** Analysis ends here*****

```

For part (e), copy the netlist given below and paste it into a text file and save it with *.cir extension.

```

*****Problem: P11_37(e) *****
***** Main circuit begins here*****
V_DD      VDD 0 1Vdc
I3        VO VSS DC 100uAdc
I2        VD4 VSS DC 300uAdc
I1        VS12 VSS DC 200uAdc
V_SS      0 VSS 1Vdc
M1        VD1 VSIG VS12 0 NMOS0P18
+ L=0.36u
+ W=8u
+ M=1
M2        VDD VO VS12 0 NMOS0P18
+ L=0.36u
+ W=8u
+ M=1
M3        VD1 VD1 VDD VDD PMOS0P18
+ L=0.36u
+ W=32u
+ M=1
M4        VD4 VD1 VDD VDD PMOS0P18
+ L=0.36u
+ W=96u
+ M=1
M5        VDD VD4 VO 0 NMOS0P18
+ L=0.36u
+ W=8u
+ M=1
V1        VSIG 0 AC 0
+SIN 0 10m 1k 0 0 0
I4        VO 0 DC 0Adc AC 1Aac
+SIN 0 0 1k 0 0 0

***** Main circuit ends here*****

***** PMOS model begins here *****
*          Level-1 Model for PMOS in model 0.18um CMOS Technology
.model PMOS0P18      PMOS(Level=1 VTO=-0.35 GAMMA=0.3 PHI=0.8
+          LD=0 WD=0 UO=118 LAMBDA=0.28 TOX=4.08E-9 PB=0.9)
***** PMOS model ends here *****

```

```

***** NMOS model begins here *****
*           Level-1 Model for NMOS in model 0.18um CMOS Technology
.model NMOS0P18      NMOS(Level=1 VTO=0.35 GAMMA=0.3 PHI=0.84
+           LD=0 WD=0 UO=473 LAMBDA=0.28 TOX=4.08E-9 PB=0.9)
***** NMOS model ends here *****

***** Analysis begins here*****
.OP
.TRAN 0.01mS 2mS
*.AC DEC 20 1 100K
.PROBE
.END
***** Analysis ends here*****

```

For part (f), copy the netlist given below and paste it into a text file and save it with *.cir extension.

```

*****Problem: P11_37(f) *****
***** Main circuit begins here*****
V_DD      VDD 0 1Vdc
I3        VO VSS DC 100uAdc
I2        VD4 VSS DC 300uAdc
I1        VS12 VSS DC 200uAdc
V_SS      0 VSS 1Vdc
M1        VD1 VSIG VS12 0 NMOS0P18
+ L=0.36u
+ W=8u
+ M=1
M2        VDD VG2 VS12 0 NMOS0P18
+ L=0.36u
+ W=8u
+ M=1
M3        VD1 VD1 VDD VDD PMOS0P18
+ L=0.36u
+ W=32u
+ M=1
M4        VD4 VD1 VDD VDD PMOS0P18
+ L=0.36u
+ W=96u
+ M=1
M5        VDD VD4 VO 0 NMOS0P18
+ L=0.36u
+ W=8u
+ M=1
V1        VSIG 0 AC 0
+SIN 0 10m 1k 0 0 0
I4        VO 0 DC 0Adc AC 0Aac
+SIN 0 0 1k 0 0 0
R1        0 VG2 1MEG TC=0,0
R2        VO VG2 5.39MEG TC=0,0
***** Main circuit ends here*****

***** PMOS model begins here *****
*           Level-1 Model for PMOS in model 0.18um CMOS Technology
.model PMOS0P18      PMOS(Level=1 VTO=-0.35 GAMMA=0.3 PHI=0.8
+           LD=0 WD=0 UO=118 LAMBDA=0.28 TOX=4.08E-9 PB=0.9)
***** PMOS model ends here *****


***** NMOS model begins here *****
*           Level-1 Model for NMOS in model 0.18um CMOS Technology
.model NMOS0P18      NMOS(Level=1 VTO=0.35 GAMMA=0.3 PHI=0.84
+           LD=0 WD=0 UO=473 LAMBDA=0.28 TOX=4.08E-9 PB=0.9)
***** NMOS model ends here *****

***** Analysis begins here*****
.OP
.TRAN 0.01mS 2mS
*.AC DEC 20 1 100K
.PROBE
.END
***** Analysis ends here*****

```

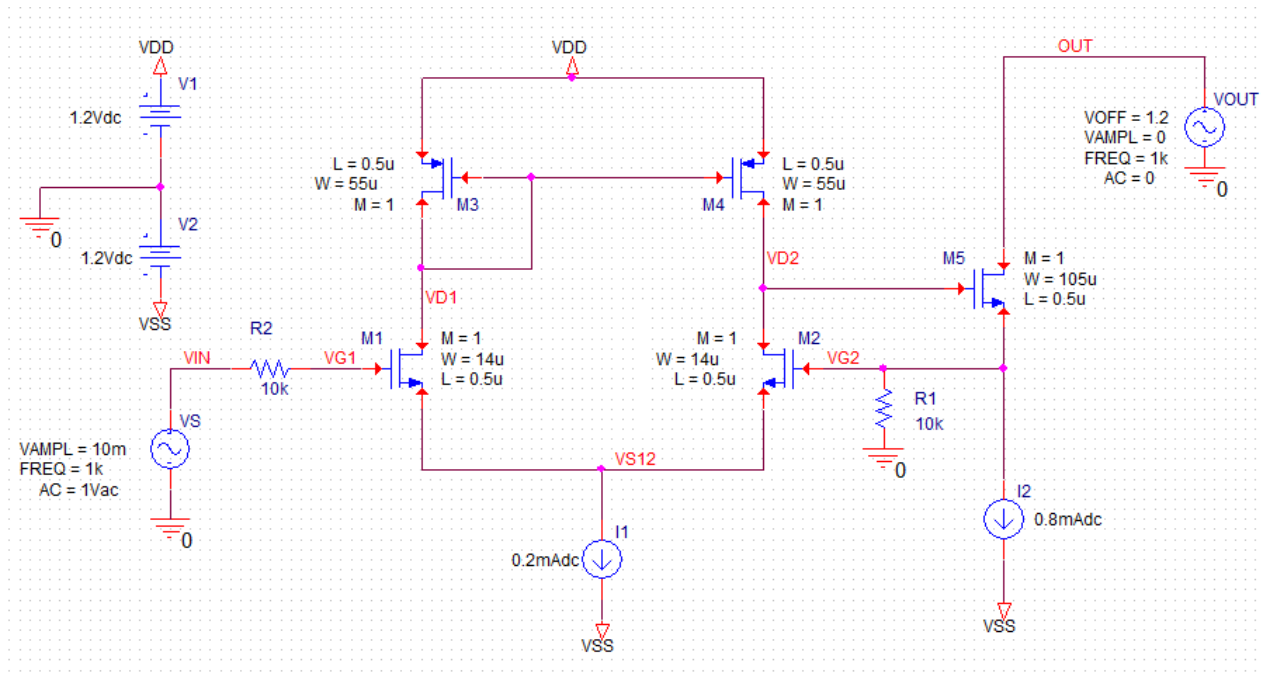
Problem: 10.51

- The schematic for this problem is shown below.




- For part (a), run the netlist and perform operating point analysis and find out the node voltages and currents.

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(OUT)	1.2000	(VD1)	.5945	(VD2)	.6072	(VDD)	1.2000
(VG1)	0.0000	(VG2)	-122.1E-06	(VIN)	0.0000	(VSS)	-1.2000
(VS12)	-.6008						

NAME	M1	M2	M3	M4	M5
MODEL	NMOS0P5	NMOS0P5	PMOS0P5	PMOS0P5	NMOS0P5
ID	1.00E-04	1.00E-04	-1.00E-04	-1.00E-04	8.00E-04
VGS	6.01E-01	6.01E-01	-6.06E-01	-6.06E-01	6.07E-01
VDS	1.20E+00	1.21E+00	-6.06E-01	-5.93E-01	1.20E+00
VBS	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00
VTH	4.00E-01	4.00E-01	-4.00E-01	-4.00E-01	4.00E-01
VDSAT	2.01E-01	2.01E-01	-2.06E-01	-2.06E-01	2.07E-01

 - For part (c), perform AC analysis and plot I(VOUT)/V(VIN) as shown below.




4. So, A_f is 99 $\mu A/V$.

5. For part (d) to calculate the R_{out} , make the AC amplitude of V_S zero and that of V_{OUT} 1Vac as shown below.

```


VS          VIN 0  AC 0Vac
.
.
VOUT       OUT 0  AC 1Vac
    
```

 6. Perform an AC analysis and plot $V(OUT) / I(VOUT)$ as shown below.




7. So, R_{out} is 214.4 $M\Omega$.

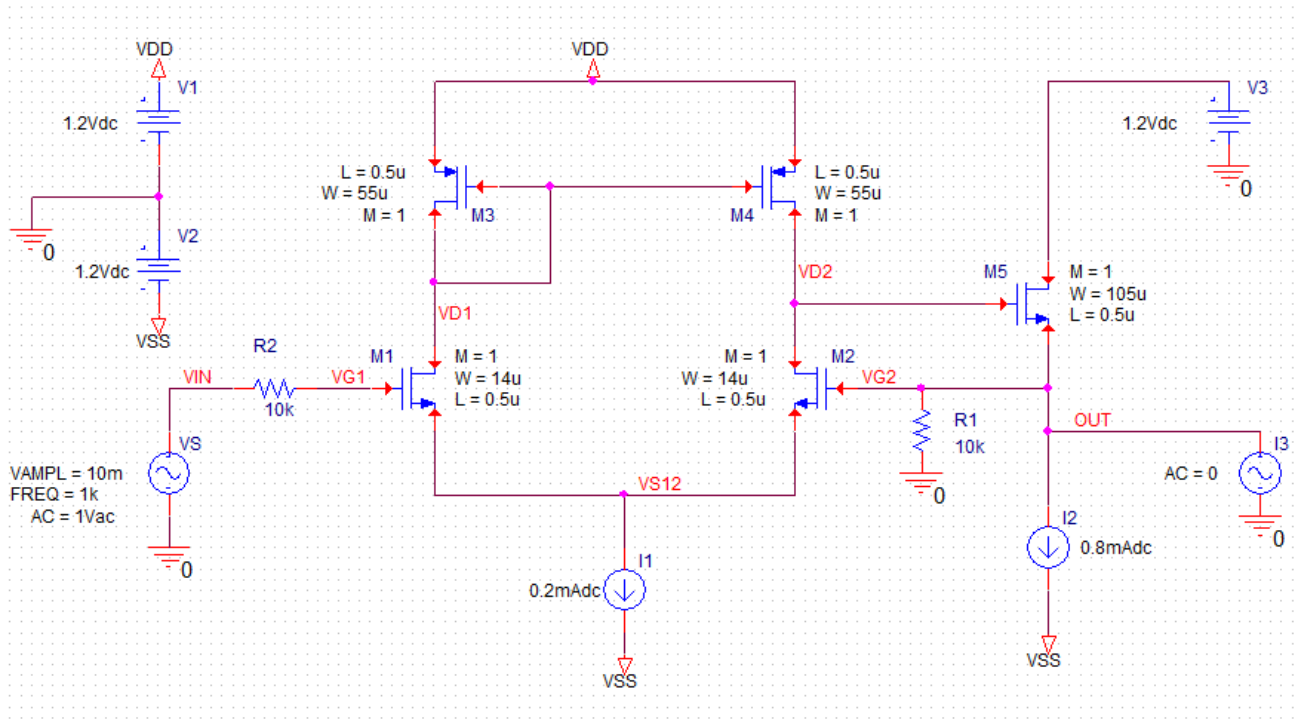8. The schematic for part (e) is shown below




 9. Run the netlist and plot the $DB(V(OUT)/ V(VIN))$ in dB.



10. The gain is 0.98 V/V

 11. Now make the AC amplitude of VS zero and the AC amplitude of I3 as 1. Then run the AC simulation again and plot V(OUT)/I(I3) as shown below



12. The output impedance is 1.07Ω .

Netlist:

Copy the netlist given below and paste it into a text file and save it with *.cir extension.

```
*****Problem: P11_58*****
***** Main circuit begins here*****
M1      VD1 VG1 VS12 VS12 NMOS0P5
+ L=0.5u
+ W=14u
+ M=1
M2      VD2 VG2 VS12 VS12 NMOS0P5
+ L=0.5u
+ W=14u
+ M=1
M3      VD1 VD1 VDD VDD PMOS0P5
+ L=0.5u
+ W=55u
+ M=1
M4      VD2 VD1 VDD VDD PMOS0P5
+ L=0.5u
+ W=55u
+ M=1
I1      VS12 VSS DC 0.2mAdc
M5      OUT VD2 VG2 VG2 NMOS0P5
+ L=0.5u
+ W=105u
+ M=1
I2      VG2 VSS DC 0.8mAdc
V1      VDD 0 1.2Vdc
V2      0 VSS 1.2Vdc
VS      VIN 0 AC 1Vac
+SIN 0 10m 1k 0 0 0
R1      0 VG2 10k TC=0,0
R2      VG1 VIN 10k TC=0,0
VOUT    OUT 0 AC 0Vac
+SIN 1.2 0 1k 0 0 0

***** Main circuit ends here*****
```

```

***** PMOS model begins here *****
.model PMOS0P5 PMOS(Level=1 VTO=-0.4 GAMMA=0.05 PHI=0.8
+
LD=0 WD=0 UO=115 LAMBDA=0.05 TOX=9.5E-9 PB=0.9)
***** PMOS model ends here *****

***** NMOS model begins here *****
.model NMOS0P5 NMOS(Level=1 VTO=0.4 GAMMA=0.05 PHI=0.8
+
LD=0 WD=0 UO=460 LAMBDA=0.05 TOX=9.5E-9 PB=0.9)
***** NMOS model ends here *****

***** Analysis begins here*****
.OP
.AC DEC 20 1 100K
.PROBE
.END
***** Analysis ends here*****

```

Copy the netlist given below for part (e) and paste it into a text file and save it with *.cir extension.

```

*****Problem: P11_58 (e)*****
***** Main circuit begins here*****
M1 VD1 VG1 VS12 0 NMOS0P5
+ L=0.5u
+ W=14u
+ M=1
M2 VD2 OUT VS12 0 NMOS0P5
+ L=0.5u
+ W=14u
+ M=1
M3 VD1 VD1 VDD VDD PMOS0P5
+ L=0.5u
+ W=55u
+ M=1
M4 VD2 VD1 VDD VDD PMOS0P5
+ L=0.5u
+ W=55u
+ M=1
I1 VS12 VSS DC 0.2mAdc
M5 N16841 VD2 OUT 0 NMOS0P5
+ L=0.5u
+ W=105u
+ M=1
I2 OUT VSS DC 0.8mAdc
V1 VDD 0 1.2Vdc
V2 0 VSS 1.2Vdc
VS VIN 0 AC 1Vac
+SIN 0 10m 1k 0 0 0
R1 0 OUT 10k TC=0,0
R2 VG1 VIN 10k TC=0,0
V3 N16841 0 1.2Vdc
I3 OUT 0 DC 0Adc AC 0
+SIN 0 0 1 0 0 0
***** Main circuit ends here*****

***** PMOS model begins here *****
.model PMOS0P5 PMOS(Level=1 VTO=-0.4 GAMMA=0.05 PHI=0.8
+
LD=0 WD=0 UO=115 LAMBDA=0.05 TOX=9.5E-9 PB=0.9)
***** PMOS model ends here *****

***** NMOS model begins here *****
.model NMOS0P5 NMOS(Level=1 VTO=0.4 GAMMA=0.05 PHI=0.8
+
LD=0 WD=0 UO=460 LAMBDA=0.05 TOX=9.5E-9 PB=0.9)
***** NMOS model ends here *****


***** Analysis begins here*****
.AC DEC 20 1 100K
.PROBE
.END

```

***** Analysis ends here*****

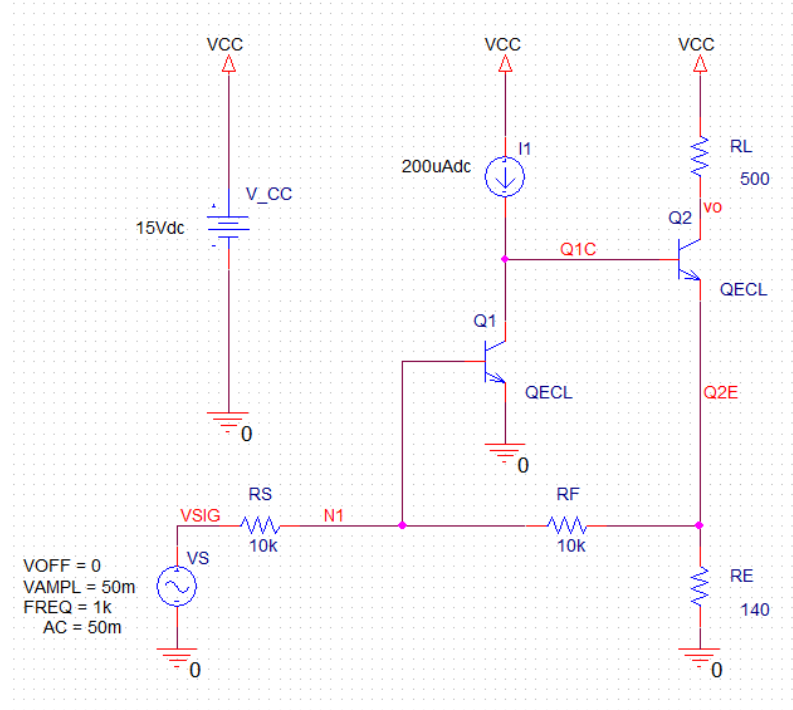Problem: 10.75

- The schematic for this problem is shown below




- The node voltages are

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(N1)	.6006	(VO)	10.6840	(Q1C)	1.9391	(Q2E)	1.2162
(VCC)	15.0000	(VSIG)	0.0000				


- The operating conditions of the transistors are

NAME	Q1	Q2
MODEL	QECL	QECL
IB	1.51E-06	1.17E-04
IC	8.27E-05	8.63E-03
VBE	6.01E-01	7.23E-01
VBC	-1.34E+00	-8.75E+00
VCE	1.94E+00	9.47E+00
BETADC	5.49E+01	7.36E+01
GM	3.19E-03	3.02E-01

 - Run the transient simulation and plot V(VO) and V(VSIG) to get the gain



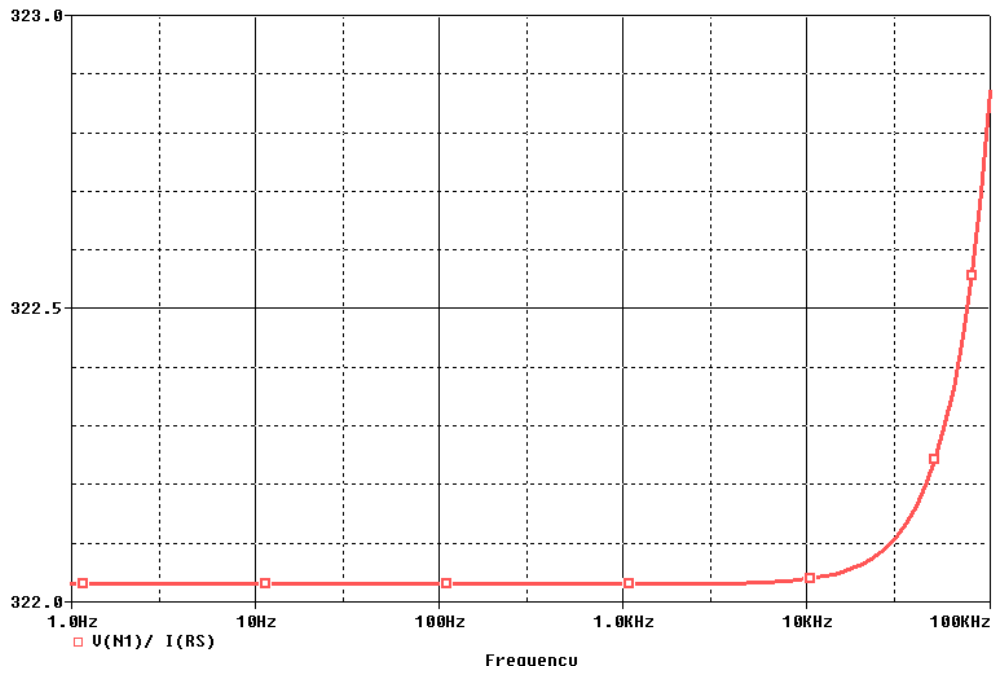5. The gain is 3.3 V/V.
6. Plot $V(N1)/I(RS)$ to calculate the input resistance.



7. The input resistance is 322 Ω .

Netlist:

For part (b) and (c), copy the netlist given below and paste it into a text file and save it with *.cir extension.

```

*****Problem: P11_79 *****
***** Main circuit begins here*****
RS      VSIG N1  10k
RF      N1 Q2E 10k
RE      0 Q2E  140
I1      VCC Q1C DC 200uAdc
RL      VO VCC  500
V_CC    VCC 0 15Vdc
Q1      Q1C N1 0 QECL
Q2      VO Q1C Q2E QECL
VS      VSIG 0  AC 50m
+SIN 0 50m 1k 0 0 0
***** Main circuit ends here*****

***** Model for ECL BJT begins here*****
.model QECL  NPN(Is=6.734f Xti=3 Eg=1.11 Vaf=100 Bf=100 Ne=1.259
+           Ise=6.734f Ikf=66.78m Xtb=1.5 Br=.7371 Nc=2 Isc=0 Ikr=0 Rc=1
+           Cjc=3.638p Mjc=.3085 Vjc=0.70 Fc=.5 Cje=4.493p Mje=.2593 Vje=0.70
+           Tr=239.5n Tf=301.2p Itf=.4 Vtf=4 Xtf=2 Rb=10)
***** Model for ECL BJT begins here*****

***** Analysis begins here*****
.OP
.TRAN  0.01mS  2mS
*.AC  DEC  20  1 100K
.PROBE
.END
***** Analysis ends here*****

```