

Microelectronic Circuits

8th Edition


A. Sedra, K.C. Smith
T. Chan Carusone, V. Gaudet

Spice Problems Solutions
Chapter 6

Prepared by: Nijwm Wary
2019

Problem: 6.49

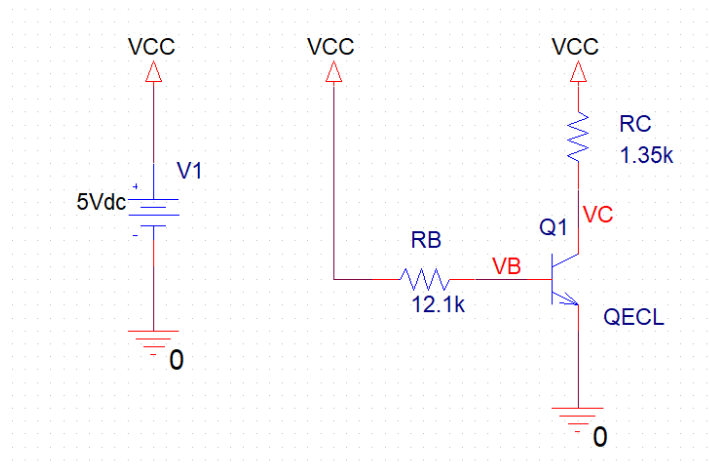1. The schematic for this problem is shown below.



2. Run the netlist and calculate the operating point. The total power drawn from the supply is 20mW as shown below

```
VOLTAGE SOURCE CURRENTS
NAME          CURRENT
V1            -4.001E-03

TOTAL POWER DISSIPATION  2.00E-02  WATTS
```

3. The current I_B and I_C are given below. The forced β is the ratio $I_C/I_B=10.4$.

```
NAME      Q1
MODEL    QECL
IB        3.48E-04
IC        3.65E-03
VBE       7.87E-01
VBC       7.19E-01
VCE       6.84E-02
BETADC    1.05E+01
```

Netlist:


Copy the netlist given below and paste it into a text file and save it with *.cir extension.

```
*****Problem: P6_49 *****
***** Main circuit begins here*****
Q1      VC VB 0 QECL
RB      VCC VB 12.1k TC=0,0
RC      VC VCC 1.35k TC=0,0
V1      VCC 0 5Vdc
***** Main circuit ends here*****
***** Model for ECL BJT begins here*****
.model QECL NPN(Is=0.26fA Bf=100 Br=1 Tf=0.1ns Cje=1pF Cjc=1.5pF Va=100)
***** Model for ECL BJT begins here*****

***** Analysis begins here*****
.OP
***** Analysis ends here*****
```

Problem: 6.60

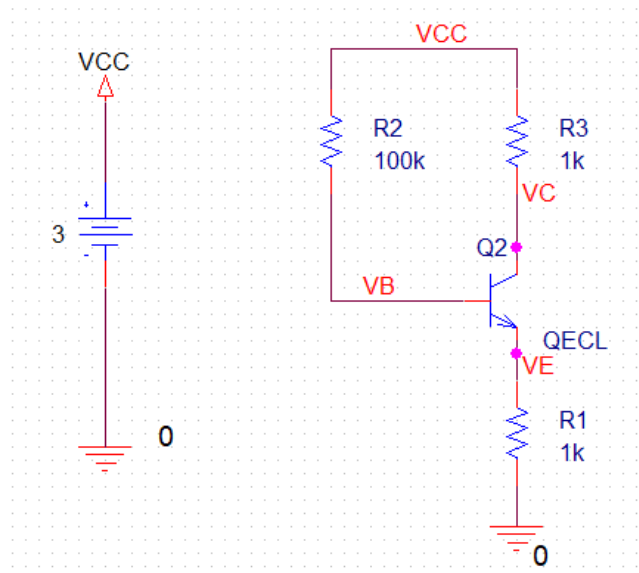1. The schematic for this problem is shown below.



2. Run the netlist and calculate the operating point. Open the “output file” and see the node voltages and find out V_B , V_C and V_E .

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(VB)	1.8818	(VC)	1.8818	(VE)	1.1294	(VCC)	3.0000

3. Change R_2 to $10\text{ k}\Omega$ and $1\text{ k}\Omega$ and find the voltages again.

Netlist:

Copy the netlist given below and paste it into a text file and save it with *.cir extension.

```

*****Problem: P 6.60 *****
***** Main circuit begins here*****
Q2      VC VB VE QECL
R1      0 VE 1k TC=0,0
R2      VB VCC 100k TC=0,0
R3      VC VCC 1k TC=0,0
V_sup   VCC 0 3
***** Main circuit ends here*****

***** Model for ECL BJT begins here*****
.model QECL NPN(Is=0.26fA Bf=100 Br=1 Tf=0.1ns Cje=1pF Cjc=1.5pF Va=100)
***** Model for ECL BJT begins here*****

***** Analysis begins here*****
.OP
.END
***** Analysis ends here*****

```